

--	--	--	--	--	--	--	--	--	--

First/Second Semester B.E. Degree Examination, Dec.2017/Jan.2018
Basic Electronics

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Choose the correct answers for the following : (04 Marks)
- i) A diode has _____ terminals and _____ junctions
- A) 2, 2 B) 1, 1
 C) 2, 1 D) 1, 2
- ii) The line connecting I_F and V_F on the diode forward characteristics is called as _____ line
- A) Power B) Forward
 C) AC load D) DC load
- iii) The intersection of the diode forward characteristics and the DC load line is called as
- A) P Point B) Q Point
 C) R Point D) S Point
- iv) A filter connected to a rectifier output removes
- A) Ripple B) Attenuation
 C) Noise D) Unwanted frequency.
- b. Draw a Labelled circuit diagram of a half wave rectifier with C filter and explain the associate waveforms. (08 Marks)
- c. Design Zener diode voltage regulator to meet the following specifications :
- Unregulated DC input voltage V_i : 8V to 12V
 Regulated DC output voltage V_o : 5V
 Minimum Zener current I_{Zmin} : 5mA
 Maximum Zener current I_{Zmax} : 80mA
 Load current I_L : 0 t 20mA. (08 Marks)
- 2 a. Choose the correct answers for the following : (04 Marks)
- i) β_{DC} of a transistor is given by
- A) $\frac{I_B}{I_C}$ B) $\frac{I_C}{I_E}$
 C) $\frac{I_C}{I_B}$ D) $\frac{I_E}{I_C}$
- ii) The common–Emitter output characteristics waveform is plotted as _____ Vs _____
- A) V_{CE}, I_C B) V_{BE}, I_C
 C) V_{CE}, I_E D) V_{BE}, I_E
- iii) The DC loadline drawn on the CE output characteristics has a slope of
- A) $1/RC$ B) $-RC$
 C) R_C D) $-1/R_C$
- iv) For the normal operation of a transistor, Base–Emitter junction is _____ biased and collector–base junction is _____ biased
- A) FB, FB B) FB, RB
 C) RB, FB D) RB, RB
- b. Draw the circuit diagram of a PNP transistor in common –base configuration and explain its input and output characteristics. (08 Marks)
- c. Find α_{DC} , I_B and β_{DC} for a transistor with $I_C = 2.5mA$ and $I_E = 2.55mA$. (04 Marks)
- d. Explain the significance of active, cutoff and saturation regions in a transistor. (04 Marks)

3 a. Choose the correct answers for the following :

(04 Marks)

- i) Biasing a transistor means
 A) Applying heat
 B) Discharging
 C) Displacing
 D) Applying Voltages
- ii) A transistor in CE configuration having collector current zero has V_{CE} as
 A) $\frac{V_{CC}}{R_C + R_E}$
 B) $\frac{V_{CC}}{R_C}$
 C) V_{CC}
 D) $\frac{V_{CC}}{R_E}$
- iii) The biasing circuit which gives most stable operating point is
 A) Base bias
 B) Voltage -divider
 C) Collector-base
 D) Emitter
- iv) The stability factor $S = 1 + \beta_{DC}$ applies to _____ biasing
 A) Base
 B) Voltage-divider
 C) Collector-base
 D) Emitter.
- b. Sketch the circuit of voltage divider bias and discuss its approximate analysis. (08 Marks)
- c. A collector-to-base bias circuit shown in Fig.Q3(c) has $V_{CC} = 15V$, $R_C = 1.8k\Omega$, $R_B = 39k\Omega$, $\beta_{DC} = 50$ and $V_{BE} = 0.7V$. Determine the I_C and V_{CE} levels. Draw the DC load line and locate the Q point. (08 Marks)

 


Fig.Q3(c)

4 a. Choose the correct answers for the following :

(04 Marks)

- i) An SCR is a _____ with a gate
 A) Oscillator
 B) Rectifier
 C) Regulator
 D) Clipper
- ii) Over voltage protection circuit in an SCR is called as
 A) Hen bar
 B) Bird bar
 C) Sparrow bar
 D) Crow bar
- iii) An UJT has _____ bases
 A) Two
 B) Three
 C) Zero
 D) One
- iv) Pinch-off voltage is normally associated with
 A) Diode
 B) UJT
 C) JFET
 D) SCR.
- b. Draw a circuit diagram for UJT and sketch and explain the V-I characteristics mentioning different regions. (08 Marks)
- c. Explain the structure and operation of an n-channel JFET. (04 Marks)
- d. Draw the forward characteristics of an SCR with suitable labeling. Describe the characteristics curves. (04 Marks)

PART - B

- 5 a. Choose the correct answers for the following : (04 Marks)
- For a 2-stage amplifier with gain A_{V1} and A_{V2} for Stage-1 and Stage-2, the overall gain A_V is

A) $A_{V1} \times A_{V2}$	B) $A_{V1} + A_{V2}$
C) $A_{V1} - A_{V2}$	D) A_{V1}/A_{V2}
 - A oscillator requires input as

A) DC input	B) No input
C) AC input	D) Any input
 - Hartley and Colpitts oscillator use _____ circuit to generate oscillations

A) Bucket	B) Tap
C) Drum	D) Tank
 - The frequency of oscillation for a colpitts oscillator is given by $1/(2\pi\sqrt{LC})$ where C is

A) $C_1 C_2$	B) $C_1 + C_2$
C) $\frac{C_1 C_2}{C_1 + C_2}$	D) $\frac{C_1 + C_2}{C_1 C_2}$
- b. Draw the circuit diagram of a single stage common emitter RC coupled amplifier and explain various component in the circuit, mentioning the input and output waveforms. (08 Marks)
- c. Find the values of L and C for a colpitts oscillator whose frequency of oscillation is 40KHz. Assume $L = 10\text{mH}$, $C_1 = C_2$. Find C_1 and C_2 . (04 Marks)
- d. State Barkhasen criteria used for sustained Oscillations and mention any two reasons for using -ve feedback. (04 Marks)
- 6 a. Choose the correct answers for the following : (04 Marks)
- An Op-Amp has _____ input terminals

A) One	B) Two
C) Three	D) Four
 - An ideal Op-Amp has input resistance and output resistance as

A) ∞ and 0	B) 0 and ∞
C) 0 and 0	D) ∞ and ∞
 - Deflection system in a CR_0 consists of _____

A) Horizontal	B) Vertical
C) Diagonal	D) horizontal and Vertical
 - In an Op-Amp inverting amplifier $R_l = 1\text{k}\Omega$, $R_f = 10\text{k}\Omega$. The output voltage is _____ if the input voltage is 2V

A) -10V	B) 12V
C) -20V	D) 8V.
- b. Design an inverting adder circuit using Op-Amp to obtain an output voltage given by $V_0 = 2[0.1V_1 + 0.5V_2 + 2.0V_3]$ where V_1, V_2, V_3 are the input voltages. Assume $R_f = 10\text{k}\Omega$. (06 Marks)
- c. With a neat diagram explain how an Op-Amp can be used as a differentiator. (06 Marks)
- d. List out any Four ideal characteristics of Op-Amp. (04 Marks)

- 7 a. Choose the correct answers for the following : (04 Marks)
- In a superheterodyne receiver the output of the mixer is always _____
 A) 455 KHz
 B) 1055 KHz
 C) 955 KHz
 D) 544 KHz
 - 2's complement of 10101 is
 A) 00011
 B) 01010
 C) 01011
 D) 10100
 - $(001001101)_2 = (\quad)_{16}$
 A) $(113)_{16}$
 B) $(261)_{16}$
 C) $(4D0)_{16}$
 D) $(04D)_{16}$
 - The maximum power in an AM system is _____
 A) P_C
 B) $1.5P_C$
 C) $0.5P_C$
 D) $0.99P_C$
- b. Draw the block diagram of a superheterodyne AM receiver. Explain the function of each block mentioning the waveforms at the outputs of each block. (08 Marks)
- c. Convert $(110101)_2 = (\quad)_{10} = (\quad)_{16} = (\quad)_8 = (\quad)_{BCD}$. (04 Marks)
- d. Simplify the following expression and implement using N and gates only : (04 Marks)
 $F = ZY + \bar{Z} + XYZ$.
- 8 a. Choose the correct answers for the following : (04 Marks)
- When Demorgan's theorem applied to $\overline{A \cdot B}$, we get _____
 A) $A \cdot B$
 B) $\bar{A} + \bar{B}$
 C) A
 D) B
 - $Y = AB + \bar{A}\bar{B}$ is a Boolean expression for _____ gate
 A) OR
 B) NOR
 C) E XOR
 D) E XNOR
 - Universal gates are
 A) AND, NAND
 B) OR, NOR
 C) NOR, NAND
 D) AND, OR
 - $A + \bar{A}B =$
 A) $A + B$
 B) B
 C) A
 D) $\bar{A}B$
- b. With a neat diagram, explain the working principle of a parallel binary adder. Give a numerical example. (08 Marks)
- c. Realize $Y = \bar{A}B + A\bar{B}$ using NAND gates only after simplification. (04 Marks)
- d. Realize $Y = \bar{A}B + A\bar{B}$ using NOR gates only after simplification. (04 Marks)
