

CBCS Scheme

USN

--	--	--	--	--	--	--	--

15ELE15/25

First/Second Semester B.E. Degree Examination, Dec.2017/Jan.2018 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. State and explain Kirchoff's law. (05 Marks)
 b. Refer Fig Q1(b). Find I_1 , I_2 and I_3 . (07 Marks)

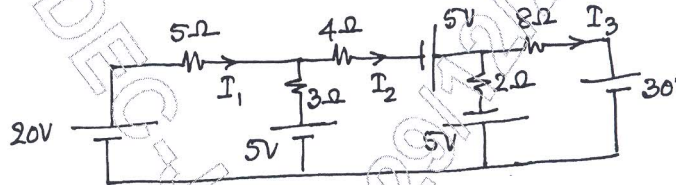


Fig. Q1(b)

- c. Coil A of 230 turns and coil B of 240 turns share a magnetic circuit of mean length 0.8m and uniform cross section area 115cm^2 . Relative permeability of the core material is 1350. Find the self inductances of the coils. Find the average emf induced in coil A when, in coil B, the current changes from 2A to 6.5A in 0.03s. Assume $k = 1.0$ between the coils. (04 Marks)

OR

- 2 a. Define 'Self Inductance' of a coil. Derive an expression for the self inductance of a coil in terms of its geometry and material properties. (05 Marks)
 b. Refer Fig Q2(b) find I_1 , I_2 and the power in the 6Ω resistor. (07 Marks)

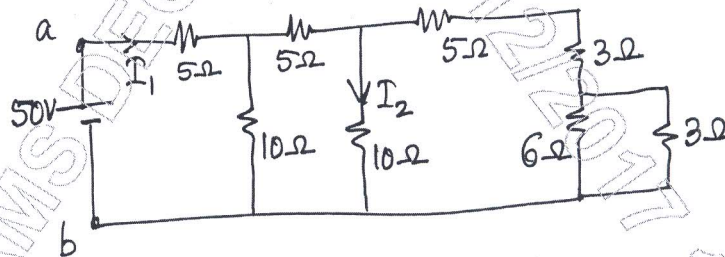


Fig. Q2(b)

- c. Coil A of 600 turns and coil B of 500 turns have $k = 0.2$. A current of 8A in coil A produces 40mWb flux in it. Find : i) Inductance of coil A with coil B open circuited ; ii) the flux linking coil B ; iii) the emf induced in coil B if the flux linking it falls to zero from its full value in 2ms ; and iv) mutual inductance between the coils. (04 Marks)

Module-2

- 3 a. Deduce an expression for the armature torque, T_a , developed in a dc motor and hence show that $T_a \propto \phi I_a$. (02 Marks)
 b. A 100V short shunt dc generator supplies 200 lamps of 55W at 110V rating. $R_a = 0.06\Omega$; $R_{se} = 0.04\Omega$; and $R_{sh} = 25\Omega$. Sketch the circuit diagram and find the emf generated. (07 Marks)
 c. With a neat sketch, explain the working of a 1ϕ energy meter. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, $42+8=50$, will be treated as malpractice.

OR

- 4 a. "A dc series motor should never be run on light or no load". Justify. (03 Marks)
 b. A shunt dc generator delivers 65kW at 250V and 500rpm. $R_a = 0.015\Omega$ and $R_{sh} = 85\Omega$. Find its speed when running as a motor taking 40kW from 240V supply. BCD = 1V/Brush. Sketch relevant circuit diagrams. (07 Marks)
 c. With a neat schematic, describe the construction and working of a dynamometer type wattmeter. (06 Marks)

Module-3

- 5 a. Show that a pure inductor is lossless. (03 Marks)
 b. Refer Fig. Q5 (b). Find the real power, reactive power and the apparent power supplied.

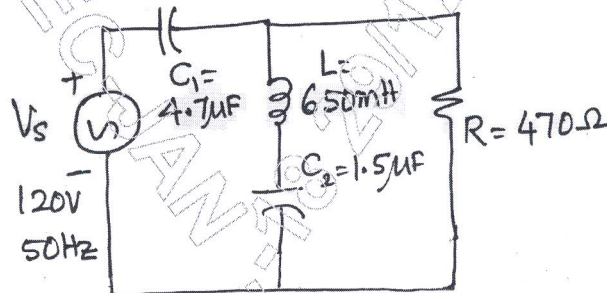


Fig. Q5(b)

(06 Marks)

- c. With a neat circuit diagram and truth table, explain the working of a 3-way control of a device. (07 Marks)

OR

- 6 a. Show that an R-C series circuit takes a leading current. Sketch a phasor diagram indicating the supply emf, the current and the two drops. (07 Marks)
 b. A resonant series circuit with $R = 5\Omega$, $L = 1\text{mH}$ and $C = 0.001\mu\text{F}$ is connected to a 100V supply. Find :
 i) the drop across L ; and
 ii) drop across C. Take the supply as the reference phasor. (05 Marks)
 c. For a fuse, define i) Rated current, ii) Fusing current ; and iii) Fusing factor. Why is the fusing factor greater than unity? (04 Marks)

Module-4

- 7 a. Sketch a 4-wire STAR supply and identify the phase and line voltages. With balanced supply taking $E_R = E_P \angle 0^\circ$, obtain the relationship between the phase and line voltages. Hence, sketch a phasor diagram indicating all phase and line voltages. (08 Marks)
 b. 2 wattmeters connected to measures 3 ϕ power of a balanced Δ load read 2.5 kW and 0.5kW. Find the load pf if i) both readings are positive; and ii) the latter reading is obtained after reversing the connections of the potential coil. (04 Marks)
 c. In a 3 ϕ alternator, why is it advantageous to have the armature on the stator and the excitation on the rotor? (04 Marks)

OR

- 8 a. With a neat circuit diagram, show how 3 ϕ power can be measured using two Wattmeters. State the NECESSARY CONDITION clearly. (07 Marks)
- b. A balanced Δ load of $(8+j6) \Omega$ /phase is connected to a 400V supply. Find i) the phase current ii) the line current. If the same impedances are connected in STAR, what is the reactive power consumed and at what pf? (04 Marks)
- c. A 4-pole, 3 ϕ alternator driven at 1800rpm has 42 slots with 4 conductors/slot. Average flux/pole is 0.36 Wb, sinusoidally distributed. $K_p = 0.956$ and $K_d = 0.952$. Find the line voltage on no-load if connected in i) Δ ; and ii) STAR. (05 Marks)

Module-5

- 9 a. Starting from expression for the efficiency of a transformer derive the condition for maximum efficiency and the expression for maximum efficiency. (05 Marks)
- b. A 135 kVA, 1 ϕ transformer has primary of 2kV, 50Hz. Primary and secondary number of turns are 162 and 48 respectively. Neglecting losses, find i) no-load secondary emf ; ii) full load primary and secondary currents; and iii) maximum core flux. (04 Marks)
- c. With a neat sketch, explain the working of a STAR - Δ starter, for a 3 ϕ induction motor. Show that the starting inrush current is reduced by 66.7%. (07 Marks)

OR

- 10 a. "A 3 ϕ induction motor can never run at N_s ". Justify. (04 Marks)
- b. A single phase transformer has a maximum efficiency of 98% at 75% load, upf. The copper loss at maximum efficiency is 314W. Find its efficiency at 50% load, 0.9 pf. (04 Marks)
- c. A 6-pole, 3 ϕ alternator running at 1200rpm feeds a 4-pole, 3 ϕ induction motor having slips of 3% at full load and 2.5% at half load. The rotor induced emf/phase at stand still is 160V. At full load and half load, find each of the following: i) the motor speed ; ii) frequency of the rotor induced emf and (iii) the rotor induced emf/phase. (08 Marks)

* * * * *