

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, Dec.2018/Jan.2019
Linear IC's and Application

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer FIVE full questions, selecting atleast TWO questions from each part.**
2. Use of standard resistance/capacitance chart permitted.

PART – A

- 1
 - a. Sketch the circuit of high input impedance capacitor coupled voltage follower. Develop the equation for input impedance list design steps. (08 Marks)
 - b. A capacitor coupled non-inverting amplifier is to be designed with $A_v = 120$ and $V_L = 4.2V$. Load resistance is $8.2K\Omega$ and lower cut off frequency is 60Hz. Design the circuit using 715 op-amp [Assume $I_{B(max)} = 1.5\mu A$] (07 Marks)
 - c. What is setting upper cut-off frequency? Why is it necessary explain how it can be achieved for an inverting amplifier. (05 Marks)
- 2
 - a. Explain : i) phase lag ii) phase lead compensation methods for op-amp circuits with lower closed loop gains. (08 Marks)
 - b. Explain effect of slew rate on :
 - i) Band-width and output amplitude
 - ii) Output pulse rise time and amplitude. (08 Marks)
 - c. A 741 op-amp is used as an inverting amplifier with a gain of 50. The voltage gain versus frequency plot is flat upto 20KHz. What is peak to peak sine wave input that can be amplified without any distortion. Assume $SR = 0.5V/\mu sec$. (04 Marks)
- 3
 - a. Draw on high input impedance full-wave precision rectifier. Show various waveforms. Write down appropriate equations to show that full wave rectification is achieved. (09 Marks)
 - b. Explain with a neat circuit working of a precision clamping circuit. Show how output can be biased at any desired level. (06 Marks)
 - c. With a neat circuit, explain working of a sample and hold circuit. (05 Marks)
- 4
 - a. With a neat circuit, explain working of an inverting Schmitt trigger. Draw waveforms and transfer char. Give equations for designing. (07 Marks)
 - b. An inverting Schmitt trigger with $UTP = 0$ and $V_H = 0.2V$ converts a 1KHz sine wave of amplitude 4V peak to peak to a rectangular wave. Determine T_{ON} and T_{off} . (06 Marks)
 - c. Draw a monostable multivibrator circuit and draw various waveforms at different points of the circuit write an expression for pulse width of the output. (07 Marks)

PART – B

- 5
 - a. Compare an RC phase shift oscillator with Wien bridge oscillator. (06 Marks)
 - b. Draw a triangular/rectangular wave generator circuit. Explain how frequency and duty cycle control is achieved. (09 Marks)
 - c. Design a RC phase shift oscillator, to give a maximum output of $\pm 3V$ at a frequency of 6KHz. Include distortion minimization adjustment. (05 Marks)

- 6 a. Compare a wide band filter with a narrow band filter. (06 Marks)
b. Explain a second order high pass filter. List out design steps show the frequency response. (08 Marks)
c. Using 741 op-amp design a bandpass filter with centre frequency at 1KHz and passband to be approximately $\pm 33\text{Hz}$ on each of 1KHz. (06 Marks)
- 7 a. What is a power amplifier? List features of LM380 audio amplifier. (06 Marks)
b. List advantages of switched capacitor filter and explain how a switched capacitor can simulate a resistor. (07 Marks)
c. Explain phase locked loop with block diagram. define the terms :
i) lock range ii) capture range. (07 Marks)
- 8 a. Define terms :
i) Line regulation
ii) Load regulation
iii) Ripple rejection, applied to voltage regulation. (06 Marks)
b. With a neat circuit explain operation of adjustable output regulator. (06 Marks)
c. A positive voltage regulator is to produce an output voltage of 2V. Design the circuit using LM217 IC voltage regulator. (08 Marks)
