

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC34

## Third Semester B.E. Degree Examination, June/July 2018 Network Analysis

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Determine the equivalent resistance across XY shown in Fig.Q1(a) (05 Marks)

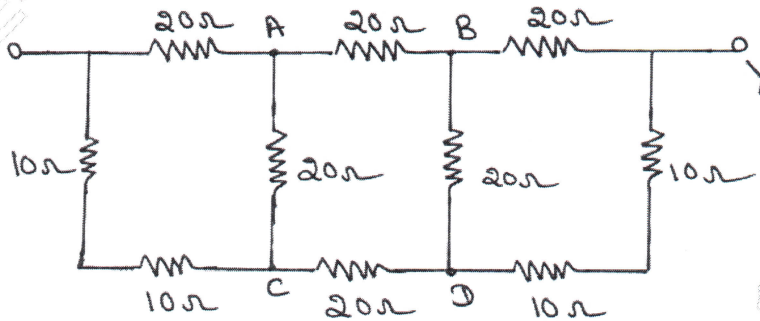


Fig.Q1(a)

- b. Calculate the voltage across the  $6\Omega$  resistor using source shifting and transformation technique shown in Fig.Q1(b). (05 Marks)

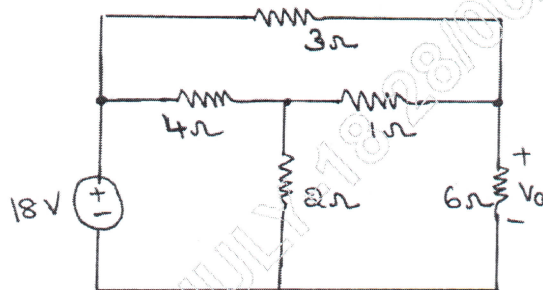


Fig.Q1(b)

- c. Determine the power supplied by the dependent source of Fig.Q1(c) shown. (06 Marks)

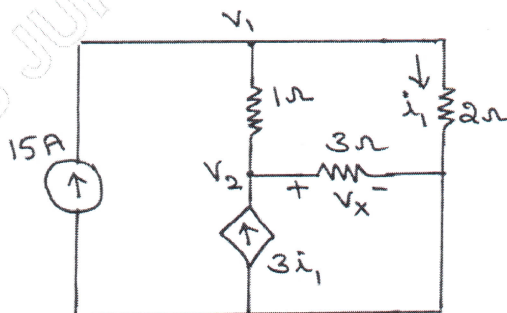


Fig.Q1(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 2 a. Using Mesh current analysis, find the current through  $24\Omega$  in the circuit shown in Fig.Q2(a). (08 Marks)

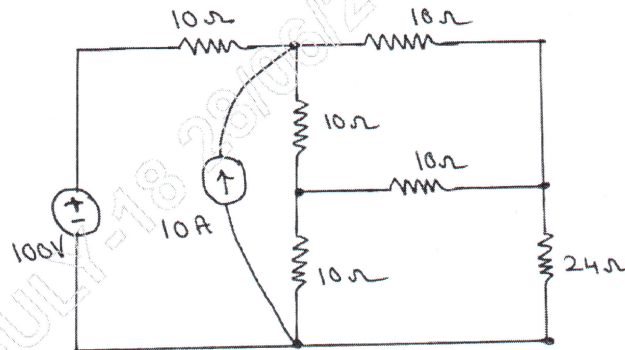


Fig.Q2(a)

- b. For the network of Fig.Q2(b) determine the node voltage by nodal analysis. (08 Marks)

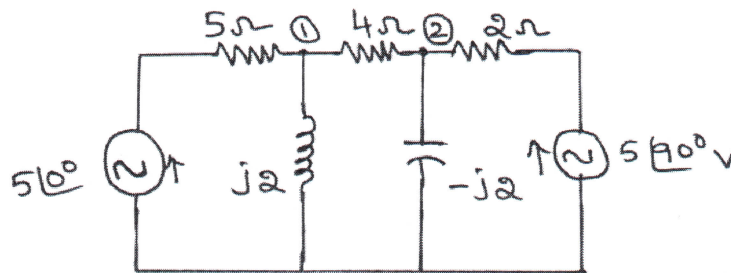


Fig.Q2(b)

**Module-2**

- 3 a. State superposition theorem. In the circuit of Fig.Q3(a), use the superposition principle to determine the value of  $i_x$ . (08 Marks)

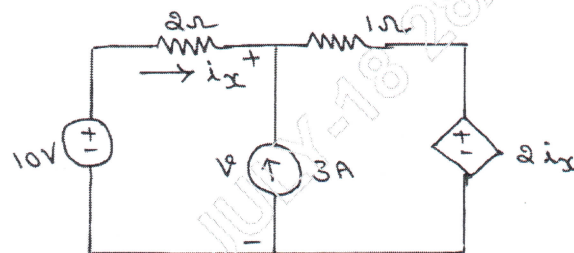


Fig.Q3(a)

- b. Obtain the Thevenin and Norton equivalent circuits at terminals AB for the network shown in Fig.Q3(b). (08 Marks)

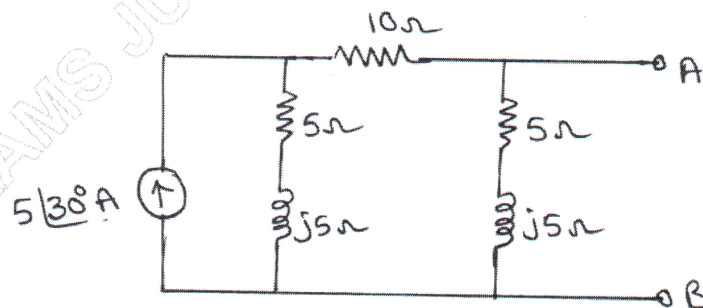


Fig.Q3(b)

OR

- 4 a. Using Millman's theorem, find  $I_L$  through  $R_L$  for the network shown in Fig.Q4(a). (06 Marks)

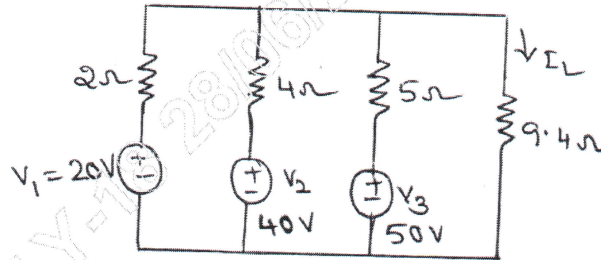


Fig.Q4(a)

- b. Verify reciprocity theorem for the circuit shown in Fig.Q4(b). (06 Marks)

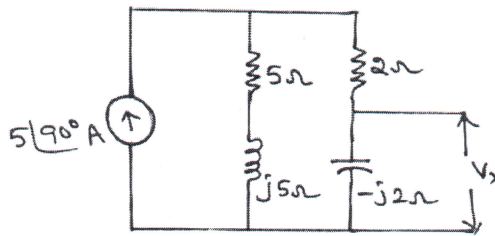


Fig.Q4(b)

- c. State and explain maximum power transfer theorem. (04 Marks)

**Module-3**

- 5 a. In the circuit shown in Fig.Q5(a), the switch K is changed from position 1 to position 2 at  $t = 0$ , the steady state has been reached before switching. Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{di^2}{dt^2}$  at  $t = 0$ . (08 Marks)

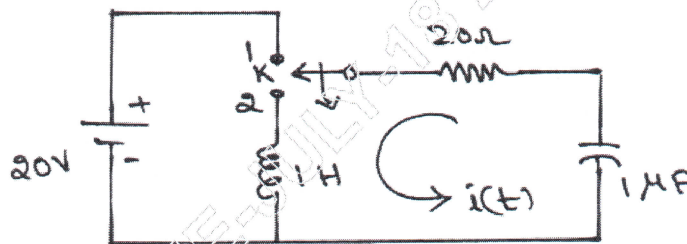


Fig.Q5(a)

- b. The switch in the network shown in Fig.Q5(b) is closed at  $t = 0$ . Determine the voltage across the capacitor. Use Laplace transform. (08 Marks)

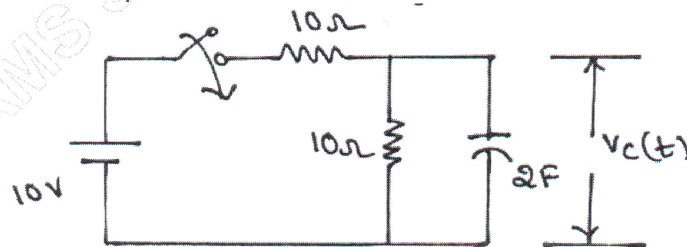


Fig.Q5(b)

OR

- 6 a. In the network shown in Fig.6(a), the switch K is opened at  $t = 0$ . At  $t = 0^+$ , solve for the values of  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  if  $I = 2A$ ,  $R = 200\Omega$  and  $L = 1H$ . (08 Marks)

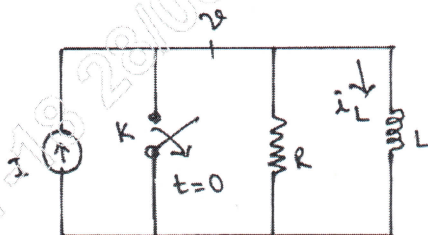


Fig.Q6(a)

- b. Determine the Laplace transform of the periodic saw tooth waveform of Fig.Q6(b). Use gate function. (08 Marks)

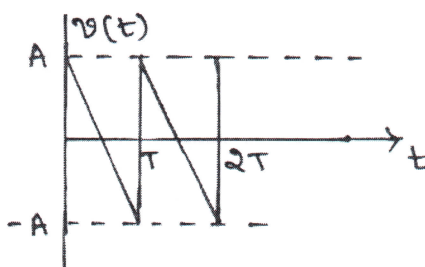


Fig.Q6(b)

Module-4

- 7 a. Derive for a resonant circuit, the resonant frequency  $f_0 = \sqrt{f_1 f_2}$ , where  $f_1$  and  $f_2$  are the two half power frequencies. (07 Marks)  
 b. Find the value of L for which the circuit shown in Fig.Q7(b) is resonant at a frequency of  $\omega = 5000$  rad/sec. (06 Marks)

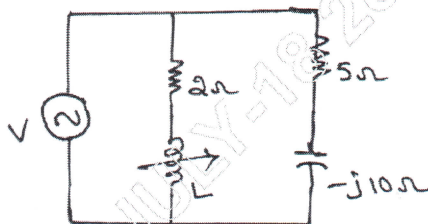


Fig.Q7(b)

- A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01H$  and  $c = 0.01\mu F$  and it is connected across 10mV supply. Calculate : i)  $f_0$  ii)  $Q_0$  iii) B.w. (03 Marks)

OR

- 8 a. A series RLC circuit has a resistance of  $10\Omega$ , an inductance of  $0.3H$  and a capacitance of  $100\mu F$ . The applied voltage is  $230V$ . Find : i) Resonant frequency ii) Quality factor iii) Lower and upper cut off frequencies iv) Bandwidth v) Current at resonance vi) currents at  $f_1$  and  $f_2$  vii) voltage across inductance at resonance. (08 Marks)  
 b. Derive an expression for the resonant frequency of a parallel resonant circuit. Also show that the circuit is resonant at all frequencies if  $R_L = R_C = \sqrt{\frac{L}{C}}$  where  $R_L$  = Resistance in the inductor branch,  $R_C$  = resistance in the capacitor branch. (08 Marks)

**Module-5**

- 9 a. Find Y parameters and Z parameters for the circuit show in Fig.Q9(a).

(08 Marks)

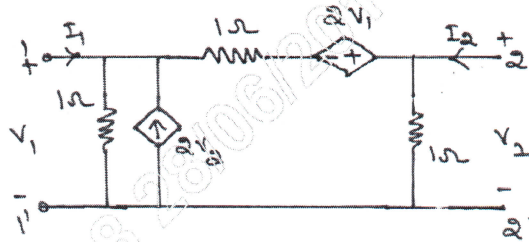


Fig.Q9(a)

- b. Express ABCD parameters interms of Y-parameters and h-parameters.

(08 Marks)

**OR**

- 10 a. Determine z parameters for the network shown in Fig.Q10(a).

(08 Marks)

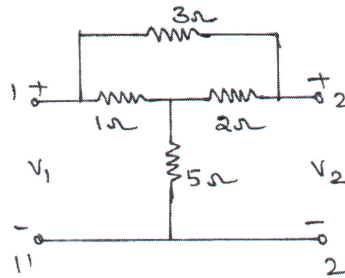


Fig.Q10(a)

- b. Express h-parameters interms of Y-parameters.

(08 Marks)

\*\*\*\*\*