

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC34

## Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Network Analysis

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Reduce the network shown in Fig.Q1(a) to a single voltage source in series with a resistance using source shift and source transformations. (08 Marks)

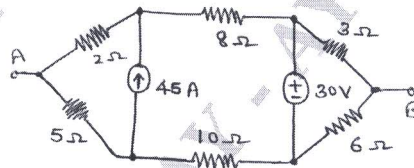


Fig.Q1(a)

- b. Using star/delta transformation, determine the resistance between M and N for the network shown in Fig.Q1(b). (08 Marks)

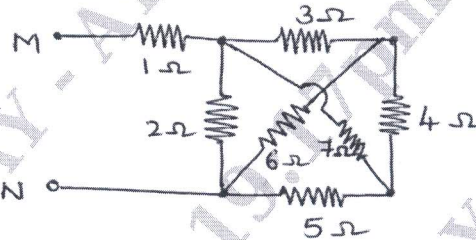


Fig.Q1(b)

OR

- 2 a. Find the power delivered by the dependent voltage source in the circuit shown in Fig.Q2(a) by Mesh current method. (06 Marks)

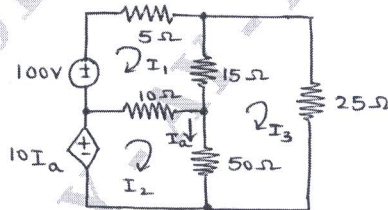


Fig.Q2(a)

- b. Define super Mesh and super node. (02 Marks)  
 c. Use the node-voltage method to find the power developed by the 20V source in the circuit shown in Fig.Q2(c). (08 Marks)

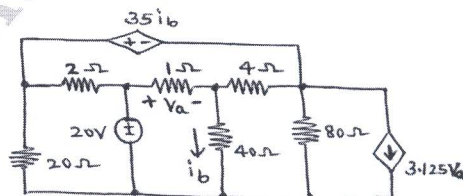


Fig.Q2(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. Use superposition theorem to find  $V_x$  in the circuit shown in Fig.Q3(a). (08 Marks)

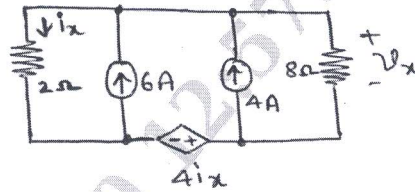


Fig.Q3(a)

- b. State and prove reciprocity theorem. (08 Marks)

OR

- 4 a. State and prove Thevenin's theorem. (06 Marks)  
 b. Find the Norton's equivalent circuit across AB terminals for the network shown in Fig.Q4(b) and hence determine current through  $5\Omega$  resistor. (06 Marks)

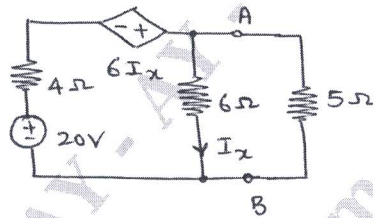


Fig.Q4(b)

- c. Find the value of  $Z_L$  for which Maximum Power transfer occurs in the circuit shown in Fig.Q4(c). (04 Marks)

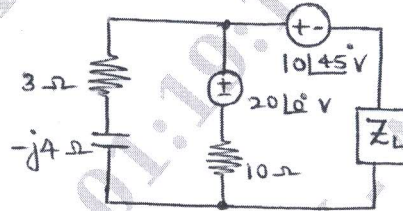


Fig.Q4(c)

**Module-3**

- 5 a. In the network shown in Fig.Q5(a), the switch k is closed at  $t = 0$ . Find the values of  $i_1$ ,  $i_2$  and  $\frac{di_1}{dt}$  and  $\frac{d^2i_2}{dt^2}$  at  $t = 0$ . (08 Marks)

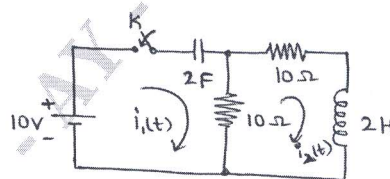


Fig.Q5(a)

- b. In the circuit shown in Fig.Q5(b), the capacitor  $C_1$  is charged to a voltage  $V_0$  at  $t = 0$ , the switch is closed. Solve for the charge as a function of time. (08 Marks)

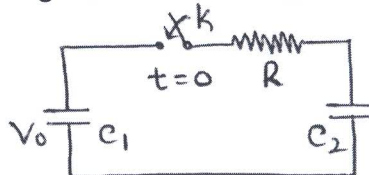


Fig.Q5(b)

OR

- 6 a. State and prove the following : i) Initial value theorem ii) Final value theorem. (08 Marks)  
 b. For the waveform shown in Fig.Q6(b), the equation of the waveforms is  $\sin(t)$  from  $0$  to  $\pi$ , and  $-\sin(t)$  from  $\pi$  to  $2\pi$ , show that the Laplace transform of this waveform is :

$$F(s) = \frac{1}{s^2 + 1} \cot h\left(\frac{\pi s}{2}\right).$$

(08 Marks)

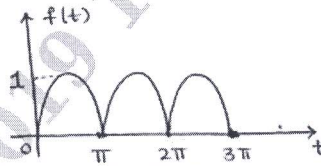


Fig.Q6(b)

**Module-4**

- 7 a. Define the following terms :  
 i) Resonance ii) Bandwidth. (02 Marks)  
 b. Prove that  $f_0 = \sqrt{f_1 f_2}$  where  $f_1$  and  $f_2$  are the two half power frequencies of a resonant circuits. (06 Marks)  
 c. A series RLC circuit has  $R = 2\Omega$ ,  $L = 2$  mH and  $C = 10\mu\text{f}$  calculate Q-factor, bandwidth, Resonant frequency and half power frequencies  $f_1$  and  $f_2$ . (08 Marks)

OR

- 8 a. Show that a two-branch parallel circuit is resonant at all frequencies if  $R_L = R_C = \sqrt{\frac{L}{C}}$ . (08 Marks)  
 b. Find the values of L for which the circuit given in Fig.Q8(b) resonates at  $\omega = 5000$  r/sec. (08 Marks)

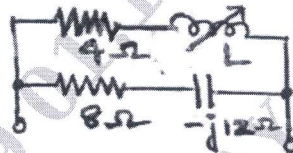


Fig.Q8(b)

**Module-5**

- 9 a. Express Z – parameters interms of Y-parameters. (08 Marks)  
 b. Obtain ABCD parameters interms of impedance parameters (Z) and hence show that  $AD-BC = 1$ . (08 Marks)

OR

- 10 a. For the network shown in Fig.Q10(a), contains an voltage controlled source and current controlled source, for the elemental values specified, determine Z and Y parameters. (08 Marks)

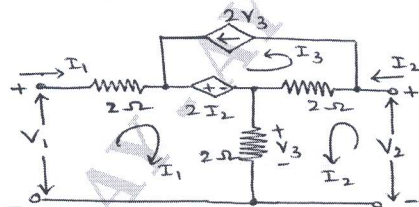


Fig.Q10(a)

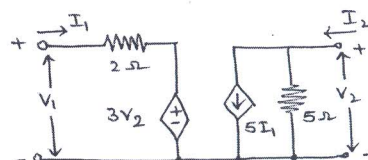


Fig.Q10(b)

- b. Determine transmission parameters for the network shown in Fig.Q10(b). (08 Marks)

\*\*\*\*\*