

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15MT63

**Sixth Semester B.E. Degree Examination, June/July 2018**

**Power Electronics**

Time: 3 hrs.

Max. Marks: 80

*Note: Answer any FIVE full questions, choosing one full question from each module.*

**Module-1**

- 1 a. Define power electronics. List the applications of power electronics. (08 Marks)
- b. With necessary waveforms, explain the switching characteristics of power MOSFET. (08 Marks)

OR

- 2 a. Write the symbol and control characteristics of the following devices:
  - i) IGBT    ii) SCR    iii) GTO. (06 Marks)
- b. Compare MOSFET and IGBT. (06 Marks)
- c. What are the different types of power electronic converters? (04 Marks)

**Module-2**

- 3 a. Explain the two transistor model of SCR and derive the expression
 
$$I_A = \frac{\alpha_2 I_G + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$
(08 Marks)
- b. A thyristor circuit is shown in Fig.Q.3(b), the SCR has a latching current of 50mA, and is fired by a pulse of length 50µsec. Show that without resistance R, the thyristor will fail to remain  $I_N$ , when the firing pulse ends. And then find the maximum value of R to ensure firing. (08 Marks)

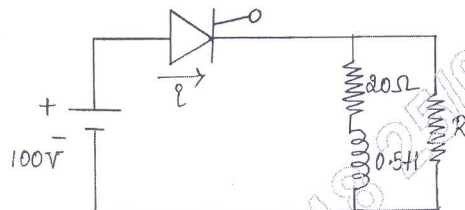


Fig.Q.3(b)

OR

- 4 a. Define commutation. Compare natural and forced commutation. (08 Marks)
- b. In the parallel capacitor turn off-circuit shown in Fig.Q.4(b), main SCR  $T_1$  is to be reversed biased for atleast 40µs for proper commutation and holding current of auxiliary SCR  $T_2$  is 2mA. Find R and C. (08 Marks)

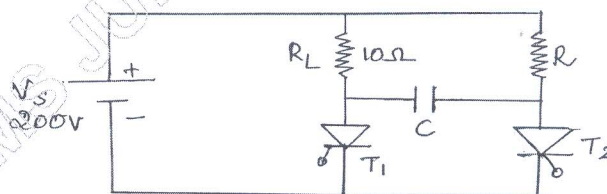


Fig.Q.4(b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

**Module-3**

- 5 a. With neat circuit diagram and waveforms, explain operation of single phase AC voltage controller using ON-OFF control. Derive an expression for RMS value of output voltage. (08 Marks)
- b. A single phase half wave AC voltage controller is shown in Fig.Q.5(b) feeds power to a resistive load of  $6\Omega$  from 230V, 50Hz source. The firing angle of SCR is  $\alpha = \pi/2$ . Calculate:
- RMS value of output voltage.
  - Input power factor.
  - Average input current.
  - Average output voltage.

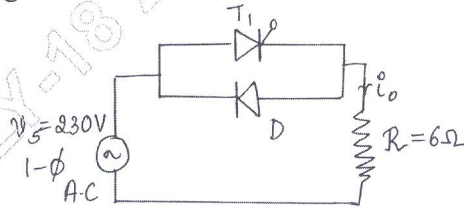


Fig.Q.5(b)

OR

- 6 a. Explain the operation of single phase semi converter with circuit and waveforms. Derive an expression for average value of output voltage (Assume R-L load). (08 Marks)
- b. What are the advantages of circulating current-mode dual converter? (04 Marks)
- c. Mention the applications of AC voltage controller. (04 Marks)

**Module-4**

- 7 a. Explain the principle of operation of a step-up chopper. (08 Marks)
- b. A D.C. chopper has an input voltage of 200V and a load resistance of  $8\Omega$ . The voltage drop across the thyristor is 2V and chopper frequency is 800Hz. The duty cycle is 0.4. Find:
- Average output voltage
  - RMS output voltage
  - Chopper efficiency.

OR

- 8 a. Derive an expression for peak-peak ripple in the load current, in case of a step down chopper with R-L load. (10 Marks)
- b. With neat diagram, explain four quadrant operation of a chopper. (06 Marks)

**Module-5**

- 9 a. Explain the principle of single phase half bridge inverter with relevant circuit diagram and waveforms. (10 Marks)
- b. Write a note on performance parameters of a inverter:
- Harmonic factor of nth harmonic.
  - Total harmonic distortion (THD).
  - Distortion factor (DF).

OR

- 10 a. Compare voltage source inverter and current source inverter. (06 Marks)
- b. With neat circuit diagram, explain the operation of a three phase transistorized inverter in  $180^\circ$  conduction mode with star connected R-load. (10 Marks)

\*\*\*\*\*