

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

16EPS/EPE41

Fourth Semester M.Tech. Degree Examination, June/July 2018

## HVDC Power Transmission

Time: 3 hrs.

Max. Marks: 80

*Note: Answer any FIVE full questions, choosing one full question from each module.*

### Module-1

- 1 a. Explain the advantages of HVDC transmission over HVAC transmission. (06 Marks)
- b. Draw a neat sketch of organization of HVDC systems. Give the function of its basic components. (06 Marks)
- c. Write short notes on HVDC system reliability. (04 Marks)

OR

- 2 a. Develop the equivalent circuit of a 3-phase converter working as rectifier with an overlap angle  $\mu$  and delay angle  $\alpha$ . Hence, show that the equivalent resistance of the converter is  $\frac{3W_L C}{\pi}$ . (08 Marks)
- b. Calculate the secondary line voltage of a transformer for three phase bridge rectifier to provide a DC voltage of 120 KV. Assume  $\alpha = 30^\circ$ ,  $\mu = 15^\circ$ . What is the effective reactance, if the rectifier gives 800 A of DC output current. (04 Marks)
- c. Draw the schematic diagram of a 12 pulse converter. What are the different modes of operation of it? (04 Marks)

### Module-2

- 3 a. What are the various sources for generation of harmonics in HVDC systems? Mention the effects caused due to the presence of harmonics. (04 Marks)
- b. Draw the wave shape of currents of the primary side of star-star and star-delta 3-phase 12 pulse converter transformer, and obtain an expression for current on the primary side in terms of harmonics. (08 Marks)
- c. What are the different types of filters used on the AC side of an HVDC system? Explain the design of active power filter. (04 Marks)

OR

- 4 a. With necessary diagrams explain the individual phase control and equidistant pulse control schemes used for firing angle control of converter. (08 Marks)
- b. Write a short note on commutation failure in HVDC converter. (02 Marks)
- c. With the help of block diagram and characteristics explain the principle of conventional HVDC control. (06 Marks)

### Module-3

- 5 a. State and explain the HVDC system control functions using hierarchical control scheme. (08 Marks)
- b. Compare various types of reactive power compensators with respect to response time, temporary over voltage and capacity. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Define short circuit ratio and effective short circuit ratio of an HVDC system. (04 Marks)  
b. With neat diagram explain the interaction between HVDC and HVAC system. (06 Marks)  
c. Explain the interaction between HVDC system and FACTS devices. (06 Marks)

**Module-4**

- 7 a. With sketches explain the methods of various gate triggering circuits in HVDC converter. (06 Marks)  
b. What are the design constraints of HVDC converter transformer? (04 Marks)  
c. Explain any one method of cooling HVDC thyristor valves. (06 Marks)

OR

- 8 a. Write short notes on bipolar HVDC overhead line. (04 Marks)  
b. Mention the types of cable used in HVDC system. Explain the design of any one cable. (08 Marks)  
c. What are the noise sources of a HVDC station? (04 Marks)

**Module-5**

- 9 a. Give the principles of various AC side apparatus protection in HVDC system from fault. (06 Marks)  
b. Explain the concept of protection by control actions in an HVDC system with a neat sketch. (06 Marks)  
c. With the help of block diagram explain fault analysis according to a valve fault in HVDC converter. (04 Marks)

OR

- 10 a. With neat sketches explain the operation of different types of Multi Terminal (MTDC) systems. (08 Marks)  
b. With the diagram, write the principle of operation of voltage source converter of HVDC systems in offshore application. (06 Marks)  
c. What are the advantages of 800 KV HVDC systems? (02 Marks)

\* \* \* \* \*