

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

16/17EPE/EPS24

## Second Semester M.Tech. Degree Examination, June/July 2018 FACTS Controllers

Time: 3 hrs.

Max. Marks: 80

**Note:** Answer FIVE full questions, choosing one full question from each module.

### Module-1

- 1 a. Explain conventional control mechanism of Automatic generation control and excitation control with block diagram. (08 Marks)
- b. Obtain the midpoint voltage conditions of a symmetrical line as a function of the power flow point. (08 Marks)

OR

- 2 a. Explain synchronous condensers and its main applications. (08 Marks)
- b. Explain operating characteristics of a Thyristor controlled Reactors without a voltage control. (08 Marks)

### Module-2

- 3 a. Explain the fixed capacitor Thyristor controlled Reactor (FC-TCR) configuration and operating characteristics without the step down transformation. (08 Marks)
- b. Explain mechanically switched capacitor Thyristor controlled Reactor (MSC – TCR) with different configuration. (08 Marks)

OR

- 4 a. Write the comparison of different Reactive compensators with respect to features. (Any eight). (08 Marks)
- b. An SVC connected to a 735KV system has reactive power range of 350MVAR production to 100MVA absorption. The droop is set to 4%. The system short circuit level is specified as follows :
- The maximum short circuit current : 50k.A
  - The minimum short circuit current under normal operating conditions : 5 KA
  - The minimum short circuit current during system restoration after loss of a transmission line : 500A form these specification.
- Determine the per-unit regulator gain that ensured stable operation from 5KA to 50KA system short circuit current.
  - Show the change of voltage control response for the system variation and regulator setting in item 1 of the sub list. (08 Marks)

### Module-3

- 5 a. Explain any two methods for improving the voltage controller response. (08 Marks)
- b. Explain influence of the 2<sup>nd</sup> harmonic voltage on the TCR with waveforms. (08 Marks)

OR

- 6 a. Explain the effect of the shunt reactor mode on the SVC voltage regulator. (08 Marks)
- b. Explain with waveform 3<sup>rd</sup> harmonic distortion. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-4**

- 7 a. Explain increase in steady state power transfer capacity. (08 Marks)  
b. Explain of voltage instability with respect to principles of SVC control A case study. (08 Marks)

**OR**

- 8 a. Write the advantages of thyristor controlled series capacitors (TCSC). (08 Marks)  
b. Explain the modes of TCSC operation. (08 Marks)

**Module-5**

- 9 a. Explain a TCSC constant current (CC) controller model. (08 Marks)  
b. Explain improvement of the system stability limit. (08 Marks)

**OR**

- 10 a. Explain the principle of operation of the STATCOM. (08 Marks)  
b. Explain the application of SSSC in power flow control by taking a case study. (08 Marks)

\* \* \* \* \*