

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15/25

First/Second Semester B.E. Degree Examination, Dec.2017/Jan.2018

Basic Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- Explain the V-I characteristics of p-n junction diode. (05 Marks)
 - The input voltage applied to the primary of a 4:1 step down transformer of a full wave centre tap rectifier is 230 V, 50 Hz is the load resistance is 600Ω and forward resistance is 20Ω . Determine the following for circuit shown in Fig.Q1(b).
 - dc power output
 - Rectification efficiency
 - PIV

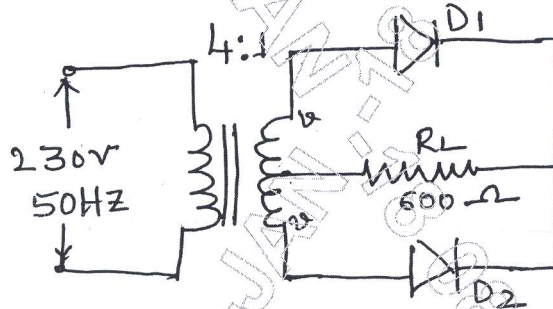


Fig.Q1(b)

- Explain CB configuration of BJT with characteristics. (06 Marks)

(05 Marks)

OR

- Derive an expression for ripple factor and output dc voltage of a full wave rectifier. (06 Marks)
 - Explain how a zener diode can be used as a voltage regulator. (05 Marks)
 - Obtain the relationship between α and β . Calculate the value of I_C , I_E for a transistor that has $\alpha = 0.98$ and $I_B = 100 \mu A$. (05 Marks)

Module-2

- What is DC load line? Explain collector to base biased method with necessary equation. (05 Marks)
 - Define the following terms with respect to op-amp: (i) Slew rate, (ii) CMRR, (iii) PSRR. (05 Marks)
 - Design an op-amp circuit that will produce an output equal to $-(4V_1 + V_2 + 0.1V_3)$. (06 Marks)

OR

- With circuit diagram, explain the operation of voltage divider bias circuit with necessary equations. (06 Marks)
 - Derive the expression of 3-i/p summing amplifier. (05 Marks)
 - Draw the circuit of inverting op-amp. Derive the expression for the voltage gain. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Perform the following:
- Convert $(725.25)_{10} = (?)_{10} = (?)_2$
 - Subtract using 2's complement $(4 - 9)_{10}$
 - $(11010.101)_2 = (?)_8 = (?)_{16}$ (06 Marks)
- b. State and prove Demorgan's theorem. (05 Marks)
- c. Simplify the expression and realize using basic gates $\overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + A\overline{B}\overline{C}$. (05 Marks)

OR

- 6 a. Convert:
- $(172.625)_{10} = (?)_{16} = (?)_2$
 - $(BDCE)_{16} = (?)_2 = (?)_8$
 - $(10111101.0110)_2 = (?)_{10} = (?)_{16}$ (06 Marks)
- b. Simplify and realize the Boolean expression using two inputs NAND gates only $(A + \overline{B} + C)(\overline{A} + B + C)$. (05 Marks)
- c. Realize the full adder circuit for sum and carry using basic gates, explain the same with truth table. (05 Marks)

Module-4

- 7 a. Explain the operation of NAND and NOR latch with symbol, circuit and truth tube. (08 Marks)
- b. With neat block diagram, describe the architecture of 8051 microcontroller. (08 Marks)

OR

- 8 a. What is flip-flop? Explain clocked R-S flip-flop with diagram and truth table. (08 Marks)
- b. Explain the working principle of microcontroller based stepper motor control system. (08 Marks)

Module-5

- 9 a. What are the basic elements of communication system? Explain with neat block diagram. (06 Marks)
- b. Distinguish between Amplitude Modulation (AM) and Frequency Modulation (FM). (04 Marks)
- c. Explain the construction and the principle of operation of LVDT. (06 Marks)

OR

- 10 a. With relevant waveforms, explain amplitude modulation. (06 Marks)
- b. What is a transducer? Mention four important parameters of an electrical transducer. (04 Marks)
- c. Write short notes on:
- Piezo electric transducer
 - Photo electric transducer. (06 Marks)

* * * * *