

# 2002 SCHEME

CS33

USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2019

## Logic Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1 a. Verify the following Boolean manipulations and justify each step with respect to postulate or theorem:
- $abc + ab\bar{c} + a\bar{b}c + \bar{a}bc = ab + ac + bc$  (06 Marks)
  - $(ab + c + d)(\bar{c} + d)(\bar{c} + d + e) = ab\bar{c} + d$  (04 Marks)
- b. Express the following Boolean functions by Maxterm canonical formula without first constructing the Truth-Table.  $f(x, y, z) = x + \bar{x}z(y + z)$  (10 Marks)
- c. Realize 4-bit odd Parity generator using X-OR gates only.
- 2 a. Using K-maps determine all minimal sums and minimal products for the following Boolean functions. In each case indicate essential Prime Implicants. (05 Marks)
- $f(w, x, y, z) = \sum m(0, 1, 6, 7, 8, 14, 15)$
- b. Design a combinational network whose input is a 4-bit binary number and whose output is a 2'S complement of input number. (05 Marks)
- c. For the following Boolean function, determine minimal sums and minimal products using VEM technique, where w, x and y are the map variables and z is map entered variable. (10 Marks)
- $f = \sum m(2, 3, 5, 12, 14) + dc(0, 4, 8, 10, 11)$
- 3 a. Using the Quine-McCluskey method and prime implicant table reductions, determine the minimal sums for the incomplete Boolean function. (10 Marks)
- $f(v, w, x, y, z) = \sum m(4, 5, 9, 11, 12, 14, 15, 27, 30) + dc(1, 17, 25, 26, 31)$
- b. Explain the procedure for loading a K-map using map entered variable technique. Write the map entered variable K-map for the Boolean function. (10 Marks)
- $f(w, x, y, z) = \sum m(2, 9, 10, 11, 13, 14, 15)$
- 4 a. Explain the operation of a two input TTL NAND-gate with totem-pole output with a neat circuit diagram. (08 Marks)
- b. What is a FET? Explain how to construct a resistor with the n-channel, enhancement type MOSFET. (06 Marks)
- c. Explain with the help of a circuit diagram the operation of a two input CMOS nor-gate. (06 Marks)
- 5 a. With a block diagram describe the principle of operation of a carry Look-ahead-adder. (06 Marks)
- b. What is a Programmable LOGIC Array (PLA)? Describe with a logic diagram the principle of operation of a PLA. What are its advantages? (08 Marks)
- c. Implement the following Boolean function using 8:1 multiplexer. (06 Marks)
- $F(A, B, C, D) = \bar{A}\bar{B}\bar{D} + ACD + \bar{B}CD + \bar{A}CD$

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- 6 a. What is a sequential circuit? Discuss the different types of sequential circuits. (06 Marks)  
 b. With a neat logic diagram and timing waveforms describe the operation of a master-slave JK flip-flop. (06 Marks)  
 c. A stable assignment table for a mod-5 counter is given below:

S	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0
1	0	0	1
2	0	1	1
3	1	1	1
4	1	1	0

Derive a counter configuration.

(08 Marks)

- 7 a. Design a clocked synchronous sequential machine using D-Flip Flops for the following [Fig.Q7(a)] state diagram. Use state reduction if possible. Also draw the logic diagram.

 


Fig.Q7(a)

(10 Marks)

- b. Design a synchronous Mod-6 counter using T-FF. Write state table and reduce the expression using K-map. Draw the logic diagram. (10 Marks)

- 8 Write short notes on:  
 a. Implies and subsumes  
 b. Fan-in and Fan-out  
 c. Universal shift register  
 d. Programmable logic arrays

(20 Marks)

\*\*\*\*\*