



10EE56

**Fifth Semester B.E. Degree Examination, June/July 2019**  
**Linear ICs and Applications**

Time: 3 hrs.

Max. Marks: 100

- Note: 1. Answer any FIVE full questions, selecting at least TWO full questions from each part.**  
**2. Standard resistance and capacitance data table may be used.**

**PART – A**

- 1 a. Give the circuit and design steps for
  - i) Capacitor coupled voltage follower.
  - ii) High zin capacitor coupled voltage follower. (08 Marks)
- b. Design the following circuits with  $f_1 = 100\text{Hz}$ ,  $R_L = 3.8\text{K}\Omega$ , gain = 10 and output = 5V p-p.
  - i) Capacitor coupled inverting amplifier
  - ii) Capacitor coupled non-inverting amplifier. (12 Marks)
- 2 a. Give the need for frequency compensation. (04 Marks)
- b. Define phase-margin and explain how phase-lead compensation circuit helps to improve the same. (06 Marks)
- c.
  - i) Draw the graph of open-loop frequency response of Op-Amp and mark  $A_{OL}$ , UGB and open-loop bandwidth (Typical values of 741).
  - ii) Derive equation to calculate maximum peak output and maximum frequency of operation for a given slew-rate.
  - iii) Find the max frequency for 741-op-amp with 5V output [Assume  $SR = 0.5\text{V}/\mu\text{sec}$ ]. (10 Marks)
- 3 a. With the help of a neat circuit diagram and waveforms, explain the working of peak clipper. (06 Marks)
- b. Explain the working of a sample-and-hold circuit. (06 Marks)
- c. Describe the operation of R-2R DAC. (08 Marks)
- 4 a. Give the design steps for inverting Schmitt trigger circuit with variable UTP and LTP. (08 Marks)
- b. Design an astable multivibrator using op-amp to produce  $\pm 1\text{kHz}$  and  $\pm 9\text{V}$  output. (06 Marks)
- c. Draw the circuit of monostable circuit using op-amp with relevant waveforms, briefly give the working. (06 Marks)

**PART – B**

- 5 a. Explain the working of op-amp RC phase-shift oscillator. (06 Marks)
- b. Design a Weinbridge oscillator using BIFET op-amp for output frequency of 10Hz with  $\pm 12\text{V}$ . (06 Marks)
- c. Give the working of a triangular/square wave generator. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- 6 a. Write the circuit and design procedure for second order lowpass and highpass active filters. Draw the expected frequency-response. (10 Marks)
- b. Design single stage band pass-filter with cutoff frequencies 300Hz and 3kHz. (05 Marks)
- c. Explain how a bandstop filter is designed using a lowpass filter and a highpass filter. (05 Marks)
- 7 a. Define the terms line regulation and load regulation. (04 Marks)
- b. With the help of block diagram, explain the PLL operation. (08 Marks)
- c. Briefly explain the operation of op-amp series voltage regulator. (08 Marks)
- 8 a. Explain how a 723 IC can be used as low voltage regulator and high voltage regulator. (12 Marks)
- b. A LM 317 regulator is to provide a 6V output from a 15V supply. The load current is 200mA. Determine suitable resistance values for  $R_1$  and  $R_2$  and calculate regulator power dissipation. (08 Marks)

\* \* \* \* \*