

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, June/July 2019**  
**Electronic Instrumentation**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART – A**

- 1 a. Define the following terms as applied to the electronic instruments i) Accuracy ii) Precision iii) Resolution. (06 Marks)
- b. Explain the working of a true rms voltmeter with the help of suitable block diagram. (08 Marks)
- c. Determine the value of the multiplier resistance on the 0–50V range of a DC voltmeter, that uses a 250 $\mu$ A meter movement with an internal resistance of 100 $\Omega$ . (06 Marks)
- 2 a. Discuss the advantages of a digital voltmeter over an analog voltmeter. (04 Marks)
- b. Explain the block diagram of successive approximation type DVM (Digital voltmeter). (10 Marks)
- c. A 4 $\frac{1}{2}$  digit voltmeter is used for voltage measurements i) Find its resolution ii) How would be 13.87V be displayed on a 10V range? iii) How would the 0.7572V be displayed on 1V and 10V ranges. (06 Marks)
- 3 a. Draw the basic block diagram of an oscilloscope and explain the function of each. (08 Marks)
- b. Describe the following modes of operation available in dual trace oscilloscope i) ALTERNATE ii) CHOP. (06 Marks)
- c. Draw and explain the circuit diagram of an electronic switch. (06 Marks)
- 4 a. With a relevant block diagrams and wave forms explain the working of sampling oscilloscope. (10 Marks)
- b. With a block diagram explain construction and working of digital storage oscilloscope. (10 Marks)

**PART – B**

- 5 a. Explain with the help of block diagram, the operation of the conventional standard signal generator. (05 Marks)
- b. What is sweep frequency generator? Explain with neat block diagram. (07 Marks)
- c. Explain the working of square wave and pulse generator with the neat block diagram. (08 Marks)
- 6 a. Define the sensitivity of a Wheatstone bridge. Derive an equation for galvanometer current of wheat stone bridge under balanced condition. (08 Marks)
- b. The four arms of the Wheatstone bridge have the following resistances arm AB = 900 $\Omega$ , BC = 900 $\Omega$ , CD = 100 $\Omega$ , DA = 100 $\Omega$ . The bridge is used for strain measurement and supplied from 5V ideal battery. The galvanometer has sensitivity of 1mm/ $\mu$ A, with internal resistance of 250 $\Omega$ . Determine the deflection of the galvanometer if arm DA increase to 101 $\Omega$  and arm CD decreases to 99 $\Omega$ . (04 Marks)
- c. Derive an equation for unknown frequency Wein's bridge, and find the equivalent parallel resistance and capacitance that causes a Wein's bridge to null with the following component values. R<sub>1</sub> = 4k $\Omega$ , C<sub>1</sub> = 6 $\mu$ F, R<sub>2</sub> = 30K $\Omega$ , f = 2KHz, R<sub>4</sub> = 120K $\Omega$ . (08 Marks)

- 7 a. What is transducer? Describe the operation of resistance pressure transducer. (06 Marks)  
b. Derive an expression for gauge factor of bonded resistance wire strain gauge. (10 Marks)  
c. A resistance strain gauge with a gauge factor of 3 is cemented to steel member, which is subjected to strain of  $2 \times 10^{-6}$ . If the original resistance value of the gauge is  $150\Omega$ . Calculate the change in resistance. (04 Marks)
- 8 Explain the following with appropriate block diagrams.  
a. Piezo – Electric transducer  
b. Led and LCD display devices  
c. Signal conditioning circuits  
d. Bolometer. (20 Marks)

\* \* \* \* \*