

# CBCS SCHEME

USN

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

17EC34

## Third Semester B.E. Degree Examination, June/July 2019 Digital Electronics

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Construct a truth table and write a Boolean expression for the problem statement. An output variable Y is to be true when the value of inputs exceeds 4. The weights for each input variable is a = 4, b = 3, c = -1, and d = 1. Design the logic circuit for the obtained expression. (10 Marks)
- b. Place the equation  $P = f(a, b, c) = ab + \bar{a}c + b\bar{c}$  into proper canonical form and write the minterms. (05 Marks)
- c. What do you mean by canonical SOP and canonical POS? Explain with example? (05 Marks)

OR

- 2 a. Simplify  $K = f(w, x, y, z) = \sum m(0, 1, 5, 13, 15) + \sum d(2, 7, 10, 14)$  using K-map method. Draw the logic diagram for obtained expression. (10 Marks)
- b. Simplify  $D = f(a, b, c, d) = \sum m(0, 1, 2, 3, 6, 7, 8, 9, 12, 15)$  using QM – method, verify the same using K–map. Draw the logic diagram for simplified expression. (10 Marks)

### Module-2

- 3 a. What is an encoder? Design 4 to 2 priority encoder? (08 Marks)
- b. Realize the function  $X = f(a, b, c, d) = \sum m(0, 3, 7, 10, 13)$  using 74LS138 ICs. (08 Marks)
- c. Design 4 : 1 Mux and draw the logic diagram using basic gates. (04 Marks)

OR

- 4 a. Implement  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 10, 15)$  using 8 : 1 Mux with a, b, c as select lines. (08 Marks)
- b. Design a binary full subtractor using NAND gates only. (06 Marks)
- c. Explain about carry look ahead adder. (06 Marks)

### Module-3

- 5 a. Obtain the characteristic equations for D and T flip-flops. (08 Marks)
- b. Explain the operation of SR-Flip-Flop with the help of logic diagram. Draw functional table. (08 Marks)
- c. What is race around condition? Explain with diagram. (04 Marks)

OR

- 6 a. Explain the working of master slave J-K flip flop with the help of logic diagram. Draw the timing diagrams of the same. (10 Marks)
- b. Explain D-flip-flop operation using positive edge triggered clock. (06 Marks)
- c. Write two-two difference between :
  - i) Combinational and sequential logic
  - ii) Latch and flip-flop. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-4**

- 7 a. What is register? Explain with diagram of 4-bit serial-in parallel-out shift register. (10 Marks)  
 b. Explain 3-bit asynchronous up and down binary counters. (10 Marks)

OR

- 8 a. Design mod-5 ripple counter using T-flip-flops. (08 Marks)  
 b. Design 3-bit synchronous up counter. (08 Marks)  
 c. Compare asynchronous and synchronous counters. (04 Marks)

**Module-5**

- 9 a. Design a Mealy type sequence detector to detect a serial input sequence of 101. (10 Marks)  
 b. Design 2-bit synchronous up counter. (10 Marks)

OR

- 10 a. Analyze the following sequential circuit, by writing input and output equations, state table and state diagram. (12 Marks)

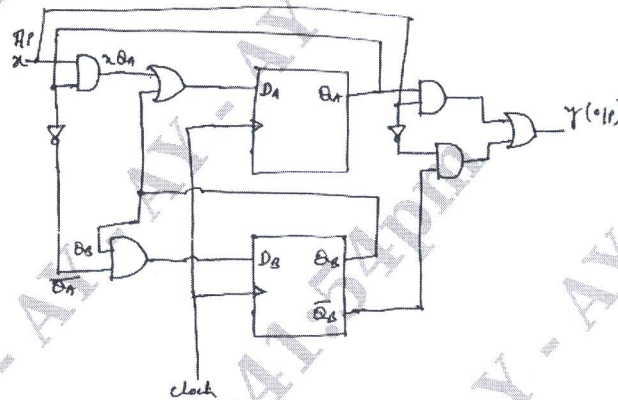


Fig.Q10(a)

- b. What are Mealy and Moore models? Explain briefly with diagram. (04 Marks)  
 c. Draw a state table and state diagram with an example. (04 Marks)

\*\*\*\*\*