

2002 SCHEME

USN

--	--	--	--	--	--	--	--	--	--

EC32

Third Semester B.E. Degree Examination, June/July 2019 Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. For the sketch shown in fig.Q1(a) below V_i varies from 0 to 150V. Sketch the output voltage V_o to the same time scale as the input voltage. Assume diodes to be ideal.

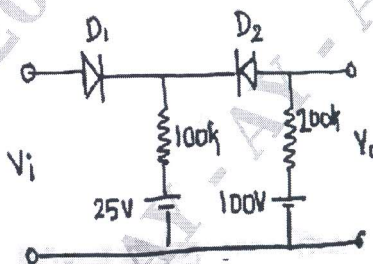


Fig. 1(a)

(08 Marks)

- b. Explain the operation of full wave voltage doubler circuit. (07 Marks)
- c. A full wave rectifier circuit is fed from a secondary center tapped transformer. The rms voltage from either end of secondary to center tap is 30V if diode resistance $R_f = 2\Omega$, half secondary resistance $R_s = 8\Omega$ and load $R_L = 1k\Omega$, calculate efficiency of rectification. (05 Marks)
- 2 a. Discuss the causes for bias instability in a transistor. (05 Marks)
- b. With neat circuit diagram, explain how compensation for V_{BE} can be obtained using diode in emitter circuit of a transistor. (05 Marks)
- c. A Ge transistor used in self biased circuit has $V_{CC} = 20V$, $R_C = 2k$, operating point $V_{CE} = 10V$ and $I_C = 4mA$, and $\beta = 50$. Calculate R_1 , R_2 and R_E if stability factor $S = \delta I_C / \delta I_{CO} = 10$ is desired. (10 Marks)
- 3 a. Draw the h-parameter equivalent circuit for CE amplifier. Derive an expression for A_i , R_i , A_v , R_0 , A_{vs} and A_{IS} . (10 Marks)

- b. For the amplifier shown in Fig.Q3(b), calculate R_i , R_i' , A_v , A_{vs} and $A_i' = -\frac{I_2}{I_1}$.

The transistor parameters are $h_{ie} = 1100\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 25 \times 10^{-6} A/V$.

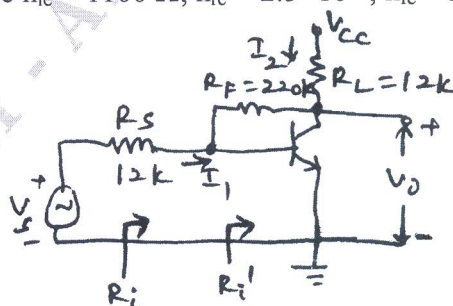


Fig.Q3(b)

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. For the SL 100 transistor following data are available:
 $h_{ic} = 2000 \Omega$, $h_{fe} = 100$, $h_{re} = 10^{-4}$, $h_{oe} = 25 \times 10^{-6} \text{ A/V}$ at $I_C = 2 \text{ mA}$ and $T = 27^\circ\text{C}$, $C_{ob} = 5 \text{ pF}$.
Assume $f_T = 50 \text{ MHz}$. Determine all the hybrid- π parameter. Draw the hybrid- π model and incorporate all the component values. (08 Marks)
- b. Derive an expression for output conductance g_{ce} . (06 Marks)
- c. Explain the different types of distortions in an amplifier. (06 Marks)
- 5 a. Discuss general characteristics of negative feedback amplifier. (08 Marks)
- b. Derive an expression for input resistance of voltage series feedback topology. (06 Marks)
- c. Draw a block diagram of feedback in amplifier and explain each block. (06 Marks)
- 6 a. Write the features of op-amp. (06 Marks)
- b. With a neat diagram, explain op-amp as differential amplifier. (08 Marks)
- c. Define: i) C.M.R.R.; ii) Slew rate; iii) P.S.R.R.; iv) Offset voltage. (06 Marks)
- 7 a. Define the following terms with respect to op-amp:
i) Input bias current ii) Output offset voltage (04 Marks)
- b. Draw the circuit of a differential instrumentation amplifier using a transducer bridge and explain its features. Also derive the expression for its output voltage. (10 Marks)
- c. Determine the circuit elements of an op-amp Schmitt trigger with the following specifications: $UTP = 2\text{V}$, $LTP = -4\text{V}$ and the output swings between $\pm 10\text{V}$. (06 Marks)
- 8 a. Explain the operation of a sample and hold circuit. (06 Marks)
- b. Explain the operation of a positive peak detector with relevant waveforms. (06 Marks)
- c. Draw the circuit diagram of a astable multi-vibrator using 555 timer and explain its operation. (08 Marks)
