

Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain five types of power electronic converter circuits briefly. Also indicate two applications of each type. (10 Marks)
- b. Give symbol, and characteristic features of the following devices: (10 Marks)
 - i) RCT ii) GTO iii) Triac iv) SCR v) IGBT
- 2 a. Give the comparison between BJT, MOSFET and IGBT. (06 Marks)
- b. What is the necessity of base drive control in a power transistor? Explain antisaturation control. (08 Marks)
- c. For a transistor switch shown in Fig.Q2(c):
 - i) Calculate the forced beta, β_f of transistor.
 - ii) If the manufacturers specified β is in the range of 8 to 40, calculate the minimum overdrive factor (ODF)
 - iii) Obtain power loss P_T in the transistor.

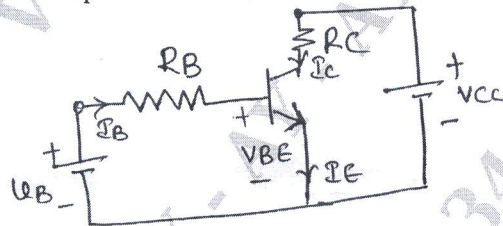


Fig.Q2(c)

$$\begin{aligned}
 V_B &= 10\text{V}, R_B = 0.75\Omega \\
 V_{BE(\text{sat})} &= 1.5\text{V} \\
 R_C &= 11\Omega, V_{CC} = 200\text{V} \\
 V_{CE(\text{sat})} &= 1\text{V}
 \end{aligned}$$

(06 Marks)

- 3 a. Draw the two transistor model of a thyristor and derive an expression for the anode current in terms of the common base current gain α_1 and α_2 of the transistors. (09 Marks)
- b. What is the need for protection of thyristor? Explain how thyristors are protected against high $\frac{di}{dt}$. (06 Marks)
- c. Explain different methods to turn on a thyristor. (05 Marks)
- 4 a. What will be the average power in the load for the circuit shown in Fig.Q4(a), when $\alpha = \frac{\pi}{4}$. Assume SCR to be ideal. Supply voltage is $330 \sin 314t$. Also calculate the RMS power and the rectification efficient. (06 Marks)

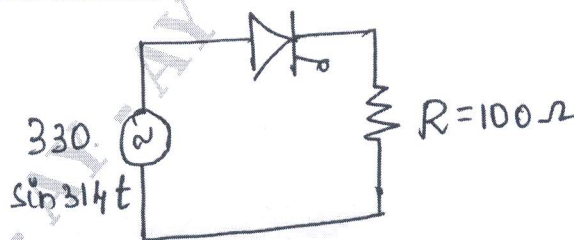


Fig.Q4(a)

(06 Marks)

- b. With a neat circuit diagram and waveforms, explain the working of a single phase full controlled bridge converter feeding highly inductive load. Derive the expression for the average output voltage and rms output voltage. (10 Marks)
- c. Compare full controlled and semi-controlled rectifiers. (04 Marks)

PART – B

- 5 a. With a neat circuit diagram and waveforms, explain complementary commutation. (10 Marks)
- b. In the resonant pulse commutation circuit, the supply voltage is $V_s = 200$ V, load current $I_o = 150$ A, the commutation inductance $L = 4\mu\text{H}$ and commutation capacitance $C = 20\ \mu\text{F}$. Determine the peak resonant reversing current of thyristor T_3 and turn OFF time t_{OFF} for T_1 . Assume $V_o = V_s$. (10 Marks)
- 6 a. With relevant circuit and waveform, explain the principle of single phase fullwave AC voltage controller with resistive load. Derive expression for RMS output voltage. (10 Marks)
- b. A single phase FW ac voltage controller working on ON-OFF control has supply voltage of 230 V RMS, 50 Hz and load is $50\ \Omega$. The controller is ON for 30 cycles and OFF for 40 cycles. Calculate:
- ON or OFF time interval
 - RMS output voltage
 - Input power factor
 - Average and RMS thyristor current
- (06 Marks)
- c. Compare ON-OFF controller and phase controller. (04 Marks)
- 7 a. Give the classification of choppers. Explain briefly each one of them. (10 Marks)
- b. Explain the working of boost regulator with waveforms. (06 Marks)
- c. Explain the principle of operation of step up chopper. (04 Marks)
- 8 a. Explain the performance parameters of inverters. (06 Marks)
- b. Explain the operations of single phase half bridge inverter. (08 Marks)
- c. Explain the working of variable DC link inverter. (06 Marks)

* * * * *