

CBCS SCHEME

15EC32

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Draw the circuit diagram of common Emitter fixed bias configuration. Derive the expression for Z_i , Z_o , A_v using r_e model. (08 Marks)
- b. For the network shown in Fig. Q1 (b), determine Z_i , Z_o , A_v and A_i . Given $h_{ie} = 1.175 \text{ K}\Omega$, $h_{fe} = 120$, $h_{oe} = 20 \mu\text{A/v}$ using approximate hybrid equivalent model. (08 Marks)

 


Fig. Q1 (b)

OR

- 2 a. Draw ' r_e ' and ' h '-parameter models for a transistor in common Emitter configuration. Also give relation between ' r_e ' and ' h '-parameter. (05 Marks)
- b. For the circuit shown below, calculate r_e , Z_i , Z_o and A_v , while consider $r_o = \infty$. (08 Marks)

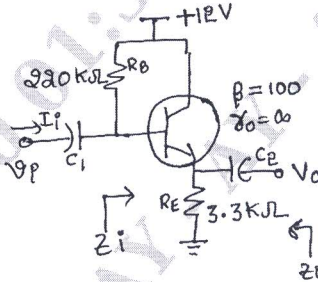


Fig. Q2 (b)

- c. What are the advantages of h-parameters? (03 Marks)

Module-2

- 3 a. Explain the small signal model of the FET. (04 Marks)
- b. Derive the expression for Z_i , Z_o and A_v for FET voltage divider bias circuit. (08 Marks)
- c. Compare JFET and MOSFET. (04 Marks)

OR

- 4 a. Explain the n-channel enhancement type MOSFETs, with their characteristics curves. (08 Marks)
- b. Derive the expression for Z_i , Z_o and A_v for FET self biased configuration (with R_s bypassed). (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Prove that
Input capacitance is $C_{Mi} = (1 - A_v)C_f$ and
Output capacitance is $C_{Mo} = \left(1 - \frac{1}{A_v}\right)C_f$ using miller effect. (08 Marks)
- b. Describe the factors that affect the low frequency response of a BJT-CE amplifier. (08 Marks)

OR

- 6 a. Explain high frequency response of FET amplifier and derive expression for cut off frequencies, defined by input and output circuits (f_{Hi} and f_{Ho}). (08 Marks)
- b. Determine the lower cut off frequency for the network shown in Fig. Q6 (b), using following parameters $g_m = 2 \text{ ms}$, $r_d = \infty \Omega$, $I_{DSS} = 8 \text{ mA}$, $V_P = -4 \text{ V}$, $V_{DD} = 20 \text{ V}$. (08 Marks)

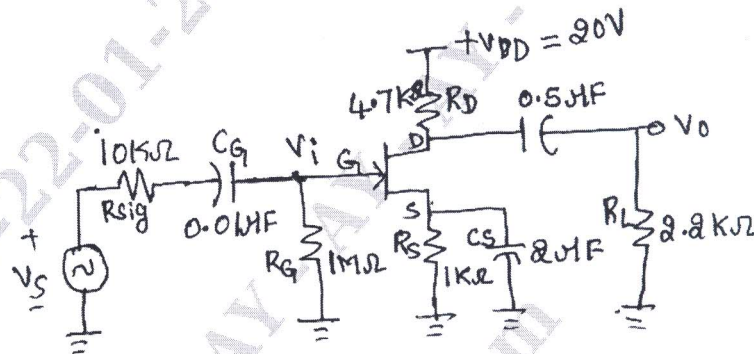


Fig. Q6 (b)

Module-4

- 7 a. With the help of a neat circuit diagram, explain the working of Hartley oscillator. (08 Marks)
- b. The following data for Colpitts oscillator are as follows : $C_1 = 1 \text{ nF}$, $C_2 = 99 \text{ nF}$, $L = 1.5 \text{ mH}$ and $h_{fe} = 110$. Calculate frequency of oscillation for the same. (04 Marks)
- c. Explain the important advantages of a negative feedback amplifier. (04 Marks)

OR

- 8 a. Mention the types of feedback connections. Draw their block diagrams indicating input and output signal. (08 Marks)
- b. Obtain expression for Z_{if} , Z_{of} for a voltage series feedback. (08 Marks)

Module-5

- 9 a. Explain the operation of a class B push-pull amplifier and also show that its efficiency is 78.50%. (08 Marks)
- b. With a neat circuit diagram, explain the operation of a transformer coupled class A power amplifier. (08 Marks)

OR

- 10 a. For a harmonic distortion reading of $D_2 = 0.1$, $D_3 = 0.02$ and $D_4 = 0.01$, with $I_1 = 4 \text{ A}$ and $R_C = 8 \Omega$, calculate the total harmonic distortion, fundamental power and total power. (04 Marks)
- b. What are the classification of power amplifiers, based on the location of Q - point? Discuss them briefly. (08 Marks)
- c. With the help of neat block diagram, explain the working of shunt voltage regulator. (04 Marks)
