

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020
Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any **FIVE** full questions, choosing **ONE** full question from each module.

Module-1

- 1 a. Derive the expression for Delta-star transformation. (06 Marks)
 b. Using source transformation, find the power delivered by 50V source shown in Fig.Q.1(b). (06 Marks)

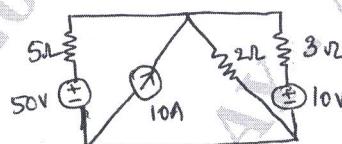


Fig.Q.1(b)

- c. Find the voltage a/c 20Ω resistor in the network shown in Fig.Q.1(c). (08 Marks)

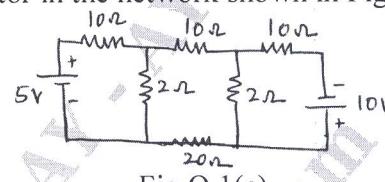


Fig.Q.1(c)

OR

- 2 a. Determine the equivalent resistance between the terminals AB for the network shown in Fig.Q.2(a). (06 Marks)

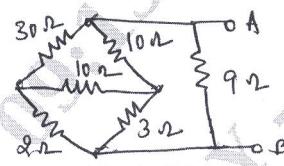


Fig.Q.2(a)

- b. Find the node voltages V_1 , V_2 and V_3 in the circuit shown in Fig.Q.2(b) using nodal analysis. (08 Marks)

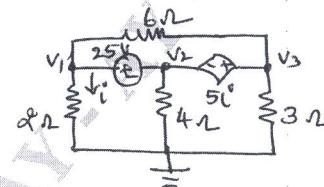


Fig.Q.2(b)

- c. Draw the dual of the network shown in Fig.Q.2(c). (06 Marks)

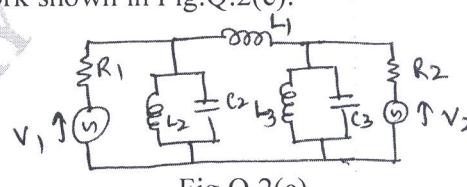


Fig.Q.2(c)

Module-2

- 3 a. State and explain superposition theorem. (06 Marks)
 b. For the circuit shown in Fig.Q.3(b) obtain Thevinins equivalent circuit as seen from terminals p-q. (08 Marks)

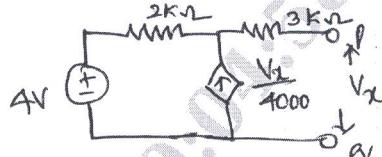


Fig.Q.3(b)

- c. Find the voltage 'Vx' and apply reciprocity theorem to the networks shown in Fig.Q.3(c). (06 Marks)

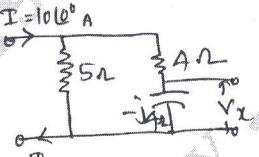


Fig.Q.3(c)

OR

- 4 a. State and explain Norton's theorem. (06 Marks)
 b. Find the current I_a in the circuit shown in Fig.Q.4(b) by applying superposition theorem. (08 Marks)

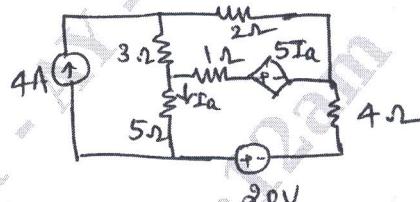


Fig.Q.4(b)

- c. Find the current through 16Ω resistance using Norton's theorem for Fig.Q.4(c) (06 Marks)

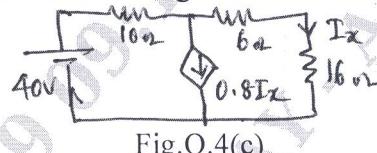


Fig.Q.4(c)

Module-3

- 5 a. Show that in series resonant circuit the resonant frequency is equal to the geometric mean of half power frequencies. (06 Marks)
 b. A circuit shown in Fig.Q.5(b), the switch 'K' is changed from position 1 to 2 at $t = 0$. The steady state having reached before closing the switch. Find the values of $i(t)$, $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t = 0^+$ (08 Marks)

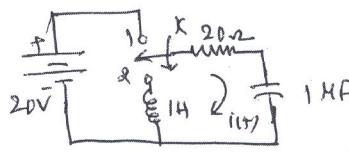


Fig.Q.5(b)

- c. A series RLC circuit has $R = 2\Omega$, $L = 2\text{mH}$ and $C = 10\mu\text{F}$. Calculate Q factor, bandwidth, resonant frequency and half power frequencies. (06 Marks)

OR

- 6 a. Show that a parallel resonant circuit will resonate for all frequencies when $R_L = R_C = \sqrt{\frac{L}{C}}$?
(06 Marks)

- b. In the circuit shown in Fig.Q.6(b) initially switch 'K' is kept open for long time. At $t = 0$, switch K is closed. Obtain the expression for current in the circuit for $t > 0$.

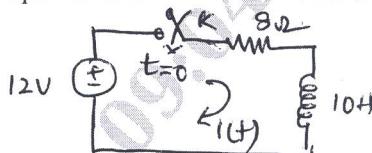


Fig.Q.6(b)

- c. Find the value of R_1 such that the circuit shown in Fig.Q.6(c) is resonant.

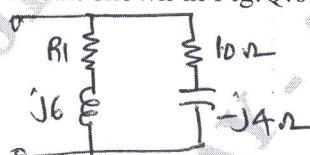


Fig.Q.6(c)

(06 Marks)

(08 Marks)

Module-4

- 7 a. Find the inverse Laplace transform of the following:

$$\text{i) } F(s) = \frac{s+2}{s(s+3)(s+4)} \quad \text{ii) } F(s) = \frac{(s-2)}{s(s+1)^3}$$

(06 Marks)

- b. State and prove initial value and final value theorem.

- c. Obtain the Laplace transform of the gate function shown in Fig.Q.7(c).

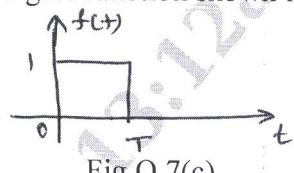


Fig.Q.7(c)

(08 Marks)

(06 Marks)

OR

- 8 a. Using Laplace transform determine the current in circuit shown in Fig.Q.8(a) when switch K is closed at $t = 0$. Assume zero initial condition.
(06 Marks)

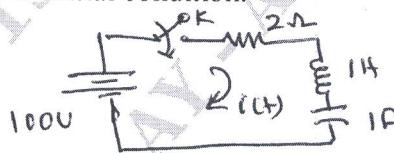


Fig.Q.8(a)

- b. Find the Laplace transform of periodic functions shown in Fig.Q.8(b)
(08 Marks)

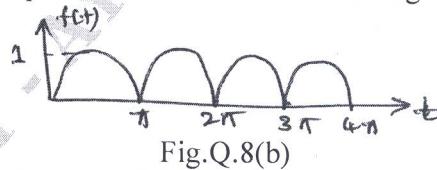


Fig.Q.8(b)

- c. Find initial value and final value of the following equations:

$$\text{i) } F(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)} \quad \text{ii) } F(s) = \frac{s(s+4)(s+8)}{(s+1)(s+6)}$$

(06 Marks)

Module-5

- 9 a. An unbalanced 3-phase, 4-wire star connected load has balanced voltages of 208V, with ABC phase sequence. Calculate the line currents and neutral current.

$$Z_A = 10\Omega; \quad Z_B = 15|30^\circ\Omega; \quad Z_C = 10|-30^\circ\Omega$$

(06 Marks)

- b. Derive Z-parameters in terms of y and h-parameters.

(08 Marks)

- c. Find Y-parameters for the network shown in Fig.Q.9(c)

(06 Marks)

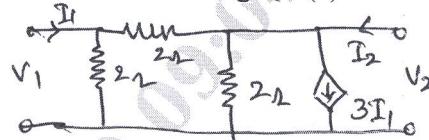


Fig.Q.9(c)

OR

- 10 a. Determine the line currents and total power supplied to a delta connected load of $Z_{ab} = 10|60^\circ\Omega$, $Z_{bc} = 20|90^\circ\Omega$, $Z_{ca} = 25|30^\circ\Omega$. Assume 3-phase 400V, ABC sequence.

(06 Marks)

- b. Determine the transmission parameters for the networks shown in Fig.Q.10(b).

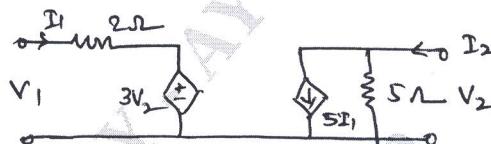


Fig.Q.10(b)

(08 Marks)

- c. Define Z-parameters and Y-parameters and write equivalent circuits.

(06 Marks)
