



## Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. For the network K shown in Fig Q1(a) find potential between M and N using source transformation. (04 Marks)
- b. Using Mesh current Analysis determine  $V_x$  and power supplied by 10 volt source of the network shown in Fig Q1(b). (06 Marks)

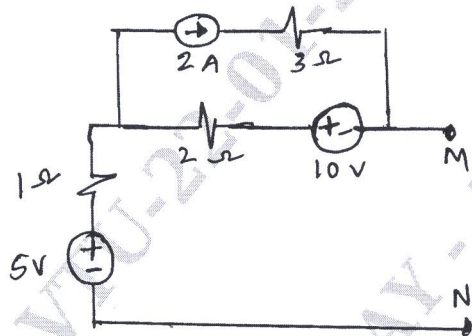


Fig Q1(a)

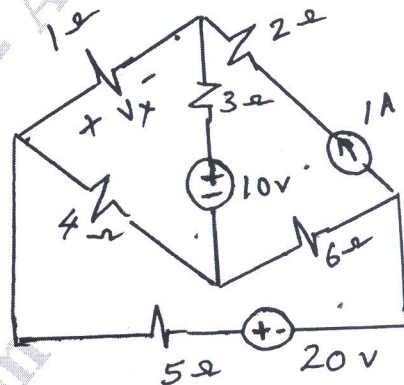


Fig Q1(b)

- c. What is Resonance? Show that the resonant frequency is geometric mean of cut off frequencies. (06 Marks)

OR

- 2 a. For the circuit shown in Fig Q2(a), find the resistance between M and N using Star/Delta transformation. (05 Marks)
- b. Using Node voltage analysis, find  $V_x$  and  $I_x$  of the circuit shown in Fig Q2(b) (06 Marks)

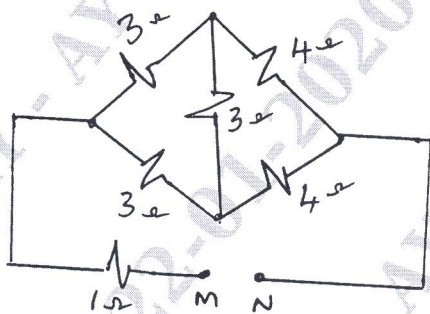


Fig Q2(a)

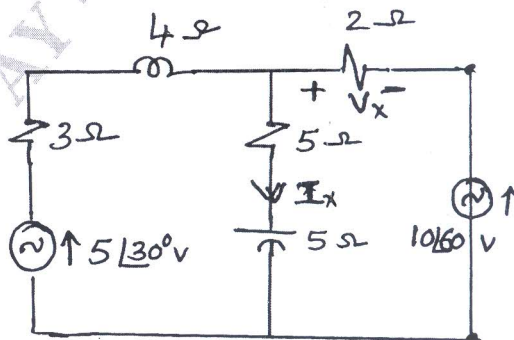


Fig Q2(b)

- c. A coil of  $20\Omega$  resistance was in inductance of 0.2 henry and is connected in parallel with capacitance of  $100\mu\text{F}$ . Find the resonant frequency at which circuit will act as non inductive resistance, Also find the dynamic resistance. (05 Marks)

### Module-2

- 3 a. State and prove Reciprocity theorem. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. For the network shown in Fig Q3(b), find current  $I$  using Milliman's theorem. (05 Marks)  
 c. For the network shown in Fig Q3(c), find current  $I$  using Norton's theorem. (06 Marks)

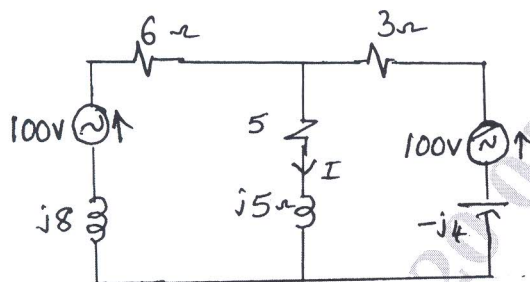


Fig Q3(b)

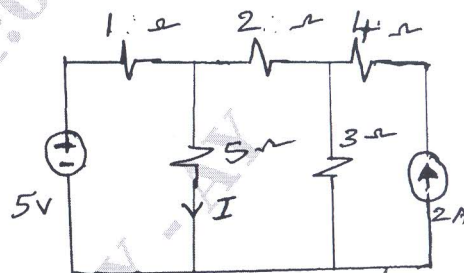


Fig Q3(c)

OR

- 4 a. Draw the Thevenin's equivalent circuit of Fig shown in Fig Q4(a). (05 Marks)  
 b. For the network shown in Fig Q4(b), find the current ' $I_x$ ' using superposition theorem. (05 Marks)

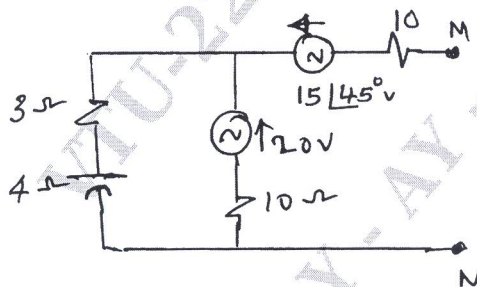


Fig Q4(a)

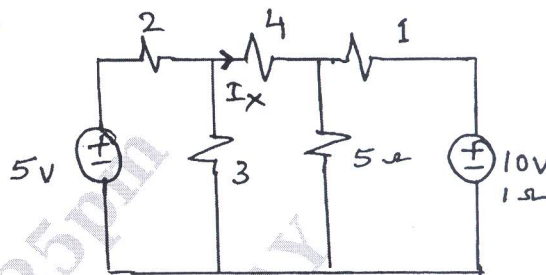


Fig Q4(b)

- c. State and obtain the condition for maximum power transfer when load consisting of variable resistance and variable reactance. (06 Marks)

**Module-3**

- 5 a. Explain the behavior of Resistance, inductance and capacitance for initial condition. (05 Marks)  
 b. For the network shown in Fig Q5(b), switch is closed at  $t = 0$ . Write expression for current  $i(t)$  for  $t > 0$ . (06 Marks)  
 c. For the circuit shown in Fig Q5(c), switch is closed at  $t = 0$ . Obtain expression for current  $i(t)$  for  $t > 0$ . (05 Marks)

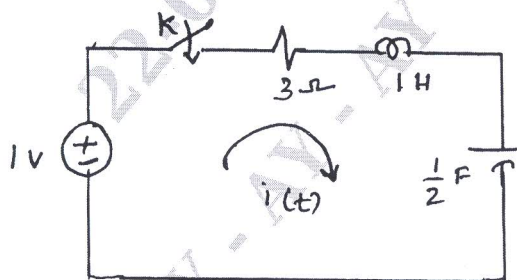


Fig Q5(b)

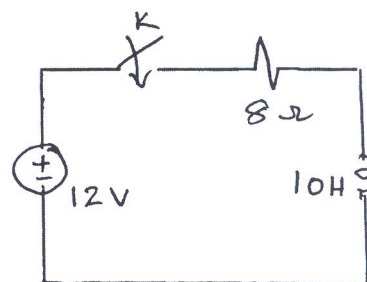


Fig Q5(c)



OR

- 6 a. Define initial condition and final condition and list merits of initial conditions. (04 Marks)  
 b. For the network shown in Fig Q6(b) switch is changed from M to N at  $t = 0$  after reaching steady state condition. Find current  $i(t)$  and its derivatives at  $t = 0^+$ . (06 Marks)  
 c. For the network shown in Fig Q6(c) switch is opened at  $t = 0$ . Find voltage  $v(t)$  and its first and second derivatives at  $t = 0^+$ . (06 Marks)

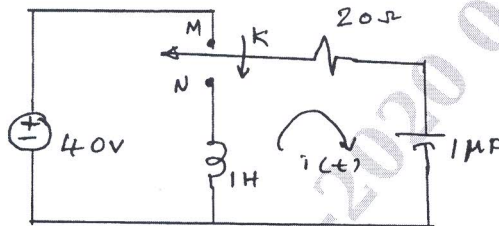


Fig Q6(b)

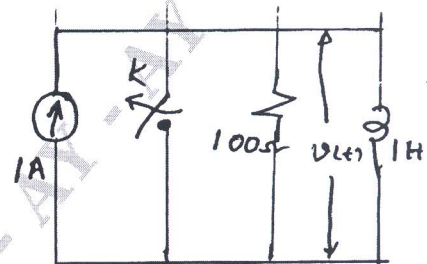


Fig Q6(c)

**Module-4**

- 7 a. State and explain Final value theorem. (05 Marks)  
 b. If the capacitors are uncharged and the inductor current is zero at  $t = 0^-$ , in the given network shown in Fig Q7(b). Show that the transform of the generator current is  $\frac{10(s^2 + s + 1)}{(s^2 + 1)(s^2 + 2s + 2)}$ . (05 Marks)  
 c. Synthesis the waveform shown in Fig Q7(c) and find the Laplace transform. (06 Marks)

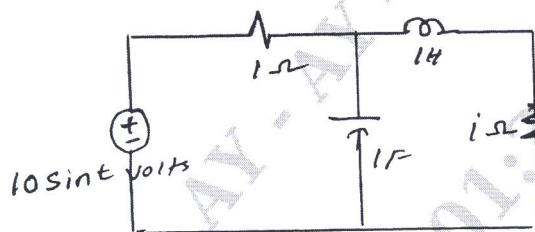


Fig Q7(b)

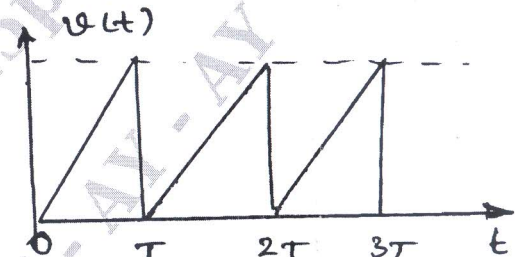


Fig Q7(c)

OR

- 8 a. Find the Laplace transform of following standard signal. i) Unit step ii) Ramp iii) Impulse (05 Marks)  
 b. Let  $I(s) = \frac{2s + 5}{(s + 1)(s + 2)}$ . Find its initial value using initial value theorem. Verify the result. (04 Marks)  
 c. For the network shown in Fig Q8(c) at  $t = 0$  switch is opened. Find node voltage  $v_1(t)$  and  $v_2(t)$ . The network is under steady state condition when the switch is closed. (07 Marks)

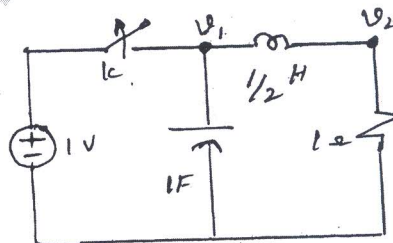


Fig Q8(c)

**Module-5**

- 9 a. Determine the line currents and total power supplied to a Delta connected load of  $Z_{AB} = 10 \angle 60^\circ$ ,  $Z_{BC} = 20 \angle 90^\circ$  and  $Z_{CA} = 25 \angle 30^\circ \Omega$ . Assume a 3 phase 400V and ABC sequence. (06 Marks)
- b. For the network shown in Fig Q9(b), obtain the z - parameters. (06 Marks)
- c. Obtain driving point impedance and driving point admittance of one port network shown in Fig Q9(c). (04 Marks)

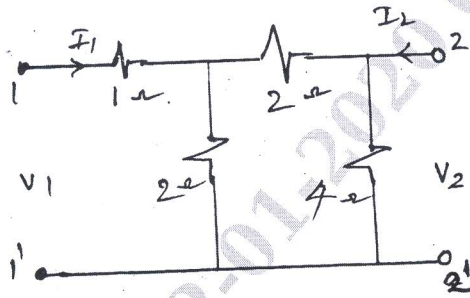


Fig Q9(b)

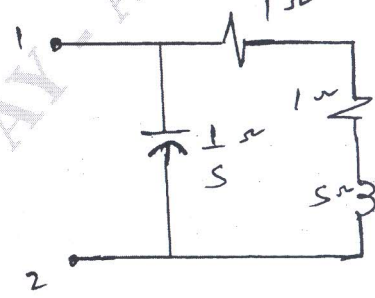


Fig Q9(c)

**OR**

- 10 a. Obtain y-parameters interms of z-parameters. (06 Marks)
- b. A voltage pulse of 10V magnitude is applied to the network shown in Fig Q10(b). Find the current  $i(t)$ . (06 Marks)
- c. Determine the system function if the d.c gain of the system is 10 and pole zero plot is as shown in the Fig Q10(c). (04 Marks)

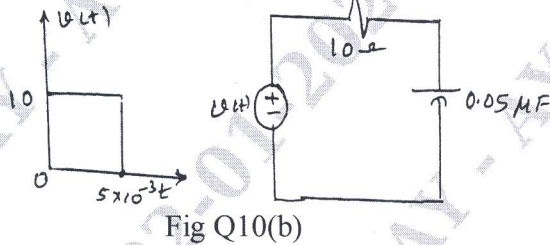


Fig Q10(b)

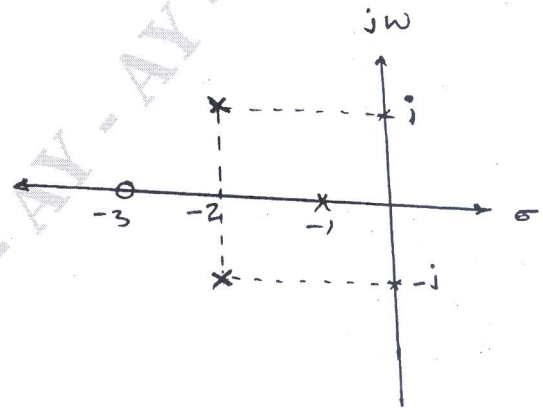


Fig Q10(c)

\*\*\*\*\*