



CBCS SCHEME

17MT35

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With a neat circuit derive the expression for gain of 1st order Butterworth High Pass filter as a function of frequency. Also write the frequency response diagram for it. (10 Marks)
- b. Explain the working of all Pass filters with neat circuit and necessary waveforms. Also derive the expression for gain. (10 Marks)

OR

- 2 a. Explain the filter design steps for 1st order low pass filter. Design a 1st order low pass filter at a cutoff frequency of 1 kHz with a pass band gain of 2. Using frequency scaling technique converts 1 kHz cutoff frequency to 1.6 kHz. (10 Marks)
- b. With neat circuit, frequency response diagram and with necessary equations explain the working of narrow band pass filter. (10 Marks)

Module-2

- 3 a. With neat sketch and necessary equations explain the operator Re phase shift oscillator. Also design a phase shift oscillator with $f_0 = 200$ Hz. (10 Marks)
- b. With neat circuit diagram, explain the working of Schmitt trigger circuit. (10 Marks)

OR

- 4 a. Explain the principle of oscillation with the help of block diagram. Also define frequency stability. (10 Marks)
- b. With the help of circuit diagram, explain the working of non-inverting comparator. Also write the output waveforms for positive V_{ref} and negative V_{ref} . (10 Marks)

Module-3

- 5 a. Explain how 555 timer can be used as monostable multivibrator. (10 Marks)
- b. Explain the application of monostable multivibrator as frequency divider circuit. A monostable multivibrator used as a divide by 2 Network. The frequency of input trigger signal is 2 kHz. If the value of $e = 0.01 \mu F$, what should be the value of resistance. (10 Marks)

OR

- 6 a. Explain the operation of Astable multivibrator circuit with neat sketch and relevant equations. (10 Marks)
- b. Explain the application of Astable multivibrator as free-running ramp generator. Also find the free running frequency of ramp generator if $V_{BE} = V_{D_1} = 0.7V$, $R = 10 k\Omega$, $e = 0.05 \mu F$ and $V_{CC} = 5 V$. (10 Marks)

Module-4

- 7 a. Simplify the Boolean function $F(W, X, Y, Z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ (06 Marks)
b. Write K map for Boolean junction with three variables. (04 Marks)
c. Construct a full adder from two half adder. (10 Marks)

OR

- 8 a. Define MUX. Construct 4 to 1 line MUX. Also implement the following function using MUX $F(A, B, C) = \sum(1, 3, 5, 6)$ (10 Marks)
b. What is decoder? Write the circuit for 2 to 4 decoder. Construct 4×16 decoder using two 3×8 decoder IC. (10 Marks)

Module-5

- 9 a. With neat sketch, explain clocked J-K flip flop. Write characteristic table and derive expression for characteristic equation. (10 Marks)
b. Design a 3 bit binary up-down counter. (10 Marks)

OR

- 10 a. With neat sketch, explain the operation of clocked D flip flop. Also derive the characteristic equation. (10 Marks)
b. Design a 3 bit synchronous binary counter. (10 Marks)
