 


CBCS SCHEME



17EE34

Third Semester B.E. Degree Examination, Aug./Sept.2020 Analog Electronic Circuits

Time: 3 hrs.


Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. For the clipper circuit shown in fig. Q1(a), the input is $V_i = 50 \sin \omega t$. Calculate and plot to scale the transfer characteristic, indicating slopes and intercept.


(10 Marks)

 

 - b. An emitter bias circuit has $R_C = 2K \Omega$, $R_E = 680 \Omega$, $V_E = 2.1V$, $V_{CE} = 7.3V$, $I_B = 20\mu A$. Find V_{CC} , R_B & β . (05 Marks)
- c. What is meant by transistor biasing? Compare different biasing methods used for transistor biasing with respect to stability. (05 Marks)

OR

- 2 a. Design a suitable circuit represented by the box shown below. Which has input and output waveforms as indicated in fig. Q2(a). (08 Marks)



- b. Find the operating point for the voltage divider bias circuit with $\beta = 80$ and $V_{BE} = 0.6V$. Find the new operating point when β changes to 100 and V_{BE} changes to 0.25V. Given $V_{CC} = 15V$, $R_1 = 100 K\Omega$, $R_2 = 18K\Omega$, $R_C = 4.7K\Omega$ and $R_E = 1K\Omega$. (08 Marks)
- c. Explain the circuit of a transistor switch being used as an inverter. (04 Marks)

Module-2

- 3 a. Draw the hybrid small signal model of a transistor. Mention the advantages of h-parameters. (04 Marks)
- b. Derive the expression for A_V , A_I , Z_i and Z_o for CE fixed bias configuration using complete hybrid equivalent model. (10 Marks)
- c. State and prove Miller's theorem. (06 Marks)

OR


- 4 a. Derive the expressions for Z_i , Z_o , A_V and A_I for CB - configuration of transistor using approximate hybrid equivalent model. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. The circuit shown in fig.Q4(b) uses transistor with $h_{ie} = 1100\Omega$, $h_{fe} = 50$, $h_{oe} = 0.025 \times 10^{-3} \Omega$, $h_{re} = 2.5 \times 10^{-4}$. Calculate $R_i = \frac{V_i}{I_i}$, $R'_i = \frac{V_i}{I_b}$, $A_v = \frac{V_o}{V_i}$ and

$$A_{v_s} = \frac{V_o}{V_s}$$

Fig.Q4(b)

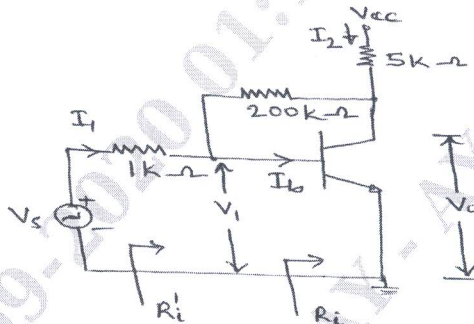

(10 Marks)

Module-3

- 5 a. Explain with the help of circuit, what is cascade connection? What are the advantages of this connection? (06 Marks)
- b. What is negative feedback in amplifiers? Show that negative feedback increases the bandwidth of an amplifier. (08 Marks)
- c. An amplifier with negative feedback has a voltage gain of 100. It is found that without feedback, an input signal of 50mV is required to produce a given output. Where as with feedback the input signal must be 0.5V for the same output. Determine the value of A and β . (06 Marks)

OR

- 6 a. With appropriate h-parameters equivalent circuit, obtain the expression for Z_i , Z_o , A_v for a Darlington emitter follower. (10 Marks)
- b. Derive expression Z_{if} and Z_{of} for voltage series feedback amplifier. (10 Marks)

Module-4

- 7 a. Discuss the different types of power amplifiers. (04 Marks)
- b. Show that the maximum percentage efficiency for a series fed class A amplifier is 25%. (10 Marks)
- c. A Quartz crystal has $L = 0.12H$, $C = 0.04 PF$, $C_M = 1PF$ and $R = 9.2 K\Omega$. Find
i) f_s and ii) f_p . (06 Marks)

OR

- 8 a. State and explain the Barkhensen's criterion to obtain sustained oscillations. (06 Marks)
- b. With the help of circuit diagram, explain the working principle of R_c = phase shift oscillator, with relevant equations. (08 Marks)
- c. A class B amplifier provides a 20V peak signal to a 16Ω load and a power supply of $V_{CC} = 30V$. Determine the input power, output power and circuit efficiency. (06 Marks)

Module-5

- 9 a. Draw the JFET amplifier using fixed bias configuration. Derive Z_i , Z_o and A_v using small signal model. (08 Marks)
- b. Compare JFET and MOSFET. (04 Marks)

- c. Design a fixed bias circuit of fig. Q9(c) to have ac gain of -15. Calculate the value of R_D to get this gain, if $V_{DD} = 40V$, $R_G = 10m\Omega$, $I_{DSS} = 10mA$, $V_P = -4V$, $Y_{OS} = 20\mu s$, $C_1 = 0.1\mu F$.
(08 Marks)

 


Fig.Q9(c)

OR

- 10 a. Sketch a typical characteristics for an n – channel JFET. Explain the shape of the characteristics and identify the regions. (10 Marks)
 b. Calculate the voltage gain, input and output impedance for the circuit of fig. Q10(b). Given $I_{DSS} = 16mA$, $V_P = -4V$, $r_d = 40K\Omega$, $V_{GSO} = -2.86V$. (10 Marks)

 


Fig.Q10(b)
