



CBCS SCHEME

17MT35

Third Semester B.E. Degree Examination, Aug./Sept. 2020

Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Design a second order lowpass Butterworth filter at a higher cutoff frequency of 1KHz and draw the frequency response. (10 Marks)
- b. Design a highpass filter at a cutoff frequency of 1KHz with a passband gain of 2 and plot the frequency response. (10 Marks)

OR

- 2 a. Design a wide bandpass filter with $f_c = 200\text{Hz}$ and $f_H = 1\text{ KHz}$ and passband gain = 4 and draw the frequency response. (10 Marks)
- b. With neat diagram, explain all pass filter and derive the expression for gain and phase angle. (10 Marks)

Module-2

- 3 a. With neat circuit diagram, explain the operation of phase shift oscillator. (08 Marks)
- b. Design a phase shift oscillator so that $f_0 = 200\text{Hz}$. (04 Marks)
- c. With a neat circuit diagram, explain the operation of wien bridge oscillator. (08 Marks)

OR

- 4 a. Explain zero crossing detectors with input and output waveforms. (10 Marks)
- b. Explain the operation of Schmitt trigger with all necessary diagrams. (10 Marks)

Module-3

- 5 a. With neat diagrams, explain the pin diagram and architecture of 555 Timer. (10 Marks)
- b. Explain the operation of 555 Timer as a monostable multi-vibration with necessary diagrams. (10 Marks)

OR

- 6 a. Explain the operation of 555 Timer as an Astable multivibrator with necessary diagram. (10 Marks)
- b. With neat circuit diagrams, explain the applications of astable multivibrator. (10 Marks)

Module-4

- 7 a. Simplify the Boolean functions using K-maps
 - i) $F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
 - ii) $F(ABCD) = A'B'C' + B'CD' + A'BCD' + AB'C'$
 - iii) $F = A'C + A'B + AB'C + BC$(10 Marks)
- b. Explain full adder and full subtractor with the help of truth table, derive the expression for sum, carry, borrow and difference. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 8 a. Implement the following function with a multiplexer $F(ABCD) = \sum(0, 1, 3, 4, 8, 9, 15)$.
By taking A as input and remaining as selection lines. (08Marks)
- b. With neat logic diagram and truth table explain octal-to-binary encoder. (06 Marks)
- c. Design a BCD to decimal decoder. (06 Marks)

Module-5

- 9 a. Explain the following flip flops with logic diagram and truth table.
i) RS Flip flop
ii) D flip flop
iii) T flip flop. (10 Marks)
- b. Explain J-K flip-flop with truth table and how race around condition will be over come by master slave. (10 Marks)

OR

- 10 a. Explain BCD ripple counter operation with the help of state diagram, logic diagram and timing diagram. (10 Marks)
- b. Design a Binary up counters using T-flip flops. (10 Marks)
