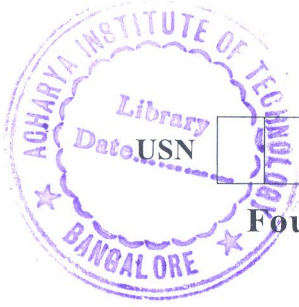


# CBCS SCHEME



16/17EPS424

## Fourth Semester M.Tech. Degree Examination, Aug./Sept.2020 Integration of Renewable Energy

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. With a neat figure, explain DC architecture of green and renewable power grid distribution system. (08 Marks)
- b. Explain how a DG system operations as a part of utility power system. (08 Marks)

OR

- 2 a. Outline the smart grid PV – UPS DG system. (08 Marks)
- b. Deduce an expression for equivalent control input of discrete time sliding mode current controller considering the inverter and filter subsystem without transformer and load dynamics. (08 Marks)

### Module-2

- 3 a. Describe grid connected and stand alone AC power supply applications of DGS. (08 Marks)
- b. Explain how power flows when two inverters are connected to load. (08 Marks)

OR

- 4 a. Outline the different methods used to control the inverter voltage. (08 Marks)
- b. Enumerate different inverter system topologies. (08 Marks)

### Module-3

- 5 a. Obtain the basic mathematical model of three phase four wire inverter with a split DC bus. (08 Marks)
- b. Write a note on Robust servo mechanism voltage controller and list out four conditions to obtain solution to RSC. (08 Marks)

OR

- 6 a. Obtain the per unit one dimensional equivalent model of the three phase inverter system and write the system equation in state space. (08 Marks)
- b. Obtain the output voltage waveform of space vector PWM in terms of base vectors assuming normalized DC bus voltage for Y connected load. (08 Marks)

### Module-4

- 7 a. Write a note on stationary  $\alpha\beta 0$  reference frame versus ABC reference frame. (08 Marks)
- b. Briefly explain the generalized uncertainty in robust stability analysis. (08 Marks)

OR

- 8 a. Write a note on real and reactive power control problem in DG–grid connected mode. (08 Marks)
- b. Explain the impact of V and  $\delta$ (Delta) variations on P and Q. (08 Marks)

### Module-5

- 9 a. List out the necessary steps to obtain the closed loop plant model. (08 Marks)
- b. Write a note on Robust stability analysis using structured singular value  $\mu$ . (08 Marks)

OR

- 10 a. Explain the control system of conventional PWM rectifier with feed forward load power. (08 Marks)
- b. Analyse the three phase AC – DC – AC system topology. (08 Marks)

\*\*\*\*\*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.