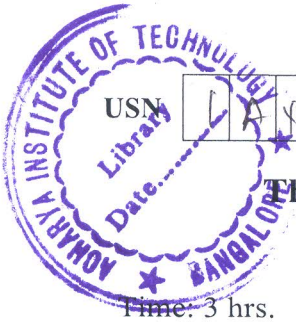


# CBCS SCHEME

15EC34



## Third Semester B.E. Degree Examination, Jan./Feb.2021 Network Analysis

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Define the terms with an example,
  - (i) Linear and non linear elements.
  - (ii) Lumped and distributed elements.
  - (iii) Unilateral and Bilateral elements.
  - (iv) Active and Passive elements.

(08 Marks)
- b. Find the current in  $28\ \Omega$  resistor using mesh analysis in Fig. Q1 (b).
 

(08 Marks)

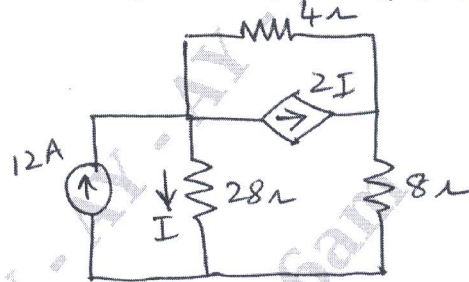


Fig. Q1 (b)

OR

- 2 a. Reduce the network in Fig. Q2 (a) to a single voltage source in series with a resistance using source shift and source transformation.

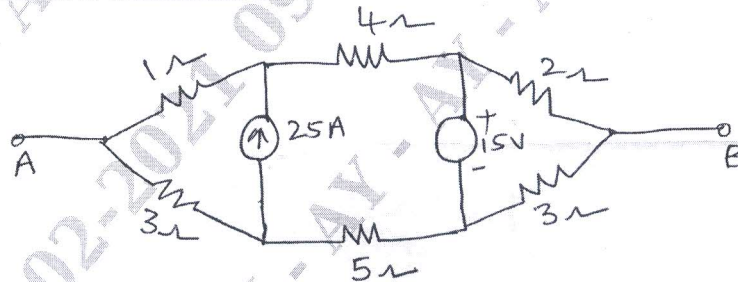


Fig. Q2 (a)

- b. The node voltage equations of a network are,
 
$$\left[ \frac{1}{5} + \frac{1}{j2} + \frac{1}{4} \right] V_1 - \frac{1}{4} V_2 = \frac{50 \angle 0^\circ}{5}$$
 and
 
$$-\frac{1}{4} V_1 + \left[ \frac{1}{4} + \frac{1}{-2j} + \frac{1}{2} \right] V_2 = \frac{50 \angle 90^\circ}{2}$$
 Derive the network.
 

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. State and prove superposition theorem. (08 Marks)  
 b. For the circuit shown in fig. Q3 (b), find the current through  $R_L$  using Thevenins theorem. (08 Marks)



Fig. Q3 (b)

OR

- 4 a. State and prove Millers theorem. (08 Marks)  
 b. Find the value of  $Z_L$  for which power transferred to the load is maximum and also determine the maximum power for the circuit shown in Fig. Q4 (b). (08 Marks)

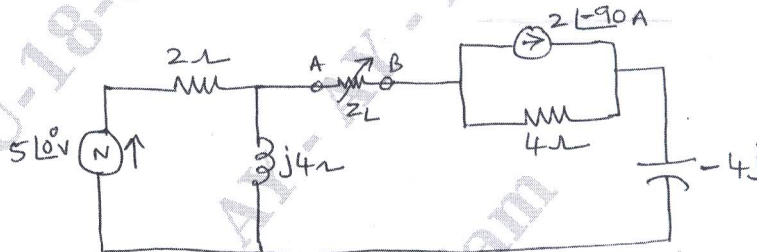


Fig. Q4 (b)

**Module-3**

- 5 a. In the circuit of Fig. Q5 (a). Switch K is opened at  $t = 0$ . Find the value of  $V$ ,  $\frac{dV}{dt}$  and  $\frac{d^2V}{dt^2}$  at  $t = 0^+$ . (08 Marks)

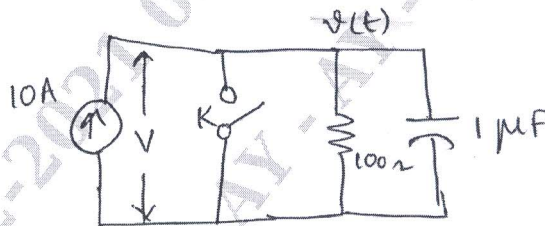


Fig. Q5 (a)

- b. Obtain the Laplace transform of the square wave shown in Fig. Q5 (b). (08 Marks)

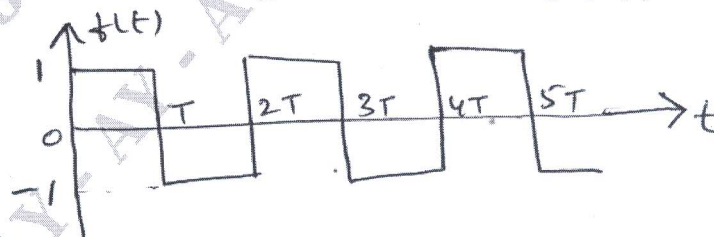


Fig. Q5 (b)

OR

- 6 a. State and prove initial value and final value theorem. (08 Marks)  
 b. For the network shown in Fig. Q6 (b) the switch is moved from position 1 to position 2 at  $t = 0$  the steady state has been reached before switching. Calculate  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . (08 Marks)

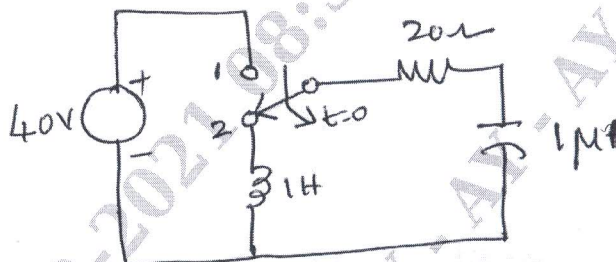


Fig. Q6 (b)

Module-4

- 7 a. Define the following terms :  
 (i) Resonance  
 (ii) Q-factor  
 (iii) Bandwidth  
 (iv) Selectivity. (04 Marks)  
 b. Derive an expression for frequency of resonance of a parallel resonant circuit containing resistance in both the branches. (06 Marks)  
 c. It is required that a series RLC circuit should resonate at 500 kHz. Determine the values of R, L and C if the bandwidth of the circuit is 10 kHz and its impedance is  $100 \Omega$  at resonance. Also find the voltages across L and C at resonance if the applied voltage is 75 volts. (06 Marks)

OR

- 8 a. Show that a two branch parallel resonant circuit is resonant at all the frequencies if  $R_L = R_C = \sqrt{\frac{L}{C}}$  where  $R_L$  = Resistance in the inductor branch,  $R_C$  = Resistance in the capacitor branch. (06 Marks)  
 b. Give the comparison between series and parallel resonance. (04 Marks)  
 c. Find the value of  $R_1$  such that the circuit given in Fig. Q8 (c) is resonant. (06 Marks)

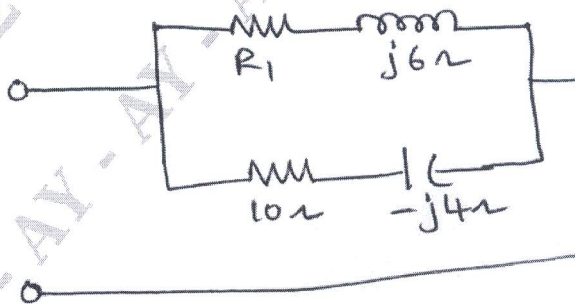


Fig. Q8 (c)

**Module-5**

- 9 a. Express Y parameters in terms of Z and T parameters. (08 Marks)  
 b. Find the transmission parameters for the network shown in Fig. Q9 (b). (08 Marks)

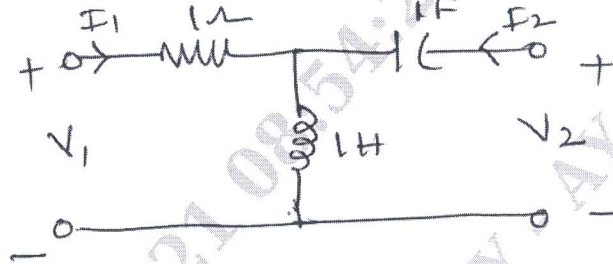


Fig. Q9 (b)

OR

- 10 a. Express ABCD parameters in terms of Y and h parameters. (08 Marks)  
 b. Find the h parameters of the network shown in Fig. Q10 (b). (08 Marks)

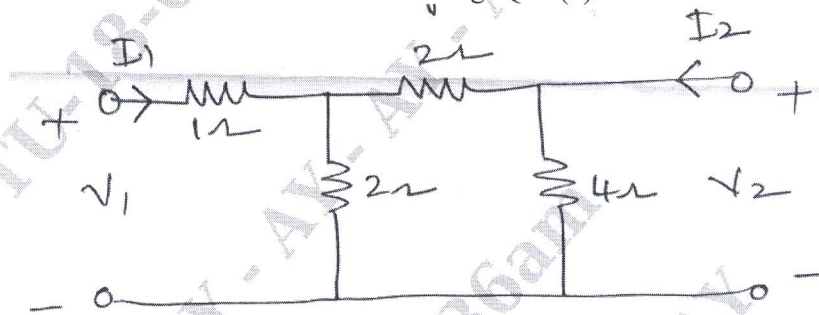


Fig. Q10 (b)

\*\*\*\*\*