

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC655

Sixth Semester B.E. Degree Examination, Jan./Feb. 2021 Microelectronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing ONE full question from each module.

Module-1

- Derive an expression for drain current of NMOS transistor operating in different regions. (08 Marks)
 - Calculate the minimum value of V_{DS} needed for a $0.8\mu\text{m}$ process technology for which $t_{ox} = 15\text{nm}$, $\mu_n = 550\text{cm}^2/\text{V.S}$.
 - Find C_{ox} , K_n^1
 - Find the over drive voltage required to operate the transistor having $(W/L) = 20$ in saturation with $I_D = 0.2\text{mA}$. (08 Marks)

OR

- Analyse the circuit in Fig.Q2(a) to determine all voltage and currents. Let :
 $V_t = 1\text{V}$, $K_n^1 \left(\frac{W}{L}\right) = 1\text{mA}/\text{v}^2$.

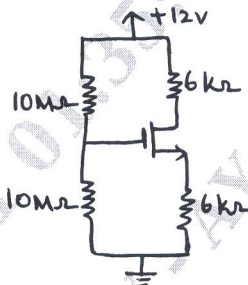


Fig.Q2(a)

- Derive an expression for resistance between drain and source from the transfer characteristics. (08 Marks)

Module-2

- Derive an expression for MOSFET transconductance using small signal operation. (08 Marks)
 - Differentiate between small signal equivalent model and T-equivalent model of MOSFET. (08 Marks)

OR

- Derive an expression for R_{in} , R_o gain for a grounded gate amplifier. Justify why it is called as current followers. (08 Marks)
 - Briefly explain all the capacitances in MOSFET and draw its high frequency model. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Compare MOSFET and BJT based on the following parameters.
 i) Current – voltage equation
 ii) Hybrid- π model
 iii) Transition frequency
 iv) Gain. (08 Marks)
- b. Draw the MOSFET constant current source and explain its operation. (04 Marks)
- c. For $V_{DD} = 3V$, $I_{ref} = 100\mu A$ design a constant current source if Q_1 and Q_2 are matched and have a channel length of $1\mu m$, channel width of $10\mu m$, $V_t = 0.7V$, $K_n^1 = 200\mu A.V^2$. (04 Marks)

OR

- 6 a. Explain MOS current steering circuits with relevant current-voltage equations. (08 Marks)
- b. Find the value of Z for the circuit shown in Fig.Q6(b) using Miller equivalent circuit when Z is : i) $1 - M\Omega$ resistance ii) $1 - pF$ capacitance.

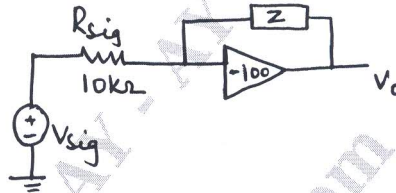


Fig.Q6(b)

(08 Marks)

Module-4

- 7 a. Derive the 3-dB frequency expression for a common source amplifier. (08 Marks)
- b. A CMOS common source amplifier has $\frac{W}{L} = \frac{7.2\mu m}{0.36\mu m}$ for all transistors,
 $\mu_n C_{ox} = 387\mu A/v^2$, $\mu_p C_{ox} = 86\mu A/v^2$, $I_{ref} = 100\mu A$, $V_A = 5V/\mu m$, $C_{gs} = 20fF$, $C_{gd} = 5fF$,
 $C_L = 25fF$, $R_{sig} = 10K\Omega$, determine F_H . (08 Marks)

OR

- 8 a. Explain an active loaded common gate amplifier and derive for its R_{in} , R_o , gain. (08 Marks)
- b. Estimate A_{vo} , R_{in} , R_o , G_v , F_H for a common gate amplifier with $\left(\frac{W}{L}\right) = \frac{7.2\mu m}{0.36\mu m}$,
 $\mu_n C_{ox} = 387\mu A/v^2$, $r_0 = 18k\Omega$, $I_D = 100\mu A$, $g_m = 1.25mA/v$, $X = 0.2$, $R_S = 10k\Omega$,
 $R_L = 100k\Omega$, $C_{gs} = 20fF$, $C_{gd} = 5fF$, $C_L = 0$. (08 Marks)

Module-5

- 9 a. Explain the MOS differential pair operation with common mode and differential input voltage. (08 Marks)
- b. Explain the effect of R_D and g_m mismatch on CMRR. (08 Marks)

OR

- 10 a. Determine the differential gain of an active loaded MOS pair. (08 Marks)
- b. With a neat circuit diagram, explain the operation of two stage CMOS opamp configuration. (08 Marks)

* * * * *