

Third Semester B.E. Degree Examination, Jan./Feb. 2021 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Define clamper circuit. Explain the positive clamper circuits with output waveforms. (05 Marks)
 - For the circuit shown, sketch the waveforms of i_R and v_o , assume S_i diodes. (07 Marks)

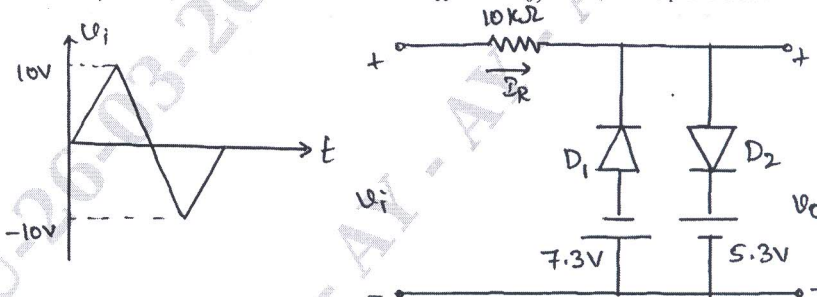


Fig. Q1 (b)

- Explain the operation of RC coupled BJT amplifier. (08 Marks)

OR

- Explain the operation of second order High pass butterworth filter and draw its frequency response. (10 Marks)
 - Design a wide band-pass filter with $f_L = 200$ Hz and $f_H = 1$ kHz and a passband gain = 4. Draw the frequency response plot and calculate the value of 'Q' for the filter. (10 Marks)

Module-2

- With a neat circuit diagram, explain wein bridge oscillator. (10 Marks)
 - Design the phase shift oscillator for frequency of oscillation, $f_0 = 200$ Hz. (05 Marks)
 - What is frequency stability? Explain its significance. (05 Marks)

OR

- Define Comparator. Explain the operation of inverting comparator. (10 Marks)
 - With the help of input and output waveforms. Explain the operation of Schmitt trigger circuit. (10 Marks)

Module-3

- Explain the operation of 555 timer as monostable multivibrator and derive the expression for pulse width. (10 Marks)
 - Design a 555 astable multivibrator for an output frequency of 1 kHz and duty cycle 60%. (10 Marks)

OR

- With a neat sketch, explain the architecture of 555 Timer. (06 Marks)
 - List out the features and applications of 555 Timer. (06 Marks)
 - Derive an expression for charging time (T_C) discharging time (T_d) frequency of oscillation and duty cycle for a astable multivibrator for 555 timer. (08 Marks)

Module-4

- 7 a. State the rules for K-map simplification. (04 Marks)
b. Simplify the following switching function using K-map:
$$F(A,B,C,D) = \sum(0, 5, 7, 8, 9, 10, 11, 14, 15) + \phi(1, 4, 13)$$
 (06 Marks)
c. Explain the working of 8×1 MUX with operation table and logic diagram using $4 : 1$ MUX. (10 Marks)

OR

- 8 a. Explain the full subtractor circuit with a truth table and logic diagram. (10 Marks)
b. What is Encoder? Realize Octal to binary Encoder using basic gates and write its truth table. (10 Marks)

Module-5

- 9 a. Explain clocked D flip-flop with the following :
(i) Logic diagram.
(ii) Truth table.
(iii) Input and Output waveform. (10 Marks)
b. Discuss BCD ripple counter using JK flip flop with state diagram, logic diagram and timing diagram. (10 Marks)

OR

- 10 a. Explain clocked JK flip flop by the following:
(i) Logic diagram.
(ii) Characteristic table.
(iii) Characteristic equation. (10 Marks)
b. Draw and explain the working of 4-bit up synchronous counter. (10 Marks)
