

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EE33

Third Semester B.E. Degree Examination, July/August 2021


## Transformers and Generators

Time: 3-hrs.

Max. Marks: 80

Note : 1. Answer any FIVE full questions.  
2. Missing data may be suitably assumed.

- 1 a. Explain the operation of a practical transformer on no – load and draw the phasor diagram. (06 Marks)  
b. Explain with diagram, the open circuit test on a Single phase transformer. (04 Marks)  
c. A single phase 500V/250V, 10 KVA, 50Hz transformer has a resistance of  $0.2\Omega$  and a reactance of  $0.6\Omega$  on H.V side. The corresponding values on the L.V side are  $0.05\Omega$  and  $0.15\Omega$  respectively. Calculate the percentage regulation on full – load at 0.7 p.f lagging and the full – load copper losses. (06 Marks)
- 2 a. Explain the delta – delta connection of three, Single phase transformers and show that V- V capacity is 57.7% of  $\Delta - \Delta$  capacity. (06 Marks)  
b. Explain the choice between star and delta connection in 3 – phase transformers. (04 Marks)  
c. The following test results were obtained for a 50kVA, 2200V/110V, 50Hz, 1 – phase transformer : O.C. test (L.V. Side) : 110V, 10A, 400W.  
S.C. test (H.V. Side) : 90V, 20.5A, 808W.  
Determine the equivalent circuit parameters referred to L.V. Side. (06 Marks)
- 3 a. What are the conditions for parallel operation of single phase and three phase transformers? (06 Marks)  
b. Two, 1 - phase transformers in parallel operation, Supply a load of impedance  $(2 + j1.5)\Omega$ . The transformer impedances as referred to the secondary windings are  $(0.15 + j0.5)\Omega$  and  $(0.1 + j0.6)\Omega$  respectively. The open circuit secondary emf's are 207V and 205V. Find  
i) The no – load circulating current ii) Total power supplied to the load. (10 Marks)
- 4 a. Derive an expression for saving in copper in a step down auto – transformer over a two winding transformer of equal rating. (05 Marks)  
b. Explain the voltage regulation in transformers by Off – circuit tap changing. (05 Marks)  
c. Draw the equivalent circuit of a tertiary winding transformer and explain the procedure to determine its parameters. (06 Marks)
- 5 a. Explain with diagram, the Sumpner's test on the transformers. (06 Marks)  
b. What is Commutation? Explain the full – load characteristics of a d.c shunt generator. (04 Marks)  
c. Define and derive the equations for Synchronous generator winding factors. (06 Marks)
- 6 a. What are the methods of Reduction and Elimination of harmonics in the generated emf? (06 Marks)  
b. What is Armature reaction in a synchronous generator? Explain its effect, with diagram at u.p.f load. (04 Marks)  
c. A three – phase , 16 pole, star connected synchronous generator has 192 slots with 8 conductors per slot. The coil span is  $160^\circ$  (ele), the speed of the generator is 375 rpm and the flux per pole is 55 mwb. Calculate the phase and line voltages. (06 Marks)

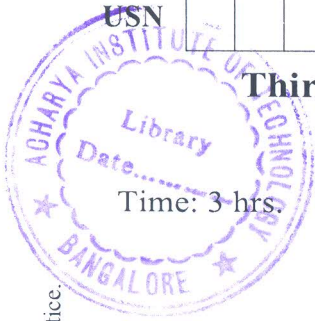

- 7 a. Define Voltage regulation of a Synchronous generator and explain its load characteristics. (05 Marks)
- b. With diagram, derive the relevant equations for load sharing between the two generators operating in parallel. (06 Marks)
- c. With load diagrams, explain the O – curves and V – curves. (05 Marks)
- 8 a. Draw the phasor diagram and derive the equation for electrical power output of a salient – pole generator. (05 Marks)
- b. With circuit diagram, explain the procedure of slip test. How can direct axis and quadrature axis reactance's found from this test? (05 Marks)
- c. A 300 MVA, 22KV, three phase salient – pole generator is operating at 250MW power output at a lagging p.f of 0.85 synchronized to 22KVbus. The generator reactances are  $X_d = 1.93\text{pu}$  and  $X_q = 1.16\text{pu}$ . Calculate the power angle and direct axis current. (06 Marks)
- 9 a. Explain the procedure to obtain the Short circuit and Open circuit characteristics and hence Synchronous reactance. (06 Marks)
- b. A 5MVA, 6.6KV, three – phase star connected Synchronous generator has a resistance of 0.075 ohm per phase. Calculate the regulation for a load of 500A at 0.71 lagging p.f, from the following characteristics :

Field current :	32	50	75	100	140
O.C line voltage :	3100	4900	6600	7500	8300
ZPFC line voltage :	0	1850	4250	5800	7000

(10 Marks)

- 10 a. Draw the capability curve of Synchronous generator. Mention the various bounds imposed on this machine. (06 Marks)
- b. With diagram, explain the control of Synchronous generators after Synchronizing. (05 Marks)
- c. What is Hunting? What are the techniques used to reduce hunting? (05 Marks)

\*\*\*\*\*