



- 6 a. Sketch the circuit diagram and frequency response of a first order high pass filter. Explain its operation and design procedure. (06 Marks)
- b. With a neat circuit diagram, explain the operation of a single stage band pass filter, and design procedure. (08 Marks)
- c. With a block diagram, explain the operation of band stop filter constructed using low pass and high pass filters, also draw the frequency response. (06 Marks)
- 7 a. List the various features of universal active filter FLT-U2. (04 Marks)
- b. Explain the operation of switched capacitor filter and draw the input output waveforms. (08 Marks)
- c. With a block diagram, explain the operation of Phase Locked Loop. Write four applications of phase locked loop. (08 Marks)
- 8 a. With a neat circuit diagram, explain the operation of a precision voltage regulator. (06 Marks)
- b. A dc voltage follower regulator has  $V_S = V_{CC} = 12\text{ V}$ ,  $V_0 = 6.3\text{ V}$ ,  $R_1 = 270\ \Omega$  and  $I_{L(\max)} = 42\text{ mA}$ . If the supply source resistance is  $25\ \Omega$ . Determine the line regulation, load regulation and ripple rejection for the circuit. The Zener diode used is 1N753,  $Z_z = 7\ \Omega$ . (06 Marks)
- c. Mention the salient features of 723 regulator. Show how a 723 regulator can be used as a positive and negative voltage regulator and explain the circuit operation. (08 Marks)

\* \* \* \* \*