 


# CBCS SCHEME



17EC33

## Third Semester B.E. Degree Examination, July/August 2021 Analog Electronics

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions.**

1.
  - a. Mention the steps involved for obtaining the AC equivalent of a transistor network. (04 Marks)
  - b. Derive an expressions for input impedance, output impedance and voltage gain for CE fixed bias configuration using  $r_e$  equivalent model. (08 Marks)
  - c. Define hybrid parameters and explain hybrid  $\pi$  model with neat sketch. (08 Marks)
2.
  - a. Draw the circuit diagrams, for transistor  $r_e$  model in common Emitter and common base configuration. (04 Marks)
  - b. Derive expressions for  $Z_i$ ,  $Z_o$ ,  $A_v$  and  $A_i$  for emitter follower configuration using approximate hybrid equivalent model. (08 Marks)
  - c. For the network shown in Fig.Q2(c), without  $C_E$ (unbypassed), determine  $r_e$ ,  $Z_i$ ,  $Z_o$  and  $A_v$ .

 


Fig.Q2(c)

(08 Marks)

3.
  - a. Mention the differences between JFET and MOSFET. (04 Marks)
  - b. Explain with neat sketches operation and characteristics of n-channel enhancement MOSFET. (08 Marks)
  - c. Find  $r_d$ ,  $Z_i$ ,  $Z_o$ , and  $A_v$  for the circuit shown in Fig.Q3(c).

 


Fig.Q3(c)

(08 Marks)

4.
  - a. Sketch the following circuit diagrams :
    - i) JFET AC equivalent model of source follower
    - ii) Cascaded FET amplifier. (04 Marks)
  - b. Derive an expressions for  $Z_i$ ,  $Z_o$ , and  $A_v$  using small signal JFET amplifier for self bias configuration (Bypassed  $R_s$ ). (08 Marks)
  - c. For the source follower network shown in Fig.Q4(c), determine : i)  $r_d$  ii)  $Z_i$  iii)  $Z_o$  iv)  $A_v$ .

 


Fig.Q4(c)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 5 a. An amplifier rated at a 40W output is connected to a  $10\ \Omega$  speaker find :  
 i) Input power required for full output if power gain is 25dB  
 ii) Input voltage for rated output if the amplifier voltage gain is 40dB. (06 Marks)  
 b. Explain high frequency response of JEFT amplifiers. (08 Marks)  
 c. Explain multistage frequency effects. (06 Marks)
- 6 a. Derive an expressions for Miller input and output capacitors. (06 Marks)  
 b. Determine  $r_e$ ,  $A_V$  and  $R_i$  for the low frequency response of BJT amplifier circuit shown in Fig.Q6(b). Assume  $r_0 = \infty$ .

 


Fig.Q6(b)

(08 Marks)

- c. Draw the circuit diagram of :  
 i) High frequency response of BJT amplifier in CE mode with capacitances effects  
 ii) Low frequency response of FET amplifier in common source mode with capacitive elements effects. (06 Marks)
- 7 a. List the conditions for sustained oscillations. (04 Marks)  
 b. Explain with neat circuit diagram, series resonant crystal oscillator using BJT. (08 Marks)  
 c. Design the RC elements of a Wein bridge oscillator for the operation at  $f = 10\text{KHz}$  and draw the oscillator circuit using op-Amp. (08 Marks)
- 8 a. Explain effect of negative feedback on gain and Bandwidth. (05 Marks)  
 b. Explain with neat circuit diagram, the operation of BJT Colpitt oscillator and mention its advantages over Hartely oscillator. (08 Marks)  
 c. Explain UJT relaxation oscillator with necessary equations and waveforms. (07 Marks)
- 9 a. Classify the power amplifiers and define them with necessary waveforms and 'Q' point. (06 Marks)  
 b. Explain series transistor voltage regulator with neat diagram. (06 Marks)  
 c. Calculate input power, output power and efficiency of the series fed class A power amplifier circuit shown in Fig.Q9(c).

 


Fig.Q9(c)

(08 Marks)

- 10 a. Define : i) Cross over distortion ii) percentage voltage regulation iii) amplifier efficiency  
 iv) harmonic distortion v) voltage regulator. (10 Marks)  
 b. Explain transformer coupled class A power amplifier with necessary equations. (06 Marks)  
 c. For class 'B' amplifier using a supply of  $V_{CC} = 30\text{V}$  and driving a load of  $16\ \Omega$ , determine maximum input power and output power. (04 Marks)

\*\*\*\*\*