

CBCS SCHEME

18MT35

USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, July/August 2021

Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1 a. With neat circuit diagrams and waveforms, explain the operation of positive and negative clippers with and without reference voltage. (10 Marks)
b. With neat circuit diagram and waveforms explain the operation of positive and negative clampers with and without reference voltage. (10 Marks)
- 2 a. Design a second order high pass Butterworth filter with a cutoff frequency 1kHz and draw the frequency response plot of the filter. (10 Marks)
b. Explain about wide band pass and narrow band reject with neat circuit diagram and waveform. (10 Marks)
- 3 a. Explain the oscillator principle and working of RC phase shift oscillator with neat diagram. (10 Marks)
b. With a neat diagram, explain Wien bridge oscillator. (06 Marks)
c. Design a Wien bridge oscillator so that $f_0 = 965\text{Hz}$. (04 Marks)
- 4 a. Explain the operation of non-inverting comparator and a circuit which converts sine wave to square wave with neat diagrams and waveforms. (10 Marks)
b. Explain the operation of a circuit which converts an irregular-shaped waveforms into a square wave or pulse with neat circuit, input and output waveforms. (10 Marks)
- 5 a. With neat diagrams, explain pin diagram and internal architecture of 555 timer. (10 Marks)
b. With neat circuit diagram, explain the operation of 555 timer as a monostable multivibrator. (10 Marks)
- 6 a. Explain the operation of 555 timer as a astable multivibrator with input and output waveforms. Derive the expressions for charging and discharging time. (10 Marks)
b. With neat circuit and waveform explain square wave oscillator and free running ramp generator. (10 Marks)
- 7 a. Simplify the following Boolean equations using k-maps:
i) $F = \overline{A}BD + \overline{A}BC\overline{D} + \overline{A}BD + \overline{A}BC\overline{D} + ABC\overline{D} + ABC + A\overline{B}CD$
ii) $F(ABCD) = \sum M(1, 2, 3, 5, 6, 7, 8, 11, 13, 15)$ (06 Marks)
b. Explain full subtractor with truth table and implement them using logic gates. (04 Marks)
c. Explain a full adder circuit using truth table, logic diagram and design full adder using two half adders. (10 Marks)
- 8 a. Explain the operation of demultiplexer using truth table and logic diagram. (06 Marks)
b. Implement the following Boolean equation with a multiplexer considering A as input.
 $F(ABCD) = \sum(0, 1, 3, 4, 8, 9, 15)$. (08 Marks)
c. Explain the operation of octal to binary encoder with truth table and logic diagram. (06 Marks)
- 9 a. Explain D-flipflop and T-flipflop with neat diagrams and truth table, timing diagrams. (10 Marks)
b. Explain race-around condition in J-K flip flop. Also explain working of master slave J-K flip flop. (10 Marks)
- 10 a. Explain modulo 16-ripple down counter using schematic, timing and state diagram. (10 Marks)
b. Design a synchronous up-down counter with neat diagram. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.