

Third Semester B.E. Degree Examination, July/August 2022 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the working principal of photodiode and discuss its applications. (08 Marks)
- b. Design a monostable multivibrator circuit using 555 Timer IC to generate an output pulse of 100 ms. Choose $C = 0.47 \mu\text{F}$. Draw the circuit. (06 Marks)
- c. Give the typical application of A/D and D/A converters with a block diagram. (06 Marks)

OR

- 2 a. Obtain the expression for collector to emitter voltage for voltage divider bias of BJT using accurate analysis. (08 Marks)
- b. Design and draw astable multivibrator circuit using 555 Timer IC to generate 1 kHz square wave (Duty cycle = 50 %). Assume $C = 0.1 \mu\text{F}$. (06 Marks)
- c. Explain R-2R ladder type DAC with a neat diagram. (06 Marks)

Module-2

- 3 a. Define prime implicant and essential prime implicant. Give an example. (04 Marks)
- b. Use a Karnaugh map to find the minimum sum-of-products form for,

$$F(A, B, C, D) = \sum m(0, 2, 4, 10, 11, 14, 15) + \sum d(6, 7)$$
 (06 Marks)
- c. Find a minimum sum-of-products solution using the Quine-McClusky method for given function,

$$f(w, x, y, z) = \sum m(1, 3, 6, 7, 8, 9, 10, 12, 13, 14)$$
 (10 Marks)

OR

- 4 a. Obtain the minimum product of sums for $f(w, x, y, z) = \bar{x}\bar{z} + wyz + \bar{w}\bar{y}\bar{z} + \bar{x}y$ using Karnaugh map. (08 Marks)
- b. Find all prime implicants of the given function $F = \sum m(0, 1, 2, 5, 6, 7)$, and find all minimal solutions using Petrick's method. (08 Marks)
- c. Explain simplification of logic functions using map-entered variables. (04 Marks)

Module-3

- 5 a. Realize the given function $f = \bar{b}\bar{c} + ab + \bar{a}b$ using only two-input NAND gates. (06 Marks)
- b. Discuss different types of hazards in combinational logic circuits. (06 Marks)
- c. What is Programmable Array Logic (PAL)? Show the implementation of a full adder using a PAL. (08 Marks)

OR

- 6 a. What is a multiplexer? Write the logic diagram for 8 : 1 multiplexer using 4 input AND and OR gates. (08 Marks)
- b. Discuss the four kinds of three state buffers. (08 Marks)
- c. Explain programmable logic array structure. (04 Marks)

Module-4

- 7 a. What is VHDL? Show how to model the 4-to-1 multiplexer using a VHDL conditional assignment statement. (06 Marks)
- b. Derive the characteristic equation for S-R flip-flop and J-K flip-flop in product-of-sums form. (06 Marks)
- c. What is D flip-flop? Illustrate the operation of the clear and preset inputs in D-flip-flop with timing diagram. (08 Marks)

OR

- 8 a. Show how to construct a VHDL module using an entity architecture pair. (06 Marks)
- b. Explain switch debouncing with an S-R latch. (06 Marks)
- c. What is T flip-flop? Show how to convert D-flip-flop into T-flip-flop. (08 Marks)

Module-5

- 9 a. What is a register? Build a parallel adder with an accumulator using registers. (06 Marks)
- b. Design 3-bit synchronous counter using T-flip-flops. (08 Marks)
- c. Design a sequential parity checker for serial data. (06 Marks)

OR

- 10 a. Explain the working of a 3 bit shift register. (06 Marks)
- b. Distinguish ring counter and Johnson counter. Also give the general form of a shift register counter. (06 Marks)
- c. Design 3-bit binary synchronous down counter using J-K flip-flops. (08 Marks)
