

USN

--	--	--	--	--	--	--	--	--	--

15EE35

Third Semester B.E. Degree Examination, July/August 2022 Digital System Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define combinational logic. List out the various steps in designing a combinational logic circuit. (04 Marks)
- b. Distinguish prime implicate and essential prime implicate. Determine the same of the function using K-maps $f(w, x, y, z) = \Sigma_m(0, 2, 5, 7, 8, 10, 13, 15)$. Hence the minimal sum expression. (08 Marks)
- c. Design a logic circuit with inputs A, B and C so that output Y is high, whenever A is zero or whenever $B = C = 1$ using only two input NAND gates. (04 Marks)

OR

- 2 a. Obtain minimal product of the Boolean function using VEM technique
 $X = f(a, b, c) = \Sigma_m(0, 1, 4, 5, 7)$. (04 Marks)
- b. Simplify the function using K-maps
 $T = f(a, b, c, d) = \Sigma_m(1, 3, 4, 5, 13, 15) + \Sigma_d(8, 9, 10, 11)$. (04 Marks)
- c. Simplify the function using Quine McCluskey techniques and realize the simplified function using NOR gates
 $f(a, b, c, d) = \Sigma_m = (7, 9, 12, 13, 14, 15) + \Sigma_d(4, 11)$. (08 Marks)

Module-2

- 3 a. Design a combinational circuit to convert BCD number to Excess-3 BCD number as following:
 - i) Construct the truth table
 - ii) Simplify each output function and write the reduced equation
 - iii) Draw a logic diagram. (10 Marks)
- b. Design a 4 to 16 line decoder using 2 to 4 line decoder with active low enable and active low outputs. (06 Marks)

OR

- 4 a. Design a binary full adder using minimum member of NAND gates. Write its truth tables. (06 Marks)
- b. What is lookahead carry adder? Derive an expression for C_{out} for a four stage lookahead carry adder. (06 Marks)
- c. Implement the Boolean function using 4:1 multiplexer
 $Y = f(x, y, z) = \Sigma_m(1, 3, 5, 6)$. (04 Marks)

Module-3

- 5 a. Differentiate sequential logic circuit and the combinational logic circuit. (04 Marks)
- b. Explain with timing diagram, the working operation of SR Latch as a switch debouncer. (06 Marks)
- c. Obtain the characteristic equation of JK and D flipflops. (06 Marks)

OR

- 6 a. With the help of logic diagram, explain the following with respect to the shift register
 i) Parallel in and serial out
 ii) Ring counter and twisted ring counter. (08 Marks)
- b. Design of a synchronous Mod – 6 counter using D – flipflops to count that sequence 0, 2, 3, 6, 5, 1, 0, . . . used as state diagram. (08 Marks)

Module-4

- 7 a. With a suitable block diagram, explain the Mealy and Moore model, in a sequential circuit analysis. (06 Marks)
- b. Analysis the following sequential circuit shown in Fig.Q7(b) and obtain
 i) FlipFlop input and output equation
 ii) Transition equation and table
 iii) State stable
 iv) Draw a state diagram.

 


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Write a note on construction of the state diagram with sequence detector. (08 Marks)
- b. Draw the state diagram of Mealy machine whose output is 1, if the last three inputs were 010 assuming that the sequence could overlap. (08 Marks)

Module-5

- 9 a. Explain the structure of the VHDL modules with an examples. (06 Marks)
- b. Compare VHDL module and verilog module. (04 Marks)
- c. Mention the types of HDL description. Explain how a half adder can be modeled in VHDL in any one of the description method. (06 Marks)

OR

- 10 a. Explain the execution of signal assignment statements in HDL. (06 Marks)
- b. List the data types used in VHDL and Verilog. (04 Marks)
- c. Write verilog code for 2×1 multiplexer with an active low enable inputs. (06 Marks)
