

USN

--	--	--	--	--	--	--	--	--	--

15EE34

Third Semester B.E. Degree Examination, July/August 2022
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Explain the fixed bias circuit with load line analysis. (08 Marks)
 - Write the procedure for analyzing the clamper circuit. Determine the output voltage for the network shown in Fig.Q1(b). Assume $f = 1\text{KHz}$ and ideal diode.

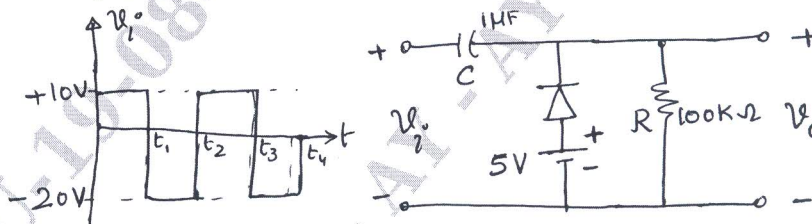


Fig.Q1(b)

(08 Marks)

OR

- Explain the operation of transistor as switch along with suitable circuit and necessary waveforms. (08 Marks)
 - For the circuit shown in Fig.Q2(b), $I_C = 2\text{mA}$, $\beta = 100$. Calculate R_E , V_{CE} and S_{ICO} . Assume S_i transistor.

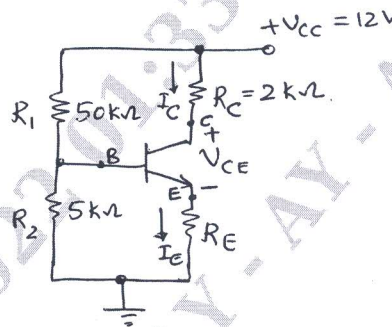


Fig.Q2(b)

(08 Marks)

Module-2

- Derive the expressions for A_i , A_v , R_i and R_o for CE amplifier using h-parameter model. (08 Marks)
 - For the emitter follower circuit shown in Fig.Q3(b). Calculate Z_i , Z_o , A_v and A_i .
Take : $h_{ie} = 1.1\text{K}\Omega$; $h_{re} = 2.5 \times 10^{-4}$; $h_{fe} = 50$; $h_{oe} = 24\mu\text{A/v}$.

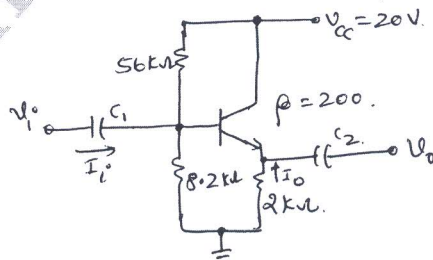


Fig.Q3(b)

(08 Marks)

OR

- 4 a. Starting from fundamentals, define h – parameters and obtain are h – parameter equivalent circuit of common emitter configuration. (08 Marks)
- b. Prove that Miller effect input capacitance, $C_{mi} = (1 - A_v)C_f$ and output capacitance, $C_{Mo} = \left(1 - \frac{1}{A_v}\right)C_f$, where A_v and C_f have their usual meanings. (08 Marks)

Module-3

- 5 a. Derive the expression for input and output impedances for feedback amplifier employing voltage series feedback. (08 Marks)
- b. Obtain an expression for voltage gain, input impedance and output impedance of a Darlington emitter follower. (08 Marks)

OR

- 6 a. With block diagram, explain the concept of different types of feedback connection. (08 Marks)
- b. If an amplifier has mid-based voltage gain of 1000 with $f_L = 50\text{Hz}$ and $f_H = 50\text{KHz}$, if 5% feedback is applied then calculate f_L and f_H with feedback. (05 Marks)
- c. A given amplifier arrangement has the following voltage gains, $A_{v_1} = 10$, $A_{v_2} = 20$ and $A_{v_3} = 40$. Calculate the overall voltage gain in dB. (03 Marks)

Module-4

- 7 a. Explain the operation of class B push – pull amplifier and derive its conversion efficiency. (10 Marks)
- b. The following distortion reading are available for a power amplifier : $D_2 = 0.2$, $D_3 = 0.02$, $D_4 = 0.06$ with $I_1 = 3.3\text{A}$ and $R_C = 4\Omega$. Calculate THD, fundamental power component and total power. (06 Marks)

OR

- 8 a. Obtain an expression for frequency of oscillation in Colpitt's oscillator. (10 Marks)
- b. With circuit diagram, explain the working principle of crystal oscillator in series resonant mode. (06 Marks)

Module-5

- 9 a. With the help of neat diagram, explain the construction, working of characteristics of n – channel JFET. (10 Marks)
- b. For the circuit shown in Fig.Q9(b). Calculate : I_D , V_{GS} , V_G , V_{DS} and V_S .

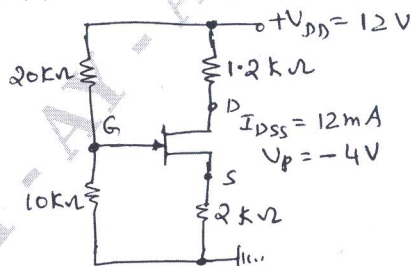


Fig.Q9(b)

(06 Marks)

OR

- 10 a. With the help of neat diagrams, explain the construction, working and characteristics of n-channel DMOSFET. (10 Marks)
- b. Differentiate between BJT and FET. (06 Marks)
