

**Third Semester B.E. Degree Examination, July/August 2022**  
**Electric Circuit Analysis**

Time: 3 hrs.

Max. Marks: 100

**Note:** Answer any **FIVE** full questions, choosing **ONE** full question from each module.

**Module-1**

- 1 a. Find the Voltage across resistance  $R$  in the network Fig. Q1(a) by Mesh analysis. (08 Marks)


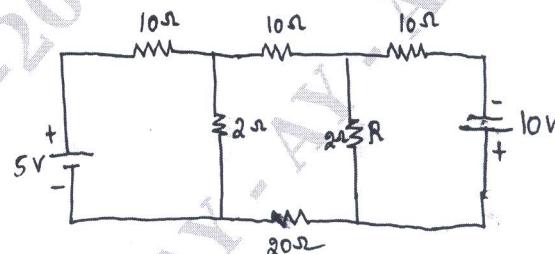


Fig. Q1(a)

- b. Find the current in the  $10\Omega$  resistor in the given network shown in Fig. Q1(b) by using Star – delta transformation. (06 Marks)

Fig. Q1(b)

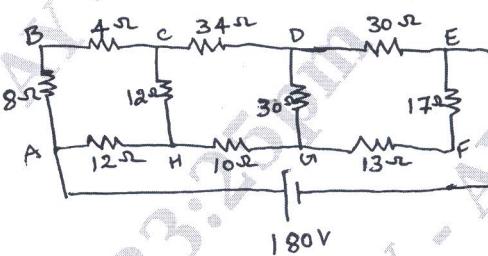

- c. Distinguish between : i) Active and Passive Elements      ii) Ideal and Practical sources  
iii) Lumped and distributed network. (06 Marks)

**OR**

- 2 a. Use source shifting and transformation techniques to find voltage across  $2\Omega$  resistor show in Fig. Q2(a). (08 Marks)

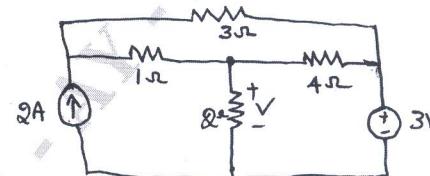


Fig. Q2(a)

- b. Use the nodal analysis to find  $V_o$  in the network shown in Fig. Q2(b). (06 Marks)

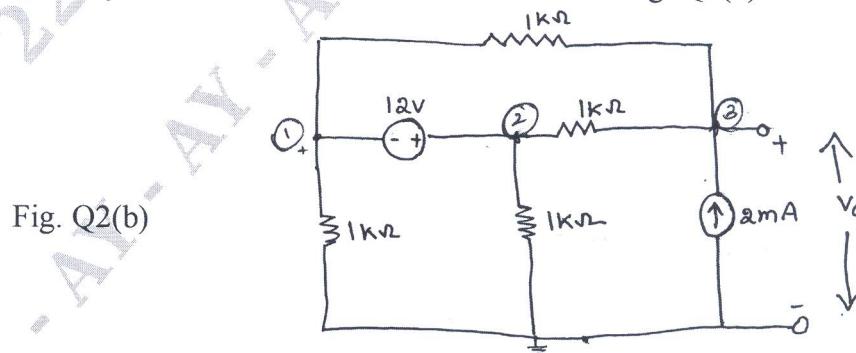


Fig. Q2(b)

- c. Determine the current  $I_o$  in the circuit of Fig. Q2(c) using Mesh analysis.

(06 Marks)

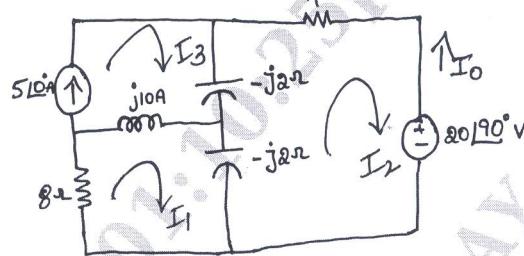


Fig. Q2(c)


**Module-2**

- 3 a. State and explain Super Position theorem with example.  
b. Verify the Reciprocity theorem for current  $I$  in the network given in Fig. Q3(b).

(08 Marks)

(06 Marks)

Fig. Q3(b)

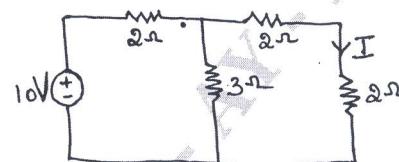


- c. State and explain Thevenin's theorem. (06 Marks)

**OR**

- 4 a. Find the current  $i$  using Super Position theorem for the Fig. Q4(a).

(10 Marks)

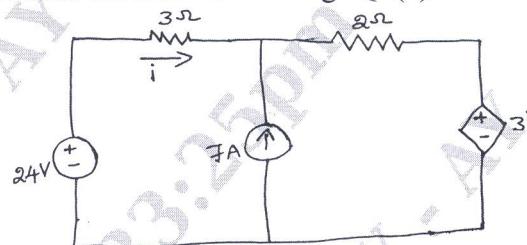

- b. State and prove Millman's theorem. (10 Marks)

**Module-3**

- 5 a. Derive the expression for resonant frequency and quality factor ( $Q_s$ ). Write expression for  $W_1$  and  $W_2$  and show that  $\sqrt{W_1 * W_2} = W_0$ .  
b. An RLC series circuit has resistance of  $10\Omega$ , a capacitance of  $100\mu F$  and a variable inductance.  
i) Find the value of inductance for which, the voltage across resistance is maximum  
ii) Q factor.  
iii) Voltage drops across R, L and C. The applied voltage is  $230V$ ,  $50Hz$ .  
c. What are initial conditions and their use in Network Analysis? (04 Marks)

**OR**

- 6 a. What is Resonance? Derive expression for cut – off frequencies.  
b. In the Fig. Q6(b), the switch S is closed at  $t = 0$ , find the time when the current from the battery reaches to  $500mA$ . (10 Marks)

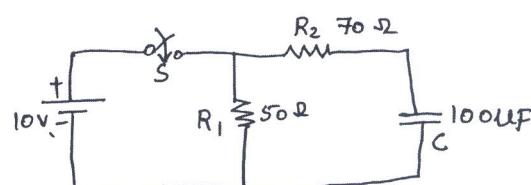
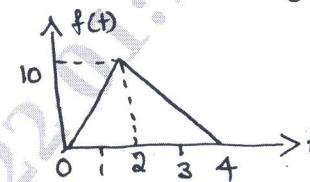


Fig. Q6(b)

**Module-4**

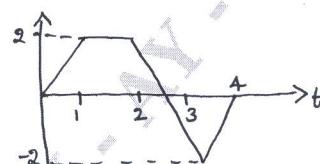
- 7 a. State and prove initial value theorem and Final Value theorem. (08 Marks)  
 b. Obtain the Laplace transform of :  
   i) Unit step functions  $f(t) = u(t)$    ii)  $f(t) = \sin wt$    iii)  $f(t) = \sin h wt$ . (06 Marks)  
 c. Obtain the Laplace transform of the function shown in Fig. Q7(c). (06 Marks)

Fig. Q7(c)

**OR**


- 8 a. Find the Laplace transform of i)  $f(t) = te^{-3t} u(t)$    ii)  $5 + 4e^{-2t}$    iii)  $e^{-at} \sin wt$   
   iv)  $t \cos at$ . (10 Marks)  
 b. Find the Laplace transform for the waveform shown in Fig. Q8(b). (10 Marks)

Fig. Q8(b)

**Module-5**

- 9 a. Find the reading on the Wattmeter in Fig. Q9(a). When the circuit is connected to a 400V , 3 -  $\phi$  supply. The phase sequence is RYB. Neglect Wattmeter losses. (10 Marks)

Fig. Q9(a)

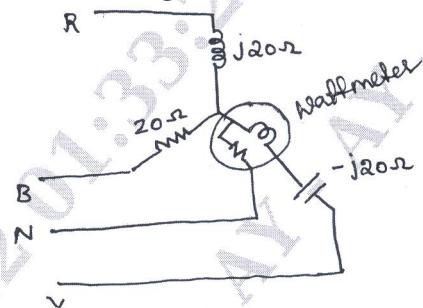


- b. Find Z parameters of the network shown in Fig. Q9(b). (10 Marks)

Fig. Q9(b)

**OR**

- 10 a. Define Y and Z parameters. Derive relation between Z and Y parameters. (10 Marks)  
 b. Find Y parameters for the network shown in Fig. Q10(b). (10 Marks)

Fig. Q10(b)

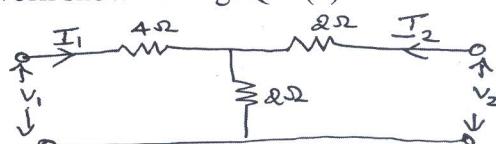

\*\*\*\*\*