



# CBCS SCHEME

USN [ ] [ ] [ ] [ ] [ ] [ ] [ ] [ ] [ ] [ ]

17EC32

**Third Semester B.E. Degree Examination, Jan./Feb. 2023**

## **Electronic Instrumentation**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Define the following terms : i) Accuracy and precision ii) Gross error and systemic error. (06 Marks)  
b. Draw the block diagram of a true RMS volt meter and explain its operation. (07 Marks)  
c. A voltmeter is calibrated to read from 100V to 200V. Its accuracy is specified within  $\pm 2\%$ . Find the max error. (07 Marks)

**OR**

- 2 a. State different types of thermocouple used for RF current measurement and explain each one of them in brief. (10 Marks)  
b. Sketch and explain the operation of a multirange Ammeter and Aryton shunt. (10 Marks)

### Module-2

- 3 a. Describe with a diagram the operation of successive approximation type DVM. (10 Marks)  
b. Explain with a diagram the working of digital pH meter and its applications. (10 Marks)

**OR**

- 4 a. Describe with the help of a diagram the operation of universal counter. (10 Marks)  
b. With the block diagram, explain the digital frequency meter. (10 Marks)

### Module-3

- 5 a. Draw the basic block diagram of an oscilloscope and explain the function of each block. (10 Marks)  
b. Sketch the block diagram and explain AF sine and square wave generator. (10 Marks)

**OR**

- 6 a. Explain with a block diagram of function generator in detail. (10 Marks)  
b. Explain the operation of digital storage oscilloscope with a help of block diagram. (10 Marks)

### Module-4

- 7 a. Explain with a help of neat diagram. Construction and principle of operation of Megger. (10 Marks)  
b. Draw the Maxwell's bridge to determine inductance in terms of known capacitance and define Q - factor and expression for inductance. (10 Marks)

**OR**

- 8 a. With neat diagram, explain the working of Wien's bridge. (10 Marks)  
b. Explain susceptance method of Q-measurement. (10 Marks)

### Module-5

- 9 a. What is transducer? Explain working of resistive position transducer with a neat sketch. (10 Marks)  
b. What are the different types of photoelectric transducer? Explain photo voltaic transducer. (10 Marks)

**OR**

- 10 a. With a neat sketch, explain construction and working of LVDT. (10 Marks)  
b. What is gauge factor? Derive an expression for gauge factor and prove that  $k = 1 + 2\mu$ . (10 Marks)

\*\*\*\*\*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg,  $42+8=50$ , will be treated as malpractice.