

# CBCS SCHEME

USN: 

--	--	--	--	--	--	--	--	--	--

Date: \_\_\_\_\_

**Third Semester B.E. Degree Examination, Jan./Feb. 2023**

**Network Analysis**

Time: 3 hrs. Max. Marks: 100

17EC35

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. What is dependent sources? Draw the symbolic representation of all four dependent sources. (04 Marks)
- b. Reduce the network shown in Fig.Q.1(b) into a single voltage source with series resistance between A and B. (08 Marks)

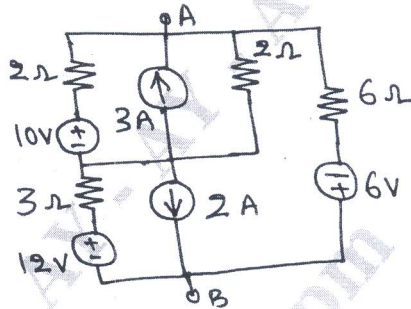


Fig.Q.1(b)

- c. Using Mesh analysis, calculate the current  $I_1$  shown in Fig.Q.1(c). (08 Marks)

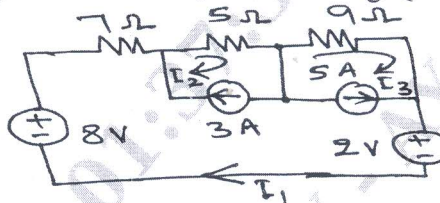


Fig.Q.1(c)

OR

- 2 a. With the help of example, explain the concept of super node. (04 Marks)
- b. Derive the expressions for converting star to delta transformation. (08 Marks)
- c. Determine the current through the branch AB of the network shown in Fig.Q.2(c). (08 Marks)

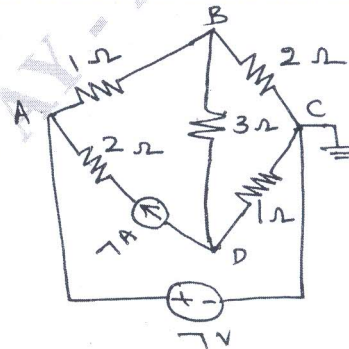


Fig.Q.2(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. State the Reciprocity and Norton's theorem. (04 Marks)  
 b. Using superposition theorem, find  $I_x$  for the circuit shown in Fig.Q.3(b). (08 Marks)

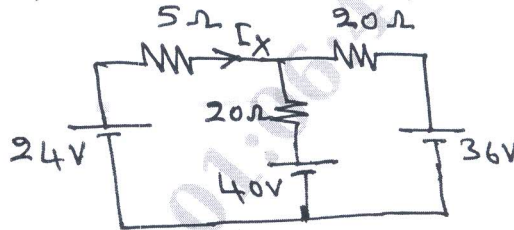


Fig.Q.3(b)

- c. Obtain the Thevenin's equivalent circuit across the terminal AB of the network shown in Fig.Q.3(c). (08 Marks)

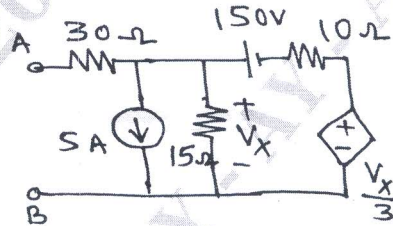


Fig.Q.3(c)

**OR**

- 4 a. State superposition theorem and mention the steps to be followed for solving the problems. (04 Marks)  
 b. Prove that  $P_{max} = \frac{|V_{th}|^2}{8R_{th}}$  for maximum power transfer of a ac circuits. (08 Marks)  
 c. Verify Reciprocity Theorem for the circuit shown in Fig.Q.4(c). (08 Marks)

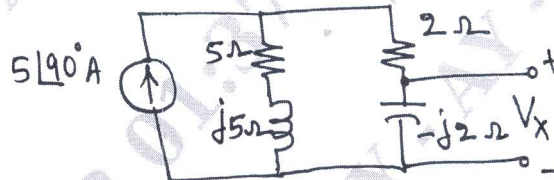


Fig.Q.4(c)

**Module-3**

- 5 a. Draw the behavior representation of inductor and capacitor at  $t = 0$ ,  $t = 0^+$  and at  $t = \infty$ . (04 Marks)  
 b. For the network shown in Fig.Q.5(b), the switch 's' is closed at  $t = 0$ , determine  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . (08 Marks)

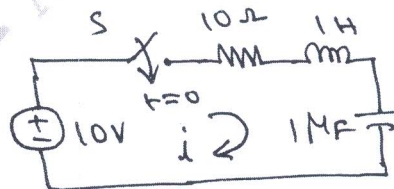


Fig.Q.5(b)

- c. Find the Laplace transform of the waveform shown in Fig.Q.5(c).

(08.Marks)

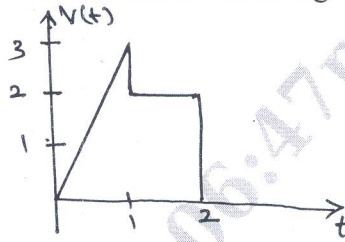


Fig.Q.5(c)

OR

- 6 a. What is the need for evaluating initial conditions and also write the procedure for evaluating initial conditions. (04.Marks)
- b. For the network shown in Fig.Q.6(b), a steady state is reached with the switch 'K' open. At  $t = 0$  the switch is closed. Determine the value of  $V_x(0^+)$  and  $V_x(0^-)$ . (08.Marks)

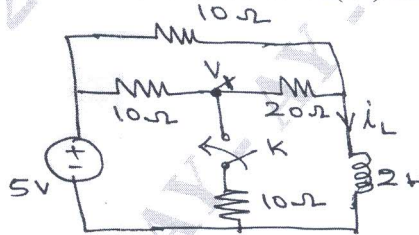


Fig.Q.6(b)

- c. Find the Laplace transform of the periodic signal  $x(t)$  shown in Fig.Q.6(c).

(08.Marks)

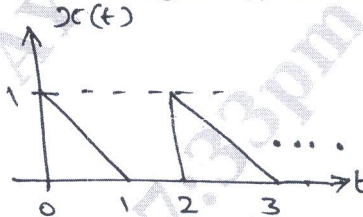


Fig.Q.6(c)

**Module-4**

- 7 a. Compare series and parallel resonance circuit. (04 Marks)
- b. Starting from the fundamentals, show that Bandwidth  $f_2 - f_1 = \frac{R}{2\pi L}$  of a series resonance circuit. (08 Marks)
- c. A coil of  $R = 10\Omega$  and  $L = 0.5H$  is connected in series with a capacitor. The current is maximum when  $f = 50Hz$ . A second capacitor is connected in parallel, with this circuit. What capacitances must it have so that the combination acts like a non-reactive circuit at 100Hz. Calculate the total current supplied in each case if the applied voltage is 220V. (08 Marks)

OR

- 8 a. What is the need for resonance circuits and mention its applications. (04.Marks)
- b. Derive the expression of resonance frequency for the circuit shown in Fig.Q.8(b). (08.Marks)

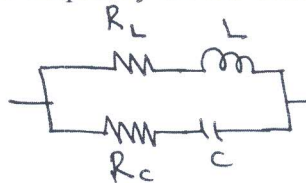


Fig.Q.8(b)



- c. Determine the RLC parallel circuit parameters whose response curve is shown in Fig.Q.8(c). What are the new values of  $W_r$  and Bandwidth if 'C' is increases to 4 times? (08 Marks)

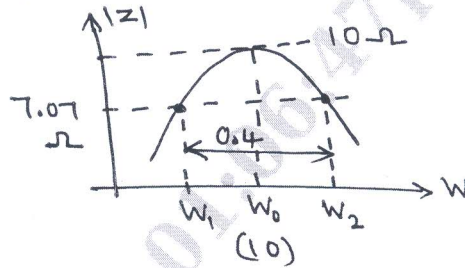


Fig.Q.8(c)

**Module-5**

- 9 a. Write the basic voltage equations of impedance parameter and also define all four parameters of Z. (04 Marks)  
 b. Obtain h-parameters interms of transmission and Z-parameters. (08 Marks)  
 c. For the network shown in Fig.Q.9(c), find Y and Z-parameters. (08 Marks)

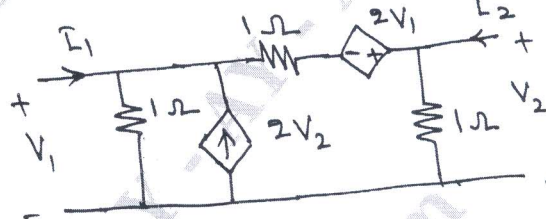


Fig.Q.9(c)

OR

- 10 a. What is hybrid parameters? And write the basic equations of h-parameter. (04 Marks)  
 b. Obtain the Y-parameters of the two networks shown in Fig.Q.10(b). (08 Marks)

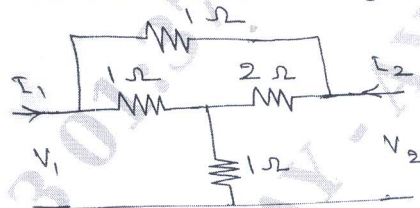


Fig.Q.10(b)

- c. Find the T-parameters for the network shown in Fig.Q.10(c). (08 Marks)

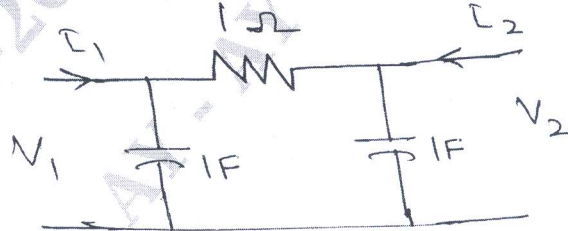


Fig.Q.10(c)

\*\*\*\*\*