



# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC42

**Fourth Semester B.E. Degree Examination, Jan./Feb. 2023**

## Analog Circuits

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- Explain the working of classical discrete circuit Bias – voltage divider bias. (10 Marks)
  - Design a collector – to – base bias circuit for the specified conditions. Given :  
 $V_{CC} = 15V$ ,  $V_{CE} = 5V$ ,  $I_C = 5mA$ ,  $\beta = 100$ . (10 Marks)

**OR**

- Draw and explain the MOSFET biasing circuit using Fixed  $V_G$ . (10 Marks)
  - Derive the expression for  $g_m$  and  $A_V$  for the MOSFET amplifier circuit. (10 Marks)

### Module-2

- Write a note on three basic configuration of a MOSFET amplifier. Derive expression for characterizing parameters of MOSFET amplifier. (10 Marks)
  - Draw the high frequency equivalent circuit of a MOSFET and explain the significance of the different elements of the circuit. (10 Marks)

**OR**

- Explain the working of RC – phase shift oscillator using FET. (10 Marks)
  - In Hartley oscillator  $L_1 = 20\mu H$ ,  $L_2 = 2mH$  and C variable. Find the range of C, if frequency is to be varied from 1 MHz to 2.5 MHz. Neglect the mutual inductance. (10 Marks)

### Module-3

- Draw the block diagram of current series feedback amplifier and derive an expression for input resistance, voltage gain, and output resistance. (10 Marks)
  - How power amplifiers are classified? Explain them briefly. (10 Marks)

**OR**

- Explain the working of class B push pull amplifier with relevant waveforms. Show that maximum conversion efficiency is 78.5%. (10 Marks)
  - Explain series – shunt (voltage series) feedback amplifier. Determine input and output resistance of the amplifier. (10 Marks)

### Module-4

- Explain the working of inverting schmitt trigger. Derive the equation for the trigger points. (10 Marks)
  - Derive an expression for the output of an inverting summing amplifier with 3 inputs and hence prove the circuit can act averaging amplifier. (10 Marks)

**OR**

- Explain the working of instrumentation amplifier. Mention its applications. (10 Marks)
  - Explain the working of practical non-inverting amplifier. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-5**

- 9 a. Explain Successive – Approximation type – ADC with neat block diagram. (10 Marks)  
b. Explain the working of precision full wave rectifier with relevant circuit and waveforms. (10 Marks)

OR

- 10 a. Explain the working of a monostable multifier with relevant circuit and wave forms. (10 Marks)  
Mention few applications of this circuit.  
b. Design a second order low-pass Butterworth filter having high cut-off frequency of 1 KHz. (10 Marks)  
Draw its frequency response.

\*\*\*\*\*