

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC33

**Third Semester B.E. Degree Examination, June/July 2023**

## Analog Electronics

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Derive an expression for  $A_V$ ,  $Z_i$ , and  $Z_o$  for CE –fixed bias using  $r_e$  equivalent model. (10 Marks)
- b. What is an emitter follower? Discuss about emitter follower circuit and find  $Z_i$ ,  $Z_o$  and  $A_V$  using  $r_e$  – model. (10 Marks)

OR

- 2 a. Define h-parameters and derive h-parameters model of CE – BJT. (10 Marks)
- b. For an emitter – bias circuit (capacitor is unbypassed), determine  $r_e$ ,  $Z_i$ ,  $Z_o$  and  $A_V$ . Given  $R_B = 470K\Omega$ ,  $R_C = 2.2K\Omega$ ,  $V_{CC} = 20V$ ,  $R_E = 0.56K\Omega$ ,  $C_E = 10\mu F$ ,  $\beta = 120$ ,  $r_o = 40K\Omega$ ,  $C_C = 10\mu F$ . (10 Marks)

### Module-2

- 3 a. For the self-bias configuration shown has an operating point  $V_{GSQ} = -2.6V$  and  $I_{DQ} = 2.6mA$  with  $I_{DSS} = 8mA$  and  $V_p = -6V$ . Assume  $Y_{OS} = 20\mu S$ . (Refer Fig.Q3(a)).  
Find : i)  $g_m$     ii)  $r_d$     iii)  $Z_i$     iv)  $Z_o$     v)  $A_V$ .

 


Fig.Q3(a)

(10 Marks)

- b. Derive an expression for  $Z_i$ ,  $Z_o$  and  $A_V$  for JFET source follower circuit using small signal model. (10 Marks)

OR

- 4 a. Explain the small-signal model of the FET. (10 Marks)
- b. Write the ac equivalent circuit for voltage – divider JET configuration. Determine  $Z_i$ ,  $Z_o$  and  $A_V$ . (10 Marks)

1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-3**

- 5 a. Determine :
- The common logarithm of the number  $2.2 \times 10^3$
  - The power gain in decibels for  $P_0 = 100\text{m watts}$ ,  $P_i = 5\text{m watts}$
  - Find voltage gain in dB for o/p voltage  $100\text{V}$  and  $R_0 = 20\Omega$ . (08 Marks)
- b. Prove that miller effect of input capacitance.  $C_{mi} = (1 - A_v) C_f$  and output capacitance
- $$C_{m_0} = \left(1 - \frac{1}{A_v}\right) C_f. \quad (12 \text{ Marks})$$

OR

- 6 a. Derive an expression for high – frequency response of FET amplifier. (12 Marks)
- b. Discuss the effect of various capacitors on multistage frequency response. (08 Marks)

**Module-4**

- 7 a. Discuss about the different types of feedback connections indicating input and output signal. (12 Marks)
- b. With a neat circuit diagram, explain the working principle of FET RC–phase–shift oscillator. (08 Marks)

OR

- 8 a. What are the effects of negative feedback in an amplifier? Show how bandwidth of an amplifier increases with negative feedback. (10 Marks)
- b. A crystal has the following parameter  $L = 0.334\text{H}$ ,  $C_m = 1\text{pF}$ ,  $C = 0.065\text{pF}$  and  $R = 5.5\text{K}\Omega$ . Calculate the series resonant and parallel resonant frequency and Q of the crystal. (10 Marks)

**Module-5**

- 9 a. With a neat circuit diagram explain the operation of a transformer coupled class A power amplifier. (10 Marks)
- b. For the following distortion values, calculate :
- THD
  - Fundamental power component
  - $P_t$ .
- Given :  $D_2 = 0.2$ ,  $D_3 = 0.02$ ,  $D_4 = 0.06$ ,  $I_L = 3.3\text{A}$  and  $R_C = 4\Omega$ . (10 Marks)

OR

- 10 a. With a neat circuit diagram, explain the working principle of complementary symmetry push – pull amplifier. (10 Marks)
- b. With a neat circuit diagram, explain the working principle of fold back current limiting circuit. (10 Marks)

\*\*\*\*\*