

USN

--	--	--	--	--	--	--	--	--	--

10EC63

Sixth Semester B.E. Degree Examination, June/July 2023
Microelectronics Circuits

Time: 3 hrs.

Max. Marks: 100

Note: 1. Note: Answer any FIVE full questions, selecting atleast THREE questions from Part-A and any TWO questions from Part-B.
2. State all assumptions, including missing data.

PART - A

- 1 a. Explain channel length modulation and derive the equation for finite output resistance of a MOSFET in saturation. (08 Marks)
- b. Explain the role of substrate in V_t variation. (04 Marks)
- c. Design the circuit shown in Fig Q1(c), to establish a dc drain current $I_D = 0.5\text{mA}$. Calculate the percentage change in the value of I_D obtained when the MOSFET is replaced with another unit having same $K'_n W/L$ but $V_t = 1.5\text{V}$. Neglect the channel length modulation effects.

 


Fig Q1(c)

(08 Marks)

- 2 a. Obtain an expression for R_{in} , A_v , A_{vo} , G_v and R_{out} for CG amplifier circuit using MOSFET. (10 Marks)
- b. Explain the development of the T-equivalent circuit model for MOSFET. (05 Marks)
- c. Mention any 5 comparison of important characteristics of MOSFET and BJT. (05 Marks)
- 3 a. Explain the various short channel effects due to scaling. (10 Marks)
- b. For the high frequency equivalent circuit of a common source amplifier shown in Fig Q3(b), having $R_{sig} = 100\text{K}\Omega$, $R_{in} = 420\text{K}\Omega$, $C_{gs} = C_{gd} = 1\text{Pt}$, $g_m = 4\text{mA/u}$, and $R'_L = 3.33\text{K}\Omega$. Find the midband voltage gain $\left(\frac{u_o}{u_{sig}}\right)$ and upper 3-db frequency f_H .

 


Fig Q3(b)

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. Consider a common – gate amplifier specified as follows :
 $W/L = 7.2\mu\text{m}/0.36\mu\text{m}$, $\mu_n C_{ox} = 387\mu\text{A}/\text{V}^2$, $r_0 = 18\text{K}\Omega$, $I_D = 100\mu\text{A}$, $g_m = 1.25\text{mA}/\text{V}$,
 $\lambda = 0.2$, $R_s = 10\text{K}\Omega$, $R_L = 100\text{K}\Omega$, $C_{gs} = 2\text{fF}$, $C_{gd} = 5\text{fF}$ and $C_L = 0$. Find : $A_{v0} = R_{in}$, R_{out} ,
 G_V , G_{is} , G_i and f_H . (10 Marks)
- b. What is cascade amplifier and explain the folded cascade circuit. (05 Marks)
- c. Explain Wilson MOS current mirror circuit. (05 Marks)
- 5 a. Draw and explain the circuit diagram of a active load MOS differential pair and derive an expression for G_m . (12 Marks)
- b. Explain a two stage CMOS opamp with neat circuit diagram. (08 Marks)

PART – B

- 6 a. Explain the properties of negative feedback with required expressions. (10 Marks)
- b. Explain the effect of negative feedback on input resistance, output Resistance and gain of an ideal series shunt feedback amplifier. (10 Marks)
- 7 a. Explain instrumentation amplifier with neat circuit diagram and list the advantages and disadvantages of it. (10 Marks)
- b. Derive an expression for an input resistance of the investing amplifier, where A is the finite open loop gains. (05 Marks)
- c. For the logarithm amplifier shown in Fig Q7(c). Prove that output voltage V_0 is the logarithm of the input signal.

 


Fig Q7(c)

(05 Marks)

- 8 a. Explain the parameters used to characterize, the operation and performance of a logic circuit family. (08 Marks)
- b. Draw a CMOS logic circuit that realizes the function $F = (A + B)(C + D)$ (04 Marks)
- c. Provide transistor (W/L) ratios for the logic circuit shown in Fig Q8(c). Assume that for the basic inverter $n = 1.5$ and $P = 5$ and the channel length is $0.25\mu\text{m}$.

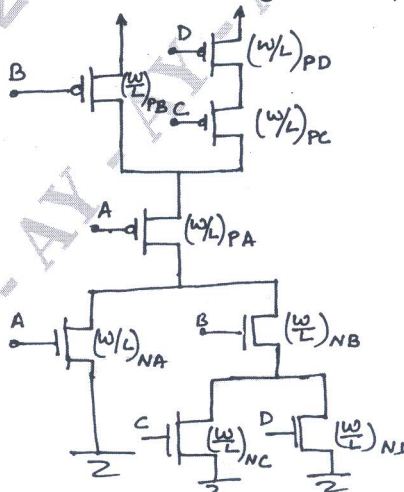


Fig Q8(c)

(08 Marks)