

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC32

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electronic Instrumentation

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. List and explain the types of static measurement errors. (06 Marks)
- b. What is a thermocouple? Explain the different types of thermocouple and what are the limitations of thermocouple. (08 Marks)
- c. Find the voltage reading and percentage error of each reading obtained with a voltmeter on 10 V range if the instrumentation has a $20 \text{ K}\Omega/\text{V}$ sensitivity and is connected across R_b of Fig.Q1(c).

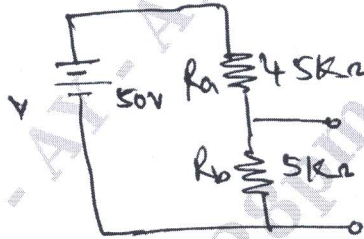


Fig.Q1(c)

(06 Marks)

OR

- 2 a. The expected value of the current through a resistor is 20 mA. However the measurement yields a current value of 18 mA. Calculate:
 - (i) Absolute error
 - (ii) Percentage error
 - (iii) Relative accuracy
 - (iv) Percentage accuracy
 (06 Marks)
- b. Explain the working of Ayrton shunt or universal shunt. (06 Marks)
- c. Explain with a diagram the operation of a multirange voltmeter. State the limitations of a multirange voltmeter. (08 Marks)

Module-2

- 3 a. Explain with the help of diagram the working principle of dual slope integrating type DVM (voltage to time conversion) (08 Marks)
- b. Explain with a diagram the working of digital PH meter. (06 Marks)
- c. A $4\frac{1}{2}$ digit voltmeter is used for voltage measurements:
 - (i) Find its resolution
 - (ii) How would 12.98 V be displayed on a 10 V range?
 - (iii) How would 0.6973 be displayed on 1V and 10V ranges?
 (06 Marks)

OR

- 4 a. Explain with a diagram, the basic principle of a successive approximation type DVM. (10 Marks)
- b. Explain the working principle of a digital frequency meter. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Explain the operation of CRO with a neat block diagram. And also mention the function of each block. (07 Marks)
- b. Explain the operation of the function generator with relevant block diagram. (07 Marks)
- c. Explain the operation of sweep generator with suitable circuit. (06 Marks)

OR

- 6 a. Briefly explain the operation of digital storage oscilloscope with relevant block diagram. (08 Marks)
- b. Describe with the help of a neat block diagram the working of a standard signal generator. (06 Marks)
- c. State the various application of an oscilloscope. (06 Marks)

Module-4

- 7 a. Explain and derive the balance equation of wheatstone bridge and mention the limitation. (06 Marks)
- b. A capacitance comparison bridge is used to measure capacity impedance at a frequency of 2 kHz. The bridge constants at balance are $c_3 = 100 \mu\text{F}$, $R_1 = 10 \text{ K}\Omega$, $R_2 = 50 \text{ K}\Omega$, $R_3 = 100 \text{ K}\Omega$. Find the equivalent series circuit of the unknown impedance. (06 Marks)
- c. With circuit diagram, explain Q-meter and mention its application. (08 Marks)

OR

- 8 a. With neat diagram, explain the working of Wein's bridge. How it can be used as oscillator? (08 Marks)
- b. What is Megger? Explain basic Megger circuit. (08 Marks)
- c. A Maxwell bridge is used to measure an inductive impedance. The bridge constants at balance are $c_1 = 0.01 \mu\text{F}$, $R_1 = 470 \text{ K}\Omega$, $R_2 = 5.1 \text{ K}\Omega$ and $R_3 = 100 \text{ K}\Omega$. Find the series equivalent of unknown impedance. (04 Marks)

Module-5

- 9 a. List the factors to be considered while selecting transducers. (06 Marks)
- b. Derive an expression for the gauge factor $K = 1 + 2\mu$ and explain. (08 Marks)
- c. What is meant by thermistor? Explain different form of thermistors. (06 Marks)

OR

- 10 a. List the advantages of LVDT and describe with the help of a diagram the construction of the LVDT. (06 Marks)
- b. Explain the operation of a piezo-electric transducer. (08 Marks)
- c. State the difference between photoemissive, photoconductive and photovoltaic transducer. (06 Marks)
