

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC34

## Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Digital Electronics

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Differentiate between :
- Combinational and sequential networks
  - Prime implicants and essential prime implicants. (04 Marks)
- b. Simplify the given Boolean function using K-map method. Obtain minimal SOP expression  $f(a, b, c, d) = \sum m(0, 1, 2, 4, 5, 7, 9, 12)$ . Draw the logic diagram using only NAND gates. (06 Marks)
- c. Construct a minimal sum for the following Boolean function using Q-M method and PI table reduction.  
 $f(a, b, c, d) = \sum m(1, 3, 13, 15) + \sum d(8, 9, 10, 11)$ . (10 Marks)

OR

- 2 a. Define the following terms: i) Literal ii) Maxterm iii) K-map iv) Product term. (04 Marks)
- b. Transform the given Boolean function and express the result in decimal notation
- $f(a, b, c) = (a + \bar{b})(\bar{b} + c)$  into maxterm canonical formula.
  - $f(a, b, c) = ac + ab + bc$  into minterm canonical formula. (06 Marks)
- c. Obtain minimal expression for the given functions using K-map
- Minimal product for  $f(a, b, c, d) = \prod M(0, 1, 2, 4, 5, 7, 9, 12)$
  - Minimal sums for  $f(a, b, c) = \sum m(0, 2, 3, 4, 5, 7)$ . (10 Marks)

### Module-2

- 3 a. What is magnitude comparator? Design a 1-bit magnitude comparator with the help of neat logic diagram. (06 Marks)
- b. Design binary full adder. Draw its logic diagram using 2 half adders and an OR gate. (06 Marks)
- c. Explain the working of 4-bit look ahead carry with relevant equations and logic diagram. (08 Marks)

OR

- 4 a. Implement  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 9, 10, 15)$  using i)  $8 \times 1$  MUX with a, b, c as select lines ii)  $4 \times 1$  MUX with a, b as select lines. (08 Marks)
- b. Realize full subtractor using 3-to-8 line decoder with OR gates. (06 Marks)
- c. What is priority encoder? Design 4-to-2 line priority encoder with MSB having highest priority and LSB having least priority. (06 Marks)

### Module-3

- 5 a. Explain the working of master-slave JK flip-flop. Draw the logic diagram using only NAND gates. (08 Marks)
- b. Explain the operation of switch debouncer circuit using SR latch. Draw necessary waveforms. (06 Marks)
- c. Obtain characteristic equation for SR and T flip-flops. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Explain the working of positive-edge triggered D flip-flop with the help of neat logic diagram and truth table. (08 Marks)
- b. Explain the following timing considerations:  
 i) Propagation delay in SR latch  
 ii) Setup and hold time in gated D latch  
 Draw necessary waveforms. (06 Marks)
- c. Discuss the working principle of gated SR latch with logic diagram and function table. (06 Marks)

**Module-4**

- 7 a. Explain the operation of SISO and SIPO shift registers with an example for each. Draw the logic diagram using 4 clocked D flip-flops. (06 Marks)
- b. Design a 3-bit binary ripple up counter using positive edge triggered T flip-flops with counting sequence and state diagram. (06 Marks)
- c. Design Mod-6 synchronous counter using clocked SR flip-flops for the sequence 0, 2, 3, 6, 5, 1. (08 Marks)


OR

- 8 a. Explain the operation of universal shift register with a neat logic diagram and mode control table. (06 Marks)
- b. Design a 4-bit Johnson counter using clocked D flip-flops. (06 Marks)
- c. Design a 3-bit synchronous down counter using clocked JK flip-flop. (08 Marks)

**Module-5**

- 9 a. Differentiate between Moore and Mealy model of sequential network. (04 Marks)
- b. Construct Mealy state diagram that will detect the input sequence 10110. When input pattern is detected, Z is asserted high. (06 Marks)
- c. Design a sequential circuit for the state diagram shown below. Consider the states as 00 – A, 01 – B, 10 – C and 11 – D. Use SR flip-flop. (10 Marks)

Fig.Q.9(c)

 

OR

- 10 a. Define the following terms:  
 i) State variable  
 ii) Excitation variable  
 iii) Next state  
 iv) Input variable. (04 Marks)
- b. Design a cyclic Mod-4 synchronous binary up counter using D flip-flops. If the input variable  $x = 0$ , it remains in the same state. Otherwise moves to next state. Obtain state table, transition table, excitation table. Draw the logic diagram. (10 Marks)
- c. Construct a Moore machine that counts the occurrences of a sequence 'abb' in any input string over {a, b}. (06 Marks)

\* \* \* \* \*