

# CBCS SCHEME

18EC72

## Seventh Semester B.E. Degree Examination, Dec.2023/Jan.2024 VLSI Design

Time: 3 hrs.

Max. Marks: 100

**Note:** 1. Answer any FIVE full questions, choosing ONE full question from each module.  
2. Missing data may be suitably assumed.

### Module-1

- 1 a. Derive an expression for drain current in linear and saturation region. (08 Marks)
- b. Draw the CMOS inverter circuit and explain its D.C. characteristic. (08 Marks)
- c. Implement a 2:1 MUX using transmission gate. (04 Marks)

OR

- 2 a. Explain the non ideal IV effect of MOSFET with respect to CMOS channel length modulation and mobility degradation. (08 Marks)
- b. Explain the operation of nMOS transistor with IV characteristics. (08 Marks)
- c. Sketch a static CMOS gate computing  $y = (A + B + C)D$ . (04 Marks)

### Module-2

- 3 a. Explain CMOS nWell process with necessary diagrams. (12 Marks)
- b. Mention different types of MOSFET capacitances with necessary diagrams and equations also MOSFET. Capacitances in cut off, linear and saturation region. (08 Marks)

OR

- 4 a. Define scaling. Explain constant field scaling and constant voltage scaling and why constant voltage scaling is usually preferred over full scaling. (07 Marks)
- b. With neat diagram, explain the Lambda based design rules for two metal layers. (06 Marks)
- c. Draw the layout for  $f = \overline{ABC}$  and estimate the cell area. (07 Marks)

### Module-3

- 5 a. Develop the RC delay model to compute the delay of the logic circuit and calculate the delay of unit sized inverter driving another unit in vertex. (06 Marks)
- b. Estimate  $t_{pdf}$  and  $t_{pdr}$  for the 3 input NAND gate shown in Fig.Q.5(b) if the output is loaded with h identical NAND gates. (08 Marks)

 


Fig.Q.5(b)


- c. Explain eVSL with an example. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Explain: i) Pseudo-nMOS ii) Ganged CMOS with necessary circuit examples. (06 Marks)
- b. If a unit transistor has  $R = 10K\Omega$  and  $e = 0.1fF$  in a 65nm process, compute the delay, in picoseconds, of the inverter Fig.Q.6(b) with a fan out of  $h = 4$ . (06 Marks)

Fig.Q.6(b)

 


- c. Explain linear delay model compare the logical effort of the following gates with the help of schematic diagrams: i) 3-input NAND gate ii) 3 input NOR gate. (08 Marks)

**Module-4**

- 7 a. Explain Resettable latches and flipflops using CMOS transmission gate. (06 Marks)
- b. Explain Dynamic logic. (06 Marks)
- c. Consider the two nFET chain in Fig.Q.7(c). The power supply is set to a value of  $V_{DD} = 3.3V$  and the nFET threshold voltage is  $V_{Th} = 0.55V$ . Find the output voltage  $V_{out}$  at the right side of the chain for the following values: i)  $V_{in} = 2.9V$  ii)  $V_{in} = 3.0V$  iii)  $V_{in} = 1.4V$  iv)  $V_{in} = 3.1V$ . (08 Marks)


Fig.Q.7(c)

 

OR

- 8 a. Explain pulsed latches with schematic and waveforms. (06 Marks)
- b. The output of an nFET is used to drive the gate of another nFET as shown in Fig.Q.8(b). Assume that  $V_{DD} = 3.3V$  and  $V_{th} = 0.6V$ . Find the output voltage  $V_{out}$  when the input voltages are at following values:  
i)  $V_a = 3.3V$  and  $V_b = 3.3V$   
ii)  $V_a = 2.0V$  and  $V_b = 2.5V$ .

Fig.Q.8(b)

 

(08 Marks)

- c. Explain Domino logic. (06 Marks)

**Module-5**

- 9 a. With neat schematic diagram explain the operation of Full CMOS static RAM cell. (10 Marks)
- b. Explain the different fault models. (10 Marks)

OR

- 10 a. With neat schematic diagram explain the operation of three transistor DRAM cell. (10 Marks)
- b. Write short notes on: i) Built in Self Test ii) Scan Design. (10 Marks)

\*\*\*\*\*