

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EE32

## Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Explain independent and dependent sources. (04 Marks)
- b. Determine the potential difference between M and N of the network shown in Fig Q1(b)

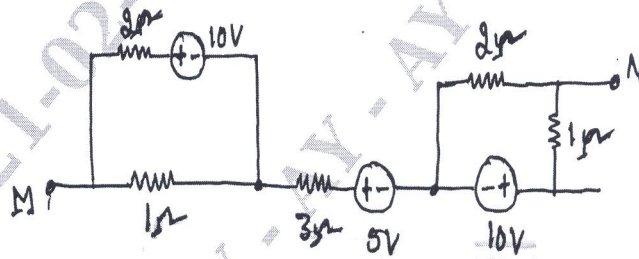


Fig Q1(b)

- c. Obtain star connected impedances to replace a set of  $\Delta$ -connected impedance. (08 Marks)

OR

- 2 a. Find equivalent resistance across x and y of the circuit shown in Fig Q2(a)

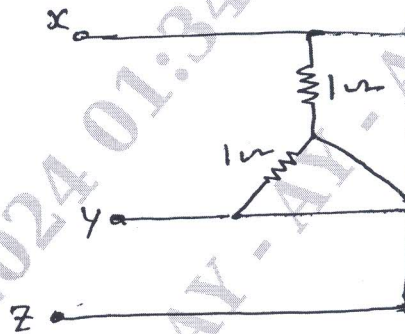


Fig Q2(a)

- b. Determine the node voltages of the circuit shown in Fig Q2(b)

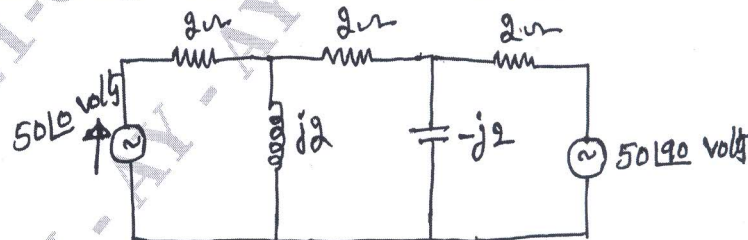


Fig Q2(b)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. Find  $I_x$ ,  $I_y$  and  $V_x$  of the circuit shown in Fig Q2(c), using mesh current analysis

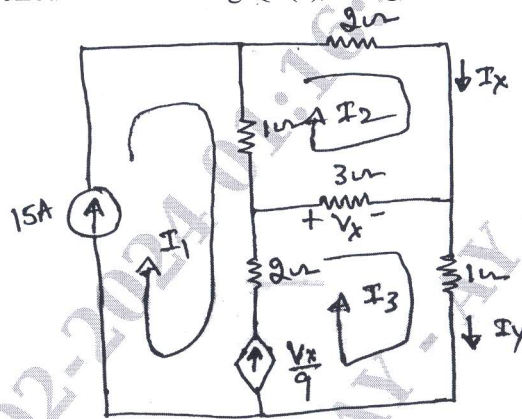


Fig Q2(c)

(08 Marks)

**Module-2**

- 3 a. Find current  $I_x$  in the network shown in Fig Q3(a) using superposition theorem.

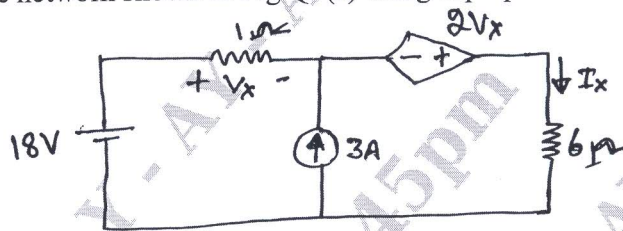


Fig Q3(a)

(10 Marks)

- b. Obtain Thevenin's equivalent circuit of the network shown in Fig Q3(b)

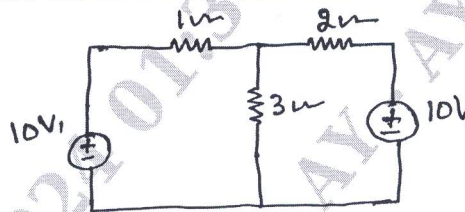


Fig Q3(b)

(10 Marks)

OR

- 4 a. State and explain nortons theorem.  
b. Determine  $I_x$  of the circuit shown in Fig Q4(b)

(08 Marks)

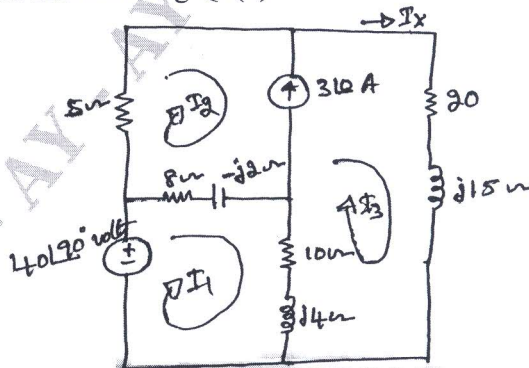


Fig Q4(b)

(12 Marks)

Module-3

- 5 a. Show that resonant frequency of series resonant circuit is equal to geometric mean of two half power frequencies. (08 Marks)
- b. Determine R, L and C of parallel circuit whose response curve shown in Fig Q5(b), what are the new value of  $\omega_0$  and bandwidth increased four times.

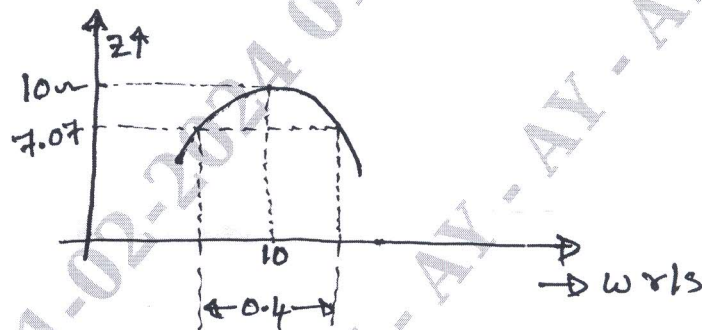


Fig Q5(b)

(12 Marks)

OR

- 6 a. Show that : i) The voltage of a capacitor cannot change instantaneously ii) The current in inductor cannot change instantaneously. (10 Marks)
- b. A series RC branch with  $R = 20\Omega$  and  $C = 1\mu\text{F}$  is shunted by an inductor of resistance  $20\Omega$  and inductance  $1\text{H}$ . This is supplied by a DC source of  $100\text{V}$  through series resistance of  $10\Omega$ . There is a switch across  $10\Omega$  resistance which is closed at  $t = 0$ . Solve for the currents in L and C and their derivatives at  $t = 0^+$ . (10 Marks)

Module-4

- 7 a. State and prove: i) Initial value theorem ii) Final value theorem. (10 Marks)
- b. Use initial value and final value theorem where they apply to find  $f(0)$  and  $f(\infty)$  for

$$F(s) = \frac{s^3 + 3s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)} \quad (10 \text{ Marks})$$

OR

- 8 a. Find Laplace transform of the function  
 $f(t) = t$  for  $0 < t < 1$   
 $= 0$  for  $t > 1$  (06 Marks)
- b. Obtain Laplace transform of impulse function. (08 Marks)
- c. Obtain Laplace transform of the function  $f(t)$  of periodic signal show in Fig Q8(c)

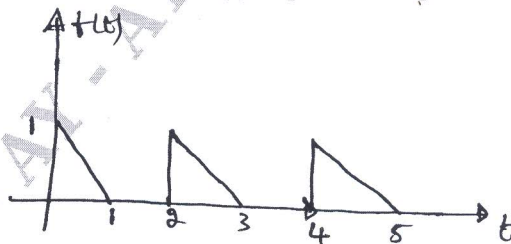


Fig Q8(c)

(06 Marks)

**Module-5**

- 9 a. A symmetrical star connected system is shown in Fig Q9(a). Calculate the three phase time voltage and power given  $V_{RN} = 230 \angle 0$  Volts assume phase sequence is RYB.

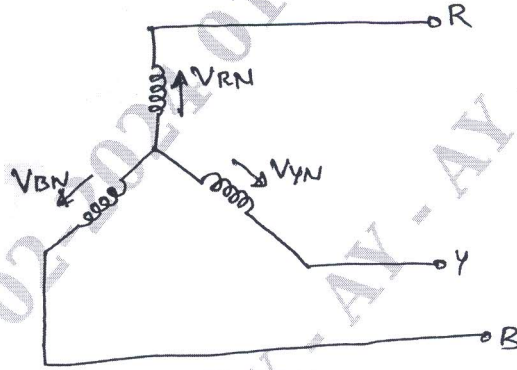


Fig Q9(a)

(10 Marks)  
(10 Marks)

- b. Define Z-parameter and draw its equivalent circuit.

OR

- 10 a. Determine Y-parameter of two part network shown in Fig Q10(a)

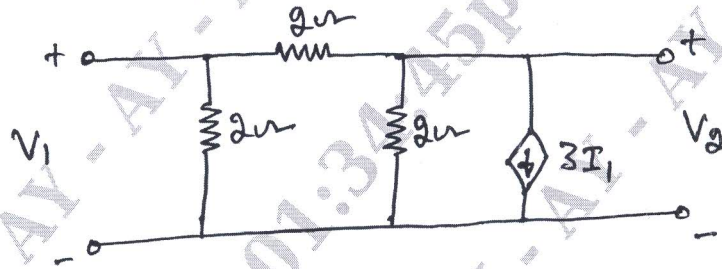


Fig Q10(a)

(10 Marks)

- b. Find the transmission parameter for the network shown in Fig Q10(b)

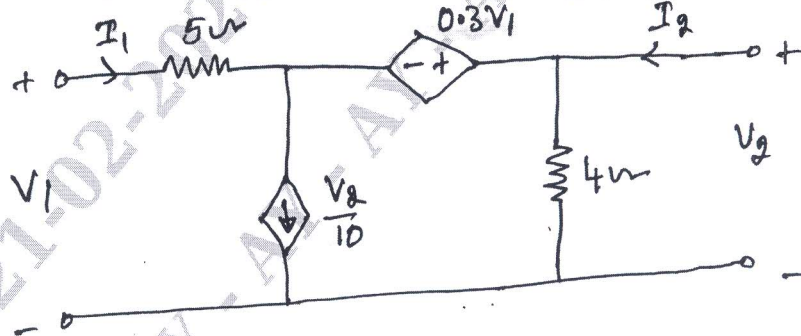


Fig Q10(b)

(10 Marks)

\*\*\*\*\*