

Fig Q2(b)

c. For the network of Fig Q2(c), find the currents I_1 , I_2 and I_3 .

6 L3 CO1

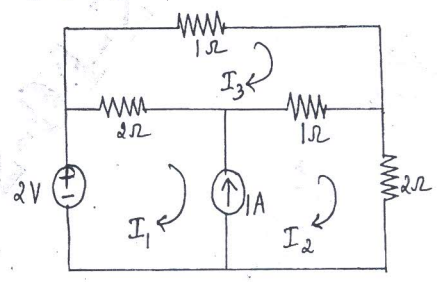


Fig Q2(c)

Module - 2

Q.3 a. State Thevenin's theorem. 2 L2 CO2

b. Find the current through 3Ω resistor using superposition theorem for Fig Q3(b) 8 L2 CO2

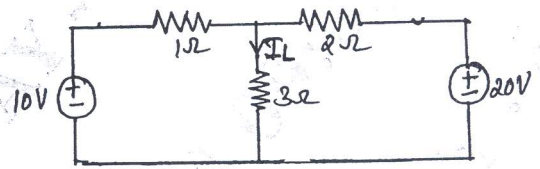


Fig Q3(b)

c. Obtain the Norton's and Thevenin's equivalent circuit at terminals 'a' and 'b' for the network of Fig Q3(c). Find ' V_0 ' 10 L3 CO2

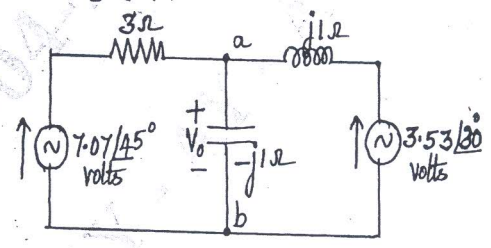


Fig Q3(c)

OR

Q.4 a. State Norton's theorem and draw the Norton's equivalent circuit. 2 L12 CO2

	b.	Obtain the condition for maximum power transfer in a circuit with AC source with source impedance Z_s connected to a load with variable resistance and variable reactance.	8	L2	CO2
	c.	Determine the maximum power transferred to the load Z_L in the network of Fig Q4(c)	10	L3	CO2

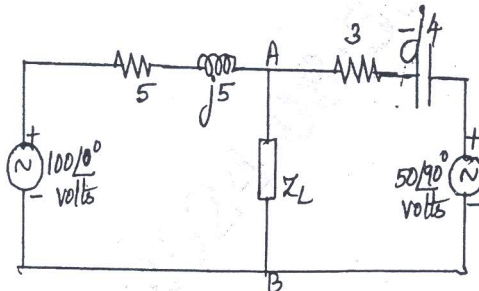


Fig Q4(c)

Module – 3

Q.5	a.	Define : i) Resonance ii) Quality factor iii) Bandwidth.	4	L1	CO3
	b.	Show that $f_0 = \sqrt{f_1 f_2}$, where f_1 and f_2 are the half power frequencies of a resonant circuit.	6	L2	CO3
	c.	In the network of Fig Q5(c), the switch K is closed at $t = 0$. Determine the values of i_1 , i_2 , $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$ at $t = 0^+$.	10	L3	CO3

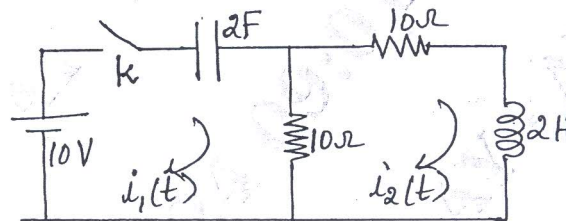
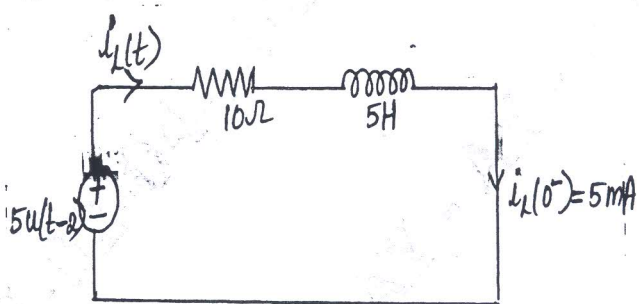
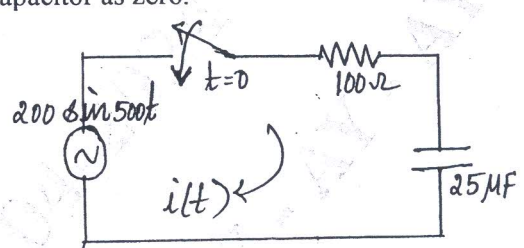


Fig Q5(c)

OR

Q.6	a.	What are initial conditions? Show the behaviour of R, L, C elements at the time of switching at $t = 0$ both at $t = 0^+$ and $t = \infty$.	6	L1	CO3
	b.	Derive the condition for parallel resonance when RL is connected parallel to RC.	6	L2	CO3
	c.	A series connected RLC circuit has $R = 4\Omega$, $L = 25\text{mH}$; calculate the value of C such that $Q = 50$. Also calculate the resonant frequency, upper and lower half power frequencies.	8	L3	CO3

Module – 4					
Q.7	a.	State and prove the following : i) Initial value theorem ii) Final value theorem	6	L2	CO4
	b.	Find the Laplace transform of the following functions : i) $f(t) = e^{-at}$; for $t \geq 0$ ii) $f(t) = K$; for $t \geq 0$	4	L1	CO4
	c.	Solve for $i_L(t)$ using Laplace transformation for the network of Fig Q7(c)	10	L3	CO4
 <p style="text-align: center;">Fig Q7(c)</p>					
OR					
Q.8	a.	Find the Laplace transform of unit step, unit impulse and unit ramp function.	4	L1	CO4
	b.	Verify initial and final value theorems for the function $f(t) = 1 + e^{-t}(\sin t + \cos t)$.	6	L2	CO4
	c.	For the circuit of Fig Q8(c), find the expression for current if the switch is closed at $t = 0$. Determine the value of current at $t = 1$ ms. Assume initial charge on the capacitor as zero.	10	L3	CO4
 <p style="text-align: center;">Fig Q8(c)</p>					
Module – 5					
Q.9	a.	Define Z – parameters with necessary equations.	4	L1	CO5
	b.	Derive Z – parameters in terms of T – parameters.	6	L2	CO5

	c.	A 3 - ϕ , 3 - wire, 400V delta connected load has impedances $Z_{ab} = 10\angle 0^\circ \Omega$, $Z_{bc} = 10\angle -30^\circ \Omega$ and $Z_{ca} = 10\angle 30^\circ \Omega$. The phase sequence is abc. Determine the phase currents and line currents.	10	L3	CO5
OR					
Q.1 0	a.	Define T- parameters with necessary equations.	4	L1	CO5
	b.	Derive Y-parameters in terms of Z-parameters.	6	L2	CO5
	c.	Obtain the Z-parameters for the circuit of Fig Q10(c)	10	L3	CO5

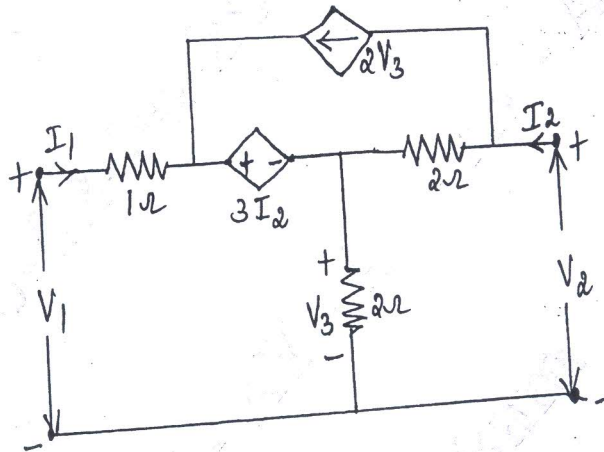


Fig Q10(c)
