

CBCS SCHEME

USN:

--	--	--	--	--	--	--	--	--	--

15EE32

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024

Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Find the power delivered by 20 volts voltage source using source transformation technique for the circuit given in Fig Q1(a).

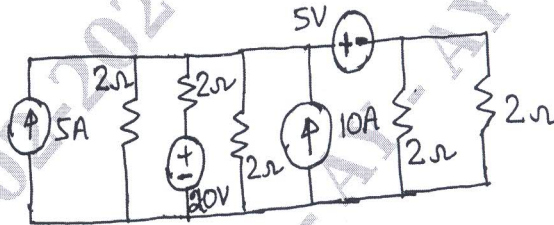


Fig Q1(a)

(08 Marks)

- b. Determine the voltage 'V_a' for the circuit shown in Fig Q1(b) using mesh analysis.

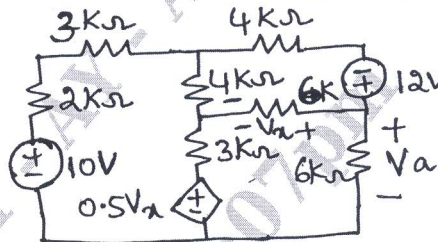


Fig Q1(b)

(08 Marks)

OR

- 2 a. Obtain the equivalent resistance between the terminals X and Y using star-Delta transformation for the circuit shown in Fig Q2(a)

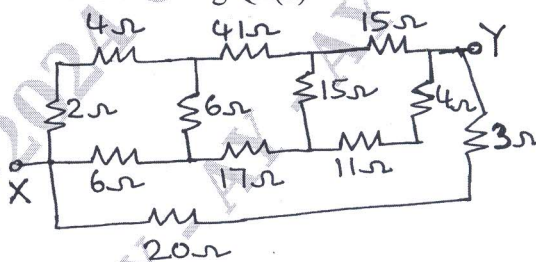


Fig Q2(a)

(06 Marks)

- b. Find the node voltages for the circuit shown in Fig Q2(b), using nodal analysis

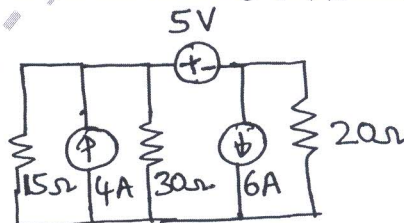


Fig Q2(b)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. A series R-L-C circuit has the following parameter values: $R = 10\Omega$, $L = 0.01\text{H}$ and $C = 100\mu\text{F}$. Compute the resonant frequency, quality factor of the circuit, bandwidth, lower and upper frequency of the bandwidth. (04 Marks)

Module-2

- 3 a. Find current through the $(3 + j4)\Omega$ impedance using superposition theorem for the circuit shown in Fig Q3(a)

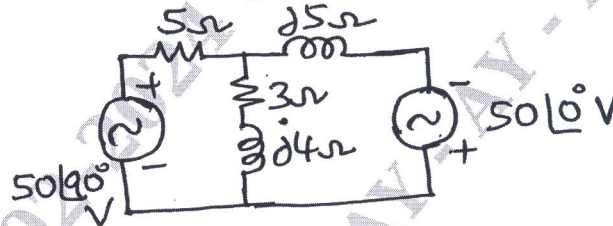


Fig Q3(a)

(08 Marks)

- b. Find I_L , using Thevenin's theorem the circuit in Fig Q3(b)

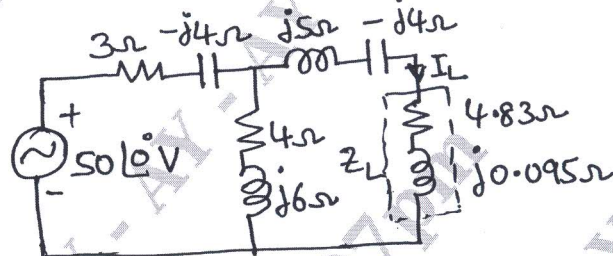


Fig Q3(b)

(08 Marks)

OR

- 4 a. Determine I_L in circuit Fig Q4(a) using Millman's theorem.

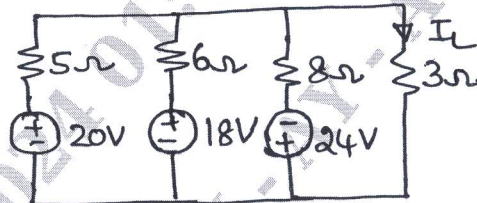


Fig Q4(a)

(08 Marks)

- b. For the circuit shown in Fig Q4(b), find the value of the resistance R_L for maximum power transfer and calculate the maximum power.

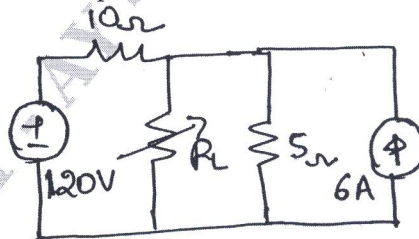


Fig Q4(b)

(08 Marks)

Module-3

- 5 a. In the circuit shown in Fig Q5(a) the switch is changed from the position 'a' to 'b' at $t = 0$. Find $i(t)$, $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t = 0^+$.

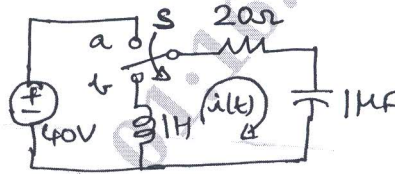


Fig Q5(a)

(08 Marks)

- b. Determine $v(t)$, $\frac{dv(t)}{dt}$ and $\frac{d^2v(t)}{dt^2}$ at $t = 0^+$ for the circuit shown in Fig Q5(b), when the switch is closed at $t = 0$.

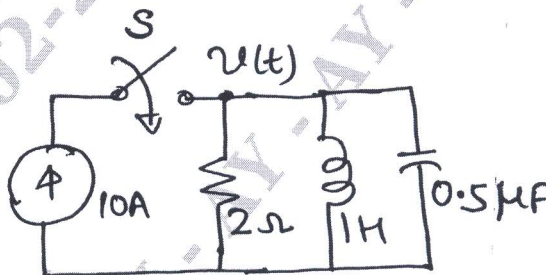


Fig Q5(b)

(08 Marks)

OR

- 6 a. In the circuit shown in Fig Q6(a), a steady state is reached when the switch is open. At $t = 0$, the switch is closed. Find the value of $V_a(0^-)$, $V_b(0^-)$, $V_a(0^+)$ and $V_b(0^+)$.

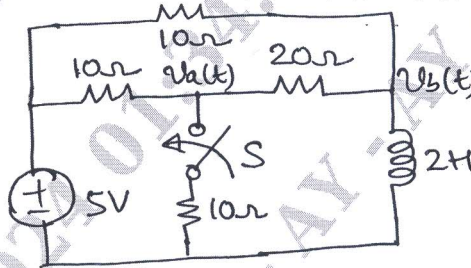


Fig Q6(a)

(08 Marks)

- b. Explain the behaviour of R.L.C elements at the time of switching at $t = 0$ both at $t = 0^+$ and $t = \infty$

(08 Marks)

Module-4

- 7 a. State and prove initial and final value theorems. (08 Marks)
 b. Find the Laplace transform of $i(t)$, for the waveform shown in Fig Q7(b).

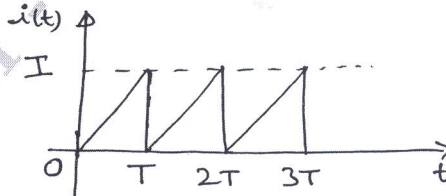


Fig Q7(b)

(08 Marks)

OR

8 a. Apply Initial value theorem to

i) $f(t) = 10e^{5t}$

ii) $5 \sin 3t$

iii) $5 - e^{-3t}$

(08 Marks)

b. Find the final value of

i) $\frac{2s+5}{(s+1)(s+2)}$

ii) $f(t) = 2 + e^{-3t} \cos 2t$

(08 Marks)

Module-59 a. Determine the line currents in a unbalanced star connected load supplied from a symmetrical 3-phase, 4-wire, 440V system. The branch impedances of the load are $Z_A = 5 \angle 30^\circ \Omega$, $Z_B = 10 \angle 45^\circ \Omega$ and $Z_C = 10 \angle 60^\circ \Omega$. The phase sequence is ABC.

(08 Marks)

b. Find the Z and Y parameters of the circuit shown in Fig Q9(b)

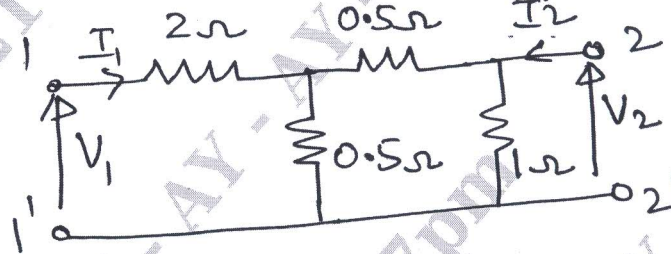


Fig Q9(b)

(08 Marks)

OR

10 a. Define ABCD and Hybrid parameters.

(08 Marks)

b. Using Millman's theorem, find the phase voltages of a 3-phase, 3-wire unbalanced star-connected load.

(08 Marks)
