

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EE35

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Digital System Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With basic block diagram, explain the combinational logic circuit. (04 Marks)
- b. Reduce the following function using K-map technique and implement using basic gates
i) $f(P, Q, R, S) = \sum m(0, 1, 4, 8, 9, 10) + d(2, 11)$
ii) $f(A, B, C, D) = \pi M(0, 2, 4, 10, 11, 14, 15)$ (12 Marks)

OR

- 2 a. Simplify using the Quine-McClusky minimization technique.
 $Y = f(a, b, c, d) = \sum m(0, 2, 8, 10)$ (08 Marks)
- b. Simplify the given function using MEV technique.
 $f(a, b, c, d) = \sum(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11).$ (08 Marks)

Module-2

- 3 a. Design a comparator to check if two N-bit numbers are equal. Configure this using cascaded stages of 1 – bit comparator. (04 Marks)
- b. Write the compressed truth table for a 4 to 2 line priority encoder with a valid output and simplify the same using K-Map. Design the logic circuit as well. (06 Marks)
- c. Implement the following Boolean function using a 4:1 MUX with A and B as select lines
 $Y = f(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 12, 14).$ (06 Marks)

OR

- 4 a. Write a short note on 4-bit parallel Adder. (04 Marks)
- b. Using active high output 3:8 line decoder, implement the following functions
 $f_1(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 11, 15)$
 $f_2(A, B, C, D) = \sum m(1, 3, 4, 11, 13, 14)$ (06 Marks)
- c. Design an 8:1 MUX Tree using only 2:1 multiplexers. (06 Marks)

Module-3

- 5 a. Explain the operation of Master-Slave JK flip-flop with logic diagram, truth table, symbol and timing diagram. (08 Marks)
- b. Distinguish between sequential circuits and combinational circuits. (04 Marks)
- c. Explain the operation of basic bistable element, using two-inverter configuration. (04 Marks)

OR

- 6 a. Derive characteristics equations for SR flip-flop and JK flip-flop, represent truth table and K-maps. (04 Marks)
- b. Explain the operation of 4-bit ring counter and twisted ring counter. (06 Marks)
- c. Design synchronous MOD6 counter using clocked 'D' flip flops for the sequence $0 \rightarrow 2 \rightarrow 3 \rightarrow 6 \rightarrow 5 \rightarrow 1$, again, 0.... represent application table, excitation table and logic diagram. (06 Marks)

Module-4

- 7 a. Distinguish between Moore and Mealy model with necessary block diagrams. (08 Marks)
 b. Give output function, transition table and state diagram by analyzing the sequential circuit shown in Fig. Q7(b). (08 Marks)

 


Fig. Q7(b)

OR

- 8 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)
 b. Design a synchronous counter using J-K flip flops to count the sequence 0, 1, 2, 4, 5, 6, 0, 1, 2. Use state diagram and state table. (10 Marks)

Module-5

- 9 a. Mention styles/types of HDL description. Explain behavioral type with half adder example in both VHDL and verilog. (08 Marks)
 b. Compare VHDL and verilog. (04 Marks)
 c. Explain verilog data types. (04 Marks)

OR

- 10 a. Tabulate Rotate operators used in HDL with example operand A = 1110. (08 Marks)
 b. Draw the block diagram of 3-bit carry look ahead adder. Write verilog code for the same. (08 Marks)
