

CBCS SCHEME

USN

18EE34

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any **FIVE** full questions, choosing **ONE** full question from each module.

Module-1

- 1 a. Draw the neat circuit diagram for negative clamper and explain with suitable waveforms. (06 Marks)
- b. For the transistor circuit shown in Fig. Q1 (b), determine R_B and R_C . Take $I_{C(Sat)} = 12 \text{ mA}$, $\beta = 200$, $V_{CE(sat)} = 0 \text{ V}$. (06 Marks)

 


Fig. Q1 (b)

- c. Determine the Q-points (I_{CQ} , V_{CEO}) for the circuit diagram shown in Fig. Q1 (c). Also find V_B , V_C , V_{BC} . (08 Marks)

 


Fig. Q1 (c)

OR

- 2 a. Derive the expression for stability factor for Emitter Bias circuit with respect to I_{CO} and V_{BE} . (08 Marks)
- b. For the circuit shown in Fig.Q2 (b) with $\beta = 100$ and $I_C = 2 \text{ mA}$ for Si transistor. Calculate V_{CE} , R_E and stability factor $S(I_{CO})$. (08 Marks)

 


Fig. Q2 (b)

- c. Determine the stability factor $S(V_{BE})$ and change in I_C from 25°C to 100°C for transistor with $V_{BE}(25^\circ\text{C}) = 0.65 \text{ V}$ and $V_{BE}(100^\circ\text{C}) = 0.48 \text{ V}$ for fixed bias arrangement with $R_B = 270 \text{ k}\Omega$ and $\beta = 120$. (04 Marks)

Module-2

3. a. Derive the expression for Miller Input capacitance with suitable circuit diagram. (07 Marks)
 b. For the circuit shown in Fig. Q3 (b), draw neat simplified h-parameter model circuit and obtain the expression for current gain and voltage gain. (06 Marks)

 


Fig. Q3 (b)

- c. For the amplifier shown in Fig.Q3 (b) with $h_{fe} = 50$, $h_{ie} = 1.1 \text{ k}\Omega$, $h_{oe} = 25 \mu\text{A/V}$, $h_{re} = 2.5 \times 10^{-4}$, $R_1 = 50 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $R_S = 1 \text{ k}\Omega$. Calculate Input impedance, Output impedance, Current gain and Voltage gain. (07 Marks)

OR

4. a. Compare the relation between the parameters of simplified hybrid model and r_e model of the transistor in CE configuration with appropriate circuit diagram and expressions. (04 Marks)
 b. Obtain the expression for Input impedance, Output impedance and voltage gain of Emitter-follower configuration using AC equivalent circuit with r_e model. (08 Marks)
 c. For the Emitter-follower configuration with $V_{CC} = 12 \text{ V}$, $R_B = 220 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $\beta = 100$ and $r_o = \infty$. Calculate r_e , Z_i , Z_o and A_v . (08 Marks)

Module-3

5. a. For the cascaded arrangement shown in Fig. Q5 (a), determine the loaded gain for each stage, total gain for the system (A_v), total current gain and total gain (A_V), if the emitter-follower configuration were removed. (10 Marks)

 


Fig. Q5 (a)

- b. For the Darlington emitter-follower with $V_{CC} = 18 \text{ V}$, $R_B = 3.3 \text{ M}\Omega$, $R_E = 390 \Omega$, $r_i = 5 \text{ k}\Omega$, $\beta_D = 8000$, $V_{BE} = 1.6 \text{ V}$. Calculate the dc bias voltages (V_B , V_E , V_C), Currents (I_B , I_C), Input impedance, Output impedance, Voltage gain and Current gain. (10 Marks)

OR

6. a. Derive an expression for Input impedance of voltage series feedback and voltage shunt feedback amplifiers with suitable circuit connections. (10 Marks)
 b. Calculate the gain of a negative feedback amplifier having $A = -2000$, if feedback factor is 20%. (04 Marks)
 c. List the important characteristics and applications of Darlington Emitter follower. (06 Marks)

Module-4

- 7 a. For the circuit shown in Fig. Q7 (a), the dc base current is 5 mA and the ac input signal results in a peak base current swing of 4 mA. Assume Si transistor with $\beta = 30$. Determine ac power delivered to the load, dc power drawn by the circuit and conversion efficiency. (10 Marks)

 


Fig. Q7 (a)

- b. A crystal has the following parameters : $L = 0.334 \text{ H}$, $C = 0.065 \text{ PF}$, $C_M = 1 \text{ PF}$, $R = 5.5 \text{ k}\Omega$. Calculate the series resonant frequency and parallel resonant frequency. By what percent does the parallel-resonant frequency exceed the series resonant frequency? Also find the Q of the crystal. (10 Marks)

OR

- 8 a. Explain the operation of Wein bridge oscillator with appropriate circuit diagram and expressions. (07 Marks)
- b. For a Class B push-pull power amplifier with $V_{CC} = 25 \text{ V}$ driving an 8Ω load, calculate maximum input power, maximum output power, maximum circuit efficiency, maximum collector dissipation and the input voltage at which maximum power dissipation occurs. (10 Marks)
- c. Write three merits of RC phase shift oscillator. (03 Marks)

Module-5

- 9 a. For the FET amplifier shown in Fig. Q9 (a), calculate Z_i , Z_o and A_v . Also calculate Z_i , Z_o and A_v , neglecting the effect of r_d and compare the results. Take $I_{DSS} = 15 \text{ mA}$, $V_P = -6 \text{ V}$, $y_{OS} = 25 \mu\text{s}$. (10 Marks)

 


Fig. Q9 (a)

- b. Draw the circuit symbol and small signal ac model of D-MOSFET and E-MOSFET. Also derive the expression for transconductance g_m for both the MOSFET's. (10 Marks)

OR

- 10 a. For the circuit shown in Fig. Q10 (a), calculate Z_i , Z_o and A_v . Also find V_0 if $V_i = 1 \text{ mV(rms)}$. (10 Marks)

 


Fig. Q10 (a)

Take $I_{DSS} = 12 \text{ mA}$,
 $V_P = -3.5 \text{ V}$
 $V_{GSQ} = -0.75 \text{ V}$,
 $r_d = 50 \text{ k}\Omega$

- b. Explain the working and construction of JFET in detail and draw its transfer characteristics and drain characteristics. (10 Marks)
