 


CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

21EE42

Fourth Semester B.E. Degree Examination, Dec.2023/Jan.2024 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define canonical minterm form and canonical maxterm form. (05 Marks)
- b. Simplify the function using K-map,
 $f(a, b, c, d) = \sum m(2,3,4,5,13,15) + \sum d(8,9,10,11)$. (07 Marks)
- c. Simplify the given Boolean function using K-map and implement using logic gates :
 $f(A, B, C, D, E) = \sum m(3,7,10,11,12,13,14,15,17,19,21,23,25,27,28,29,31) + \sum d(2,6,26,30)$. (08 Marks)

OR

- 2 a. Define combinational logic, canonical SOP canonical POS and PI with examples. (08 Marks)
- b. Obtain minimal SOP expression using Quine-McCluskey method and implement it using logic gates $f(a, b, c, d) = \sum m(0,1,4,5,9,11,13,15)$. (12 Marks)

Module-2

- 3 a. Implement Full Subtractor using a decoder and two NAND gates. Write its truth table. (08 Marks)
- b. Design a two bit magnitude comparator and draw the logic diagram. (12 Marks)

OR

- 4 a. Implement the following using 8 : 1 MUX with a, b, c as select lines.
 $f(a, b, c, d) = \sum m(0,1,5,6,7,9,10,15)$. (08 Marks)
- b. Distinguish between a decoder and encoder. (05 Marks)
- c. Explain briefly about Carry Look Ahead Adder. (07 Marks)

Module-3

- 5 a. Explain the working of Master Slave JK-Flip-Flops with functional table and neat timing diagrams. Show how race condition is overcome. (12 Marks)
- b. Derive the characteristics equations for D, JK, T and SR FlipFlops. (08 Marks)

OR

- 6 a. Explain the working of SR Flip Flop along with truth table. Show the mechanism of switch debouncer using SR latch with neat waveforms. (10 Marks)
- b. Discuss about positive and negative edge triggered D Flip Flop in brief. (10 Marks)

Module-4

- 7 a. Explain 4 modes of operation of shift register with suitable logic diagram and truth table. (10 Marks)
- b. Design a MOD-5 synchronous binary counter using clocked JK Flip-Flops. (10 Marks)

OR

- 8 a. Briefly discuss about the working of 3-bit binary ripple counter with neat logic and timing diagrams. (10 Marks)
- b. Design a 4-bit binary ripple up counter using positive edge triggered T-Flip Flop with a count enable line. Write the counting sequence and relevant timing diagram. (10 Marks)

Module-5

- 9 a. Design a sequential circuit using D-Flip Flop for the given state diagram. (12 Marks)

 


Fig. Q9 (a)

- b. Explain the procedure of designing clocked synchronous sequential circuit with a suitable example. (08 Marks)

OR

- 10 a. Discuss briefly about Mealy and Moore models with neat block diagrams. (08 Marks)
- b. Write brief notes on :
- ROM
 - RAM.
 - EPRAM
 - Flash memory.
- (12 Marks)
