

CBCS SCHEME

USN

--	--	--	--	--	--	--

15MT35

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks : 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

1. a. Explain the V-I characteristics of an Ideal diode, silicon diode, Germanium diode and zener diode. (08 Marks)
- b. Explain junction diode models with necessary equivalent circuits. (08 Marks)

OR

2. a. Explain, with diagrams, how a pn-junction diode can be used as a switch. (06 Marks)
- b. Explain how the capacitor filter reduces the ripple in rectifier circuit. (06 Marks)
- c. The input voltage of centre tapped full wave rectifier is 10V(rms). The sum of the dc resistance of the transformer winding and forward dc resistance of the diode is $R_s = 0.2\Omega$, the load resistance $R_L = 10\Omega$ and forward diode drop $V_D = 0.7V$, Find :
 - i) Peak load current
 - ii) DC load current.
 - iii) Individual diode dc current.
 - iv) DC output voltage.
 - v) PIV.(04 Marks)

Module-2

3. a. Explain first order low pass Butterworth filter and derive the gain and phase angle equations. (08 Marks)
- b. Design a wide band pass filter with $f_L = 200\text{hz}$, $f_H = 1\text{KHz}$,
 - i) passband gain = 4
 - ii) draw the frequency response of the filter
 - iii) calculate the value of Q for the filter.(08 Marks)

OR

4. a. Explain second order high pass Butterworth filter with necessary circuit diagram and equations. (04 Marks)
- b. Design Wein bridge oscillator for the Fig.Q4(b) below so that $f_0 = 965\text{hz}$. (04 Marks)

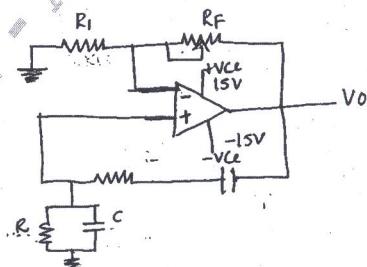


Fig.Q4(b)

- c. State Backhausen criterion for sustained oscillations and explain phase shift oscillator with necessary circuit and equations. (08 Marks)

Module-3

- 5 a. Explain op-amp as a basic comparator and mention characteristics of a comparator. (08 Marks)
 b. Explain inverting Schmitt trigger with circuit, waveforms and necessary equations for LTP, UTP and hysteresis. (08 Marks)

OR

- 6 a. Explain 555 timer operation with block diagram and 8 pins. (Pinout diagram) (08 Marks)
 b. Describe an Astable multivibrator with circuit using 555 timer IC, waveforms and necessary equations. (08 Marks)

Module-4

- 7 a. Draw R_s latch with NAND and NOR gate circuit. (04 Marks)
 b. Explain clocked master-slave JK flip-flop with necessary logic circuit. (06 Marks)
 c. Explain bi-directional shift register with parallel load. (06 Marks)

OR

- 8 a. Explain 3-bit synchronous – Binary up-down counter. (08 Marks)
 b. Explain how read and write information transfer takes place in magnetic core-memory. (08 Marks)

Module-5

- 9 a. What is multiplexer? Realize 4 : 1 multiplexer using basic gates and write its truth table. (08 Marks)
 b. Explain the operation of R-2R DAC. And also drive the expression of output voltage. (08 Marks)

OR

- 10 a. What is decoder? Realize 2 to 4 line decoder using basic gates and write its truth table. (08 Marks)
 b. Explain the operation of a successive approximation ADC. (08 Marks)
