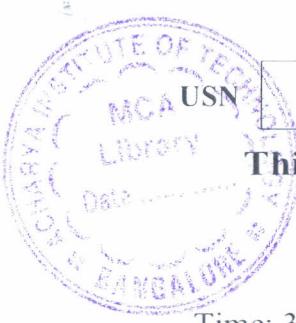


CBCS SCHEME



--	--	--	--	--	--

BEE302

**Third Semester B.E./B.Tech. Degree Supplementary Examination,
June/July 2024**


Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

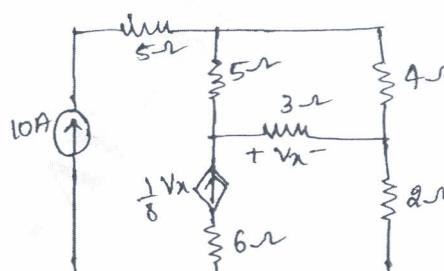Module – 1				M	L	C	
Q.1	<p>a. Explain the following terms : i) Active and Passive element ii) Ideal and practical voltage sources.</p>			6	L2	CO1	
	<p>b. Using sources transformation and source shifting techniques find the voltage across 2Ω resistor in the Fig Q1(b)</p>			6	L3	CO1	
	<p>c. Find the equivalent resistance between terminal AB shown in Fig Q1(c)</p>			8	L3	CO1	
OR							
Q.2	<p>a. Find the loop current I_1, I_2 and I_3 in the circuit shown in Fig Q2(a), by loop analysis</p>			8	L3	CO1	
	<p></p> <p>Fig Q2(a)</p>						

	b. Find the voltage at nodes 1, 2, 3, 4 for the network shown in Fig Q2(b)	8	L3	CO1
	<p style="text-align: center;">Fig Q2(b)</p>			
	c. For the network shown in Fig Q2(c) draw the dual network.	4	L3	CO1
Module – 2				
Q.3	a. State and explain the super position theorem.	8	L1	CO2
	b. For the network shown in Fig Q3(b). Find the Thevenin's voltage, Short circuit current and determine the current flowing through 6Ω resistor.	8	L3	CO2
	<p style="text-align: center;">Fig Q3(b)</p>			
	c. Find the value of Z_L for which maximum power transfer occurs in the circuit given in Fig Q3(c)	4	L2	CO2
	<p style="text-align: center;">Fig Q3(c)</p>			

OR

Q.4	a. Determine the Norton's equivalent circuit across AB terminals in network of Fig Q4(a). Hence determine the current in 5Ω . Also draw the Thevenin's equivalent circuit across AB terminals.	10	L3	CO2
	<p>Fig Q4(a)</p>			
Module – 3				
Q.5	a. Show that for a series RLC circuit the selectivity $Q_0 = \frac{f_0}{f_2 - f_1}$. Where $f_0 \rightarrow$ resonant frequency and f_1, f_2 are half power frequency.	10	L3	CO3
	b. Determine the i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$ when switch 'K' is moved from position 1 to 2 at $t = 0$ for the network shown in Fig Q5(b). Assume capacitor is initially uncharged.	10	L3	CO3
	<p>Fig Q5(b)</p>			

OR

Q.6	a.	If $R = 25\Omega$, $L = 0.5H$ and $C = 5\mu F$, find the War, Q and bandwidth for the circuit as shown in the Fig Q6(a)	6	L3	CO3
-----	----	---	---	----	-----

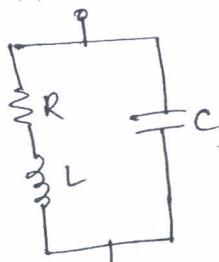


Fig Q6(a)

	b.	The network shown in Fig Q6(b) reaches a steady state with switch 'K' is closed. At $t = 0$, the switch is opened, find $i(t)$ to $t > 0$.	8	L3	CO3
--	----	--	---	----	-----

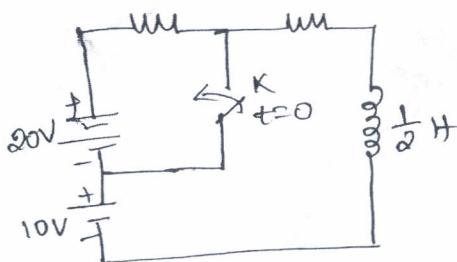


Fig Q6(b)

	c.	Write the initial conditions for the basic passive elements.	6	L2	CO3
--	----	--	---	----	-----

Module - 4

Q.7	a.	Write the definition of Laplace transform and obtain the Laplace transform of $f(t) = K$ for $t \geq 0$ = 0 for $t < 0$ Where 'K' is constant.	4	L1	CO4
-----	----	--	---	----	-----

	b.	Find the Laplace transform of i) $\delta(t)$ ii) $u(t)$ iii) $\sin \omega t$ iv) $e^{-at} \cos \omega t$	8	L3	CO4
--	----	---	---	----	-----

	c.	Obtain the Laplace transform of the function shown in Fig Q7(c)	8	L3	CO4
--	----	---	---	----	-----

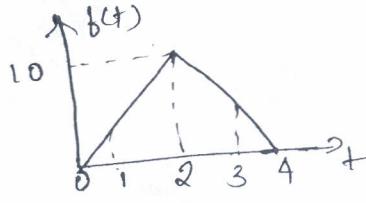


Fig Q7(c)

OR

Q.8	a.	State and prove initial and final value theorem in Laplace transform.	8	L2	CO4
-----	----	---	---	----	-----

	b.	Use initial and final value theorems, where they apply to find $f(0)$ and $f(\infty)$ for the following :	8	L3	CO4
--	----	---	---	----	-----

$$\text{i)} F(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)} \quad \text{ii)} F(s) = \frac{e^{2s}(s+2)}{s^2 + 5}$$

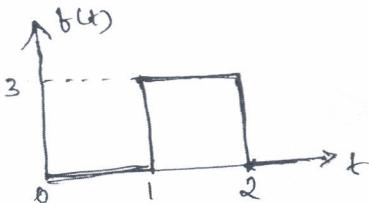
	c.	Express the waveform shown in Fig Q8(c), in terms of step functions.	4	L2	CO4
					

Fig Q8(c)

Module - 5

Q.9	a.	Determine the line current and total power supplied to a Delta connected load of $Z_{ab} = 10[60^\circ]\Omega$, $Z_{bc} = 20[90^\circ]\Omega$ and $Z_{ca} = 25[30^\circ]\Omega$. Assume 3- ϕ 400V, ABC system.	10	L3	CO5
	b.	For the network shown in Fig Q9(b), find Z-parameters	10	L3	CO5

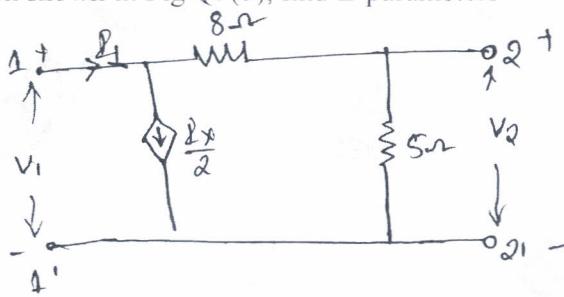


Fig Q9(b)

OR

Q.10	a.	Express Y-parameters in terms of Z-parameters	10	L2	CO5
	b.	Find the Y-parameters of the two part network shown in Fig Q10(b)	10	L3	CO5

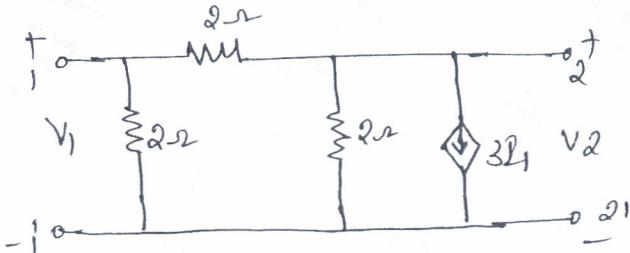


Fig Q10(b)

* * * * *