



**Third Semester B.E./B.Tech. Degree Supplementary Examination,
June/July 2024
Network Analysis**

Time: 3 hrs.

Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M : Marks , L: Bloom's level , C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Compare the following : (i) Active and Passive elements (ii) Linear and Non-linear elements	4	L2	CO1
	b.	For the circuit shown below in Fig. Q1 (b), find the mesh currents and the value I_X using mesh analysis. <div style="text-align: center;"> </div> <p style="text-align: center;">Fig. Q1 (b)</p>	8	L3	CO1
	c.	For the circuit of Fig. Q1 (c), find the equivalent resistance between a and b using star to delta transformation. <div style="text-align: center;"> </div> <p style="text-align: center;">Fig. Q1 (c)</p>	8	L3	CO1
OR					
Q.2	a.	Using source shift and source transformations, simplify the circuit between P and Q in Fig. Q2 (a). <div style="text-align: center;"> </div> <p style="text-align: center;">Fig. Q2 (a)</p>	10	L4	CO1

	<p>b. For the circuit in Fig. Q2 (b), find all the node voltages using node analysis.</p>	10	L3	CO1
--	---	----	----	-----

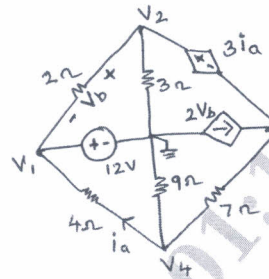


Fig. Q2 (b)

Module - 2

Q.3	a. State and prove Thevenin theorem.	5	L2	CO2
	b. For the circuit shown in Fig. Q3 (b), find the voltage V_x using superposition theorem.	8	L4	CO2

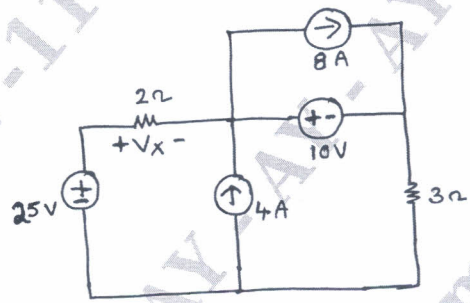


Fig. Q3 (b)

	c. Find the current through the load of $1\text{ K}\Omega$, using Millman's theorem in Fig. Q3 (c).	7	L3	CO2
--	--	---	----	-----

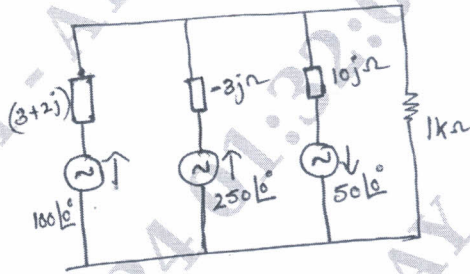


Fig. Q3 (c)

OR

Q.4	a. State and prove maximum power transfer theorem for DC circuit with variable load R_L .	6	L2	CO2
	b. For the circuit shown in Fig. Q4 (b). Find the Norton equivalent circuit across the terminal's a and b.	6	L3	CO2

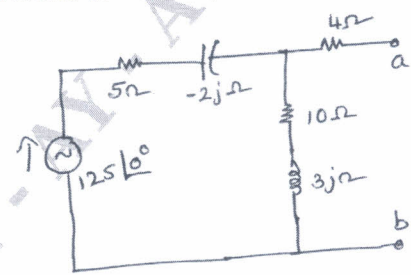


Fig. Q4 (b)

	<p>c. For the circuit shown in Fig. Q4 (c). Find the current through the load using Thevnin approach.</p>	8	L3	CO2
--	---	---	----	-----

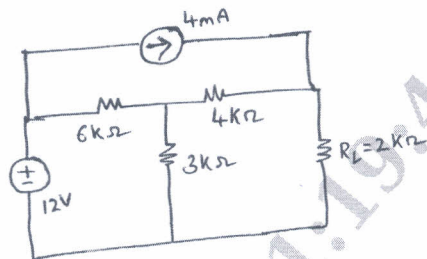


Fig. Q4 (c).

Module - 3

Q.5	<p>a. Explain the importance of study of initial conditions in electric circuit analysis and also explain the behavior of R, L and C elements for transients.</p>	10	L2	CO3
	<p>b. For the circuit shown in Fig.Q5 (b), steady state has been reached with the switch K on Position 'A'. The switch is moved to position B at $t = 0$. Determine the values of i, $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t(0^+)$.</p>	10	L3	CO3

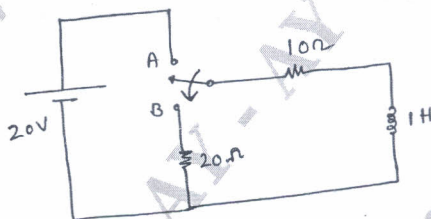


Fig. Q5 (b)

OR

Q.6	<p>a. For the network shown in Fig. Q6 (a) at $t = 0$, switch is opened, calculate v, $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0^+$.</p>	10	L3	CO3
	<p>b. For the network shown in Fig. Q6 (b). Switch is changed from position 1 to position 2 at $t = 0$. Steady condition have reaced before switching. Find the values of i, $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$.</p>	10	L3	CO3

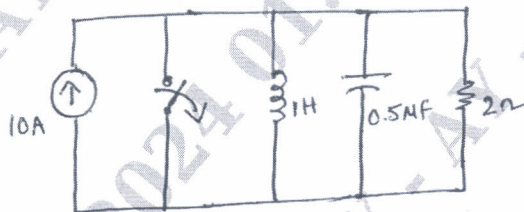


Fig. Q6 (a)

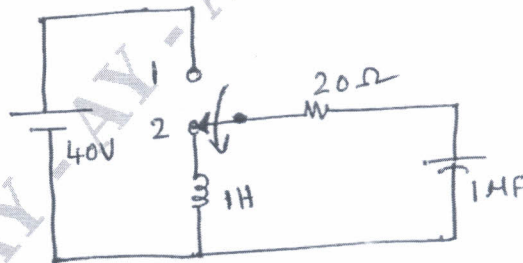


Fig. Q6 (b)

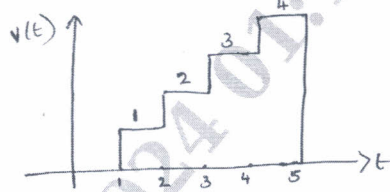
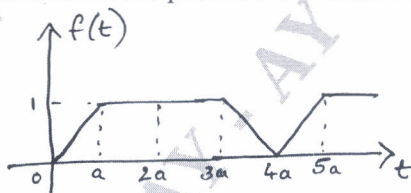
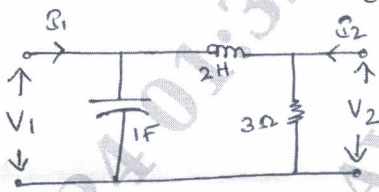
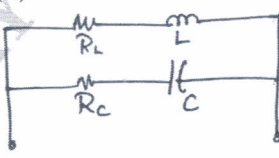
Module - 4					
Q.7	a.	Find the Laplace transform's of the following functions : (i) Unit step function (ii) $\sin \omega t$ (iii) $\cosh(at)$ (iv) $t \cdot \cos(at)$	10	L3	CO
	b.	Find the Laplace transform of the staircase waveform shown in the Fig. Q7 (b). 	10	L3	CO4
OR					
Q.8	a.	State and explain the following : (i) STEP function (ii) Impulses responses	10	L2	CO4
	b.	Find the Laplace transform of the periodic waveform shown in Fig. Q8 (b). 	10	L3	CO4
Module - 5					
Q.9	a.	Define the following : (i) Resonance (ii) Quality factor	4	L1	CO5
	b.	Obtain Z-parameters interms of Y-parameters.	6	L3	CO5
	c.	Find the H parameters for the circuit shown in the Fig. Q9 (c). 	10	L3	CO5
OR					
Q.10	a.	A series RLC circuit has $R = 10 \Omega$, $L = 0.01 \text{ H}$ and $C = 100 \mu\text{F}$, which is connected across 100 V supply. Calculate (i) F_r (ii) Q (iii) B.W (iv) I_r (v) f_1 and f_2	10	L3	CO5
	b.	Derive the expression of resonating frequency for the parallel resonant circuit shown in Fig. Q10 (b) 	10	L3	CO5

Fig. Q10 (b)
